



Province of the  
**EASTERN CAPE**  
EDUCATION

**NATIONAL  
SENIOR CERTIFICATE**

**GRADE 12**

**SEPTEMBER 2010**

**ELECTRICAL TECHNOLOGY**

**MARKS: 200**

**TIME: 3 hours**



---

This question paper consists of 12 pages.

---

**INSTRUCTIONS AND INFORMATION**

1. Answer ALL the questions.
2. Sketches and diagrams must be large, neat and fully labelled.
3. All calculations must be shown, and correct to two decimal places.
4. Answers must be clearly numbered.
5. A formula sheet is provided at the end of the paper.
6. Non-programmable calculators may be used.

**QUESTION 1        TECHNOLOGY, SOCIETY AND THE ENVIRONMENT**

- 1.1 Technological advancement has an influence on different cultures. Mention TWO examples where Electrical Technology has influenced your culture. (2)
- 1.2 Technological skills development is important for economic growth. State THREE competencies that are required of a successful entrepreneur. (3)
- 1.3 Mention ONE manner in which disease could be spread at the workplace. (1)
- 1.4 Mention TWO negative impacts that Electrical Technology has on the environment and give an example of each. (4)
- [10]**

**QUESTION 2        THE TECHNOLOGICAL PROCESS**

- 2.1 Your loving pet, a small fox terrier dog, was involved in an accident and the veterinary surgeon removed both its back legs. The dog cannot walk anymore and you are desperate to try and help the dog by designing a device to be strapped on so that the dog can move around using its front legs only. The device must use an electrical motor that will switch on when movement starts enabling the dog to move easily.
- 2.1.1 Name THREE specifications for the designed finished product that would solve the problem as stated above. (3)
- 2.1.2 Describe TWO methods of collecting data enabling you to understand and solve the design problem better. (2)
- 2.1.3 List TWO appropriate technological processes you can use to present and communicate your design effectively. (2)
- 2.1.4 When designing and building an artefact, what significant role does evaluating the solution have? (3)
- [10]**

**QUESTION 3      OCCUPATIONAL HEALTH AND SAFETY ACT**

- 3.1 Which THREE elements must be present for a fire to start? (3)
- 3.2 Name TWO precautions that one should take into account when using a multimeter. (2)
- 3.3 Explain what safety precautions you would institute in your workshop to prevent the spread of HIV/Aids. (2)
- 3.4 State ONE unsafe act that could take place in an electrical technology workshop. (1)
- 3.5 State ONE unsafe condition that could exist in an electrical technology workshop. (1)
- 3.6 Describe ONE good internal housekeeping rule. (1)
- [10]**

**QUESTION 4      THREE PHASE AC GENERATION**

- 4.1 Give TWO advantages of three phase generation over that of single phase generation. (2)
- 4.2 A three-phase delta connected motor draws 25 A from a 380 V supply at a factor of 0,86 lagging. Given  $I_L = 25 \text{ A}$ ,  $V_L = 380 \text{ V}$  and  $\cos \phi = -0,86$ , calculate:
- 4.2.1 The input power (3)
- 4.2.2 The apparent power (3)
- 4.3 The wattmeter consists of two coils. Briefly explain how these coils would be connected to the load and the supply. (2)
- [10]**


**QUESTION 5 PRINCIPLES ON AC ON RLC COMPONENTS**

- 5.1 A series circuit consists of a resistor of 25 ohms, an inductor of 0,3 henry and a 160 microfarad capacitor. The circuit is connected across a 150 V, 100 Hz supply. Given:  $R = 25 \Omega$ ,  $L = 0,3 H$ ,  $C = 160 \mu F$ ,  $V = 150 V$  and  $f = 100 Hz$ .

Calculate the following:

- 5.1.1 Inductive Reactance (3)
- 5.1.2 Capacitive Resistance (3)
- 5.1.3 Impedance (3)
- 5.1.4 Current flow (3)
- 5.1.5 Phase angle (3)
- 5.1.6 Resonant Frequency (3)

5.2

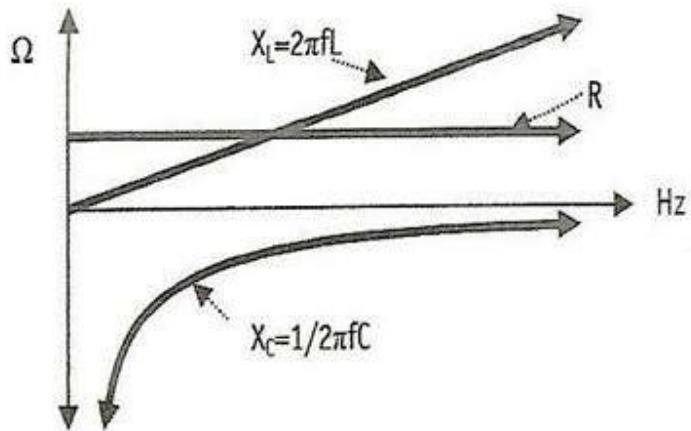

**Figure 5.2 Reactance of R, L and C versus frequency**

Study the figure above and state what effect frequency has on the following:

- 5.2.1 Resistance (2)
- 5.2.2 Inductive reactance (2)
- 5.3 Explain, with reference to  $X_L$  and  $X_C$  how you can determine if a series RLC circuit is INDUCTIVE or CAPACITIVE. (2)


- 5.4 Read the following statements and state if it is TRUE/FALSE. Write only the letter next to the number. (For example 5.4.7 T)
- 5.4.1 A series RLC circuit can have a higher voltage than the source voltage across the resistor. (1)
- 5.4.2 The impedance of a series RLC circuit is dependent on the source voltage. (1)
- 5.4.3 The total reactance of a series RLC circuit at resonance is zero. (1)
- 5.4.4 At frequencies below resonance in a parallel RLC circuit, the current lags the source voltage. (1)
- 5.4.5 The resonant frequency of a parallel circuit is the same as a series circuit using the same components when Q is very low. (1)
- 5.4.6 In a parallel RLC circuit, the total impedance is always greater than the resistance. (1)

[30]

**QUESTION 6        SWITCHING AND CONTROL**

- 6.1 There are four major devices in high-power rectification; two of those are the SCR and the TRIAC. State how the TRIAC differs from the SCR. (4)
- 6.2 Explain briefly how the DIAC operates. (4)
- 6.3 Draw fully labelled symbols for the following:
- 6.3.1 DIAC (2)
- 6.3.2 TRIAC (3)

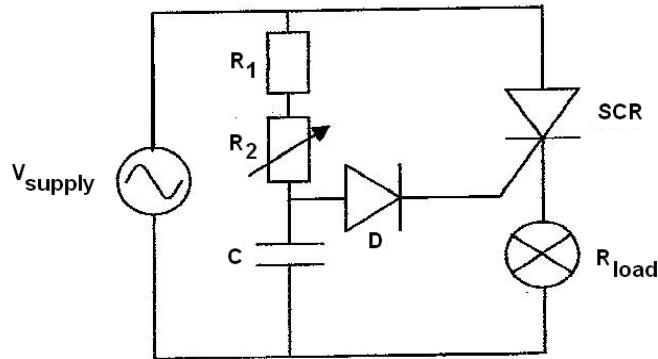6.4 Study the following figure and answer the questions that follow.



6.4.1 Answer TRUE/FALSE:

This circuit is a TRIAC light-dimming circuit with a trigger circuit to adjust the firing angle. (1)

6.4.2 Fill in the missing words:

The angle from the start of a cycle to the point of triggering is called the ... and the angle during which the SCR is on is called the ... (2)

6.4.3 Mention the process of controlling the voltage across the load (1)

6.4.4 Mention the function of the RC circuit. (3)

6.4.5 State the effect of  $R_1$  in the circuit. (2)

6.4.6 State the effect of  $R_2$  in the circuit. (3)

[25]

**QUESTION 7      OPERATIONAL AMPLIFIERS**

7.1 Various options are provided as possible answers to the following questions. Choose the correct answer and write the letter (A – D) next to the question number. For example (7.1.6 B)

7.1.1 The purpose of a comparator is to:

- A amplify an input voltage.
- B detect the occurrence of a changing input voltage.
- C produce a change in output when an input voltage equals a reference voltage.
- D maintain a constant output when the dc input voltage changes. (1)

7.1.2 To use a comparator for zero-level detection, the inverting is connected to:

- A The ground
- B The dc supply voltage
- C A positive reference voltage
- D A negative reference voltage (1)

7.1.3 The feedback path in an ideal OP-AMP integrator consists of a:

- A Resistor
- B Capacitor
- C Resistor and a capacitor in series
- D Resonant circuit (1)


7.1.4 The feedback path in an OP-AMP differentiator consists of a:

- A Resistor
- B Capacitor
- C Resistor and a capacitor in series
- D Resistor and a capacitor in parallel (1)

7.1.5 The OP-AMP comparator circuit uses:

- A Positive feedback
- B Negative feedback
- C Regenerative feedback
- D No feedback (1)

7.2

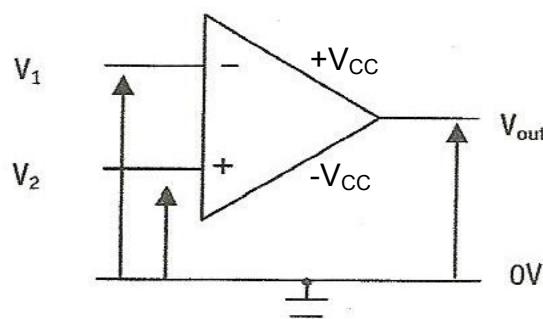

Determine the output voltage of the OP-AMP in the figure above for the following conditions:

- 7.2.1 If  $V_1 > V_2$  (1)
- 7.2.2 If  $V_1 < V_2$  (1)
- 7.2.3 If  $V_1 = V_2$  (1)
- 7.3 State THREE characteristics of an ideal OP-AMP. (3)
- 7.4 Mention THREE practical applications in which transistors are used. (3)
- 7.5 Why is it necessary for an OP-AMP to be supplied with both a positive and a negative power supply? (2)
- 7.6 What is the difference between the inverting and the non-inverting inputs of an OP-AMP? (4)
- 7.7 Name TWO advantages of negative feedback in OP-AMPS. (2)
- 7.8 State THREE advantages of negative feedback with reference to amplifiers. (3)  
[25]

**QUESTION 8      THREE-PHASE TRANSFORMERS**

- 8.1 A three-phase transformer with 3 500 turns on the primary is connected in delta-star to a supply voltage of 4 000 V. The full load line current on the primary is 20 A when the secondary line voltage is 380 V and the power factor is 0,9:
- 8.1.1 The secondary phase voltage (3)
- 8.1.2 The turns ratio (3)
- 8.2 There are various methods of connecting the primary and secondary windings of Three-phase transformers. State THREE. (3)
- 8.3 Mention THREE losses that occur in transformers. (3)
- 8.4 State TWO disadvantages of autotransformers. (2)
- 8.5 Overheating in transformers can be prevented by using various methods, mention ONE of these methods. (1)
- [15]**

**QUESTION 9      LOGIC CONCEPTS AND PLCs**

- 9.1 The PLC is CHEAPER and ECONOMICAL for a control panel with more than ten relays. This is one of the advantages of the PLC. Mention THREE more advantages of PLCs. (3)
- 9.2 There are basically THREE types of programming languages used for PLC programming. Name these THREE languages. (3)
- 9.3 Write down the question number and draw the corresponding symbol of:

Circuit Diagram Symbol	Description	Ladder Diagram Symbol
9.3.1	Normally open switch or other type of normally open device used as input to the PLC	9.3.4
9.3.2	Normally close switch or other type of normally close device used as input to the PLC	9.3.5
9.3.3	Relay or other type of device used as output from a PLC	9.3.6

(6)

9.4 Develop a truth table for this Boolean expression:

$$\text{Output} = \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} + ABC \quad (4)$$

9.5 Using Boolean algebra techniques simplify the expression in QUESTION 9.4. (7)

9.6 With reference to the truth table for the Boolean expression in QUESTION 9.4 above, draw the following:

9.6.1 The logic gate network that would represent the simplified Boolean expression in QUESTION 9.5. (8)

9.7 Sequential logic systems are combination systems with some of the outputs fed back as inputs. The simplest sequential system is multivibrators (flip-flop). Mention TWO types of multivibrators. (2)

9.8 Mention ONE key characteristic of each of the multivibrators in QUESTION 9.7. (2)

[35]

#### QUESTION 10      THREE PHASE MOTORS AND CONTROL

10.1 Name THREE tests that must be performed on the windings of a new electric motor before its put into operation. (3)

10.2 Mention the TWO factors which determine the speed of an induction type alternating current motor. (2)

10.3 Explain how the direction of a rotation can be changed in a three-phase motor. (1)

10.4 Briefly explain the operation of an induction motor. (8)

10.5 Mention FOUR examples of safety devices that could be included in the safety circuit of a motor starter. (4)

10.6 What is the purpose of the no-volt coil in a motor starter? (2)

10.7 Briefly explain the star-delta starting process. (6)

10.8 Electrical motors have internal losses which can be categorized into three types. Mention TWO of these categories. (2)

10.9 Why is star-delta starters used to start three-phase motors? (2)

[30]

**TOTAL: 200**

## ELECTRICAL TECHNOLOGY

### FORMULA SHEET

$$Z = \sqrt{R^2 + (XI \approx Xc)^2}$$

$$Vr = It \times R$$

$$It = Vt/Z$$

$$Z = \sqrt{R^2 + XI^2}$$

$$Z = \sqrt{R^2 + Xc^2}$$

$$VI = It \times XI$$

$$Vc = It \times Xc$$

$$It = \sqrt{Ir^2 + (Ic \approx II)^2} \quad Ir = Vr/R \quad II = Vc/XI \quad Ic = Vc/Xc \quad \cos \emptyset = Ir/It$$

$$XI = 2\pi FL$$

$$Xc = 1/2\pi FC$$

$$P = V \times I \times \cos \emptyset \quad \cos \emptyset = R/Z \quad \tan \emptyset = XI - Xc/R \quad \cos \emptyset = P/VA$$

$$P = I^2 R$$

$$I_{act} = I \times \cos \emptyset$$

$$I_{react} = I \times \sin \emptyset$$

Star

Delta

$$II = I_{ph}$$

$$II = \sqrt{3} \times I_{ph}$$

$$VI = \sqrt{3} \times V_{ph}$$

$$VI = V_{ph}$$

$$F = Pn/60$$

$$P = \sqrt{3} VI \times II \times \cos \emptyset$$

$$S = \sqrt{3} \times VI \times II \quad V_P/V_S = N_P/N_S = I_S/I_P \quad \text{or/of} \quad V_1/V_2 = N_1/N_2 = I_2/I_1$$

Efficiency = Output/Input

**FORMULEBLAD****ELEKTRISCHE TECHNOLOGIE**

$$V_L = I_L \times X_L$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + (X_L \approx X_C)^2}$$

$$V_R = I_L \times R$$

$$I_L = V_R/Z$$

$$V_C = I_L \times X_C$$

$$X_L = 2\pi f L \quad X_C = 1/(2\pi f C)$$

$$I_t = \sqrt{I_r^2 + (I_C \approx I_L)^2} \quad I_r = V_r/R \quad I_L = V_C/X_L \quad I_C = V_C/X_C \quad \cos \theta = I_r/I_t$$

$$P = V \times I \times \cos \theta \quad \cos \theta = R/Z \quad \tan \theta = X_L - X_C/R \quad \cos \theta = P/V_A$$

$$P = I^2 R$$

$$I_{act} = I \times \cos \theta$$

$$S_{ter} = I \times \sin \theta$$

$$I_L = I \times \sin \theta$$

$$V_L = \sqrt{3} \times V_{ph}$$

$$Effektiviteit = \frac{\text{Uitgewerkte lijnstroom}}{\text{Lijnstroom}}$$

$$P = \sqrt{3} V_L \times I \times \cos \theta$$

$$F = P/n_0$$

$$S = \sqrt{3} \times V_L \times I \quad V_P V_S = N_p / N_s = I_s / I_p \quad \text{of} \quad V_L V_2 = N_1 / N_2 = I_2 / I_1$$

**TOTAL: 200**

- [30]  
(2) **skakel?**  
10.9 Wanneer word ster-delta aansluiters gebruik om drie-fase motors aan te  
kan word. Noem TWE van hierdie kategorie.
- (2) **Elektriese motors besit intieme verliese, wat in drie type kategoriee geplaas**  
10.8  

(6) **Verduidelik kortlik die werkings van die ster-delta aansluitproses.**  
10.7  

(2) **Wat is die doel van die nul-las spoei in 'n motor se aansluitring?**  
10.6  

(4) **Noem VIER voorbeelde van veiligheidsstelle wat ingesluit kan word in  
die veiligheidskering van 'n motor se aansluitring.**  
10.5  

(8) **Verduidelik kortlik die werkings van 'n induksie-motor.**  
10.4  

(1) **Verduidelik hoe die rigting van rotasie in 'n drie-fase motor verander kan  
word.**  
10.3  

(2) **Noem TWE faktore wat die spoed van 'n induksie type wisselstoombuur  
bepaal.**  
10.2  

(3) **Elektriese motor voorvat dit in werkings gesetel word.**  
10.1 **Noem DRIE toetses wat uit gevouer moet word op die windings van 'n nuwe**

#### **VRAG 10 DRIE-FASE MOTORS EN BEHEER**

- [35]  
(3) **VRAG 9.7.**  
9.8 **Noem EEN kenmerkende eienskap vir elk van die multivibrators in  
multivibrators.**  

(2) **Opeenvolgende logiese sisteme is kombinasie sisteme met sommige van  
die uitsette wat teruggevorder word as insette. Die eenvoudigste  
opeenvolgende systeem is multi-vibrators (flip-flop). Meid TWE soortte  
multivibrators.**  
9.7  

(8) **uitdrukking in VRAG 9.5 verteenwoordig.**  
9.6.1 **Die logiese hek-netwerk wat die vereenvoudigde Boolese  
uitdrukking in VRAG 9.4 hierbo, teken die volgende:**  
9.6 **Met vereenvoudiging na die waarheidsstabiel vir die Boolese uitdrukking in  
VRAG 9.4 hierbo, teken die volgende:**  

(7) **VRAG 9.4.**  
9.5 **Deur Boolese Algebra te gebruik, vereenvoudig die uitdrukking in  
uitset =  $\underline{ABC} + \underline{ABC} + ABC + ABC$**   

(4) **Ontwikkel 'n waarheidsstabiel vir die volgende Boolese uitdrukking:  
9.4**

(6)	9.3.6	as uitset by die PLC apparaat wat gebruik word Releé of ander type	9.3.6
9.3.2	9.3.5	die PLC gebruik word as inset by geslotte apparaat wat of ander type normal Normal geslotte skakelaar	
9.3.1	9.3.4	as inset by die PLC apparaat wat gebruik word ander type normal oop Normal oop skakelaar of	
Kringdiagram simbool	Beskrywing	Leerdiaagram-simbool	

- 9.3 Skryf die vragnommer neer en teken die ooreenstemmende simbool van:
- 9.2 Daar bestaan basies drie tipes programmeertale vir die programmeering van PLC. Noem die DRIE tale.
- (3) Die PLC is GOEDKOPER en meer EKONOMIES vir 'n paneel met meer as tien releés. Dit is een van die voordele van 'n PLC. Noem nog DRIE meer voordele.
- (3) Daar is verskeie tipes van verliese wat by transformators voorkom.
- 9.1 Die PLC is GOEDKOPER en meer EKONOMIES vir 'n paneel met meer as tien releés. Dit is een van die voordele van 'n PLC. Noem nog DRIE meer voordele.

## VRAAG 9 LOGIKA KONSEPTE EN PLC's

- [15]
- (1) Noem EN van hierdie metodes.
- 8.5 Overheiting by transformators kan op verskeie wyse voorkom word.
- (2) Noem TWE nadelle van auto-transformators.
- (3) Noem DRIE tipes van verliese wat by transformators voorkom.
- (2) Daar is verskeie metodes van koppling by die primêre en sekondêre windings van 'n driе-fase transformator. Noem TWE.
- (3) 8.1.2 Die windingsverhouding
- (3) 8.1.1 Die sekondêre fase-spanning
- Bereken:
- 8.1 In driе-fase transformator met 3 500 draine op die primêre spoel is verbind in delta-stern aan 'n voorstelling van 4 000 V. Die vollaas lysroom op die primêr is 20 A as die sekondêre lyn spanning 380 V en die arbeidsfaktor 0,9 is:

Die vollaas lysroom op die primêr is 20 A as die sekondêre lyn spanning 380 V en die arbeidsfaktor 0,9 is:  
 in driе-fase transformator met 3 500 draine op die primêre spoel is verbind in delta-stern aan 'n voorstelling van 4 000 V. Die vollaas lysroom op die primêr is 20 A as die sekondêre lyn spanning 380 V en die arbeidsfaktor 0,9 is:

## VRAAG 8 DRIЕ-FASE TRANSFORMATORS

7.2

Bepaal die uitset spanning van die OP-VERSTERKER in die figuur hierbo  
vir die volgende toestande:

$$7.2.1 \quad \text{As } V_1 > V_2 \quad (1)$$

$$7.2.2 \quad \text{As } V_1 < V_2 \quad (1)$$

$$7.2.3 \quad \text{As } V_1 = V_2 \quad (1)$$

7.4 Noem DRIE praktiese toepassings waarin transistors gebruik word.


7.5 Waarom moet 'n OP-VERSTERKER voorstien word van 'n positiewe- en negatiewe kragvoorsiening?

7.6 Wat is die verskil tussen die omgekeerde- en nie-omgekeerde insette van 'n OP-VERSTERKER?

7.7 Noem TWEE voordele van negatiewe terugvoer by OP-VERSTERKERS.

7.8 Melди DRIE voordele van negatiewe terugvoer met verwysing na verstekers.


[25]  
(3)

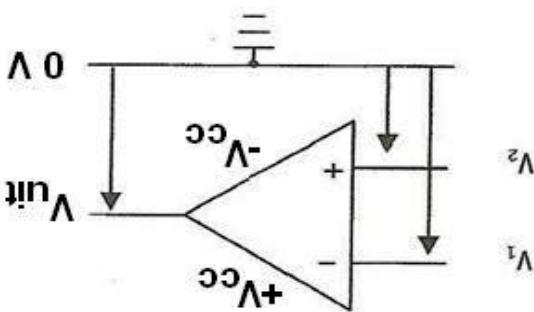

- 7.1.1 Die doel van 'n vergelyker is om:
- (1) vraagnommer, byvoorbereel (7.1.6 B)
- 7.1 Verskeie moontlike antwoorde word vir die volgende vrae gegee. Kies die korrekte antwoord en skryf slegs die letters (A – D) teenoor die vraag.
- 7.1.2 Om die vergelyker te gebruik as nul valk waarnemer, word die omkeer verbind aan:
- (1) insetspanning verander.
- 7.1.3 Die terugvoer in 'n ideale OP-VERSTERKER integreerder bestaan uit:
- (1) Resistor
- 7.1.4 Die terugvoer in 'n OP-VERSTERKER as differensieerde bestaan uit:
- (1) Resistor
- 7.1.5 Die OP-VERSTERKER as vergelykerking gebruik:
- (1) Geen terugvoer

[25]

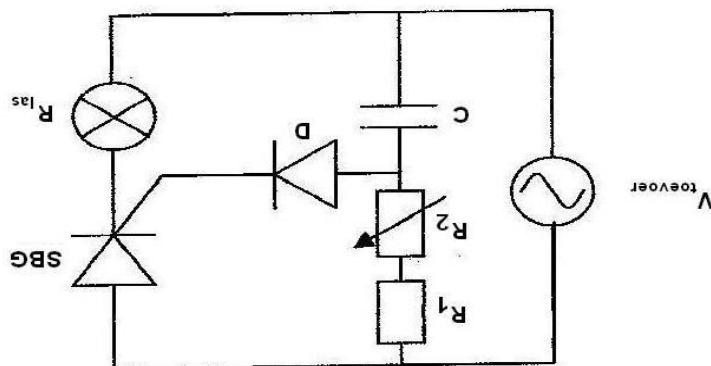- 6.4.1 Antwoord WAAR/VALS:
- Die kring is 'n TRIAK ligverdowingsskring, met 'n snellerkring om die antisithoeke te verstel.
- 6.4.2 Voltooi die sin deur die ontbrekende woorde in te vul:
- Die hoeke van die begin van die sklus tot by die punt van snellerking word die ... genoem, en die hoeke waartydens die SBG aan is, word die ... genoem.
- 6.4.3 Noem die proses wat gebruik word om die spanning oor die las te beheer.
- 6.4.4 Gee die funksie van die RC-kring.
- 6.4.5 Noem die doel van  $R_1$  in die kring.
- 6.4.6 Noem die doel van  $R_2$  in die kring.



- 6.4 Bestudeer die volgende diagram en beantwoord die vrae wat volg:

- 5.4 Lees die volgende stellings en bepaal of hulle WAAR/VALS is. Skryf slegs die letter langs die nommer. (byvoorbeeld 5.4.7 W)
- 5.4.1 In Serie RLC-kring kan in hoër spanning oor die weerstand as die toevoer bron he.
- 5.4.2 Die impedansie van in serie RLC-kring is afhanklik van die toeverspanning.
- 5.4.3 Die totale reaktansie van in serie RLC-kring by resonansie is nul.
- 5.4.4 By frekwensies onder resonansie in in parallelle RLC-kring volg die stroom die spanning van die bron.
- 5.4.5 Die resonante frekwensie van in parallelle RLC-kring is die selfde as die van in serie kring wat dieselfde komponente gebruik as Q bain lag is.
- 5.4.6 In in parallelle RLC-kring sal die totale impedansie altyd groter wees as die weerstand.
- (1) 6.1 Daar is vier hooftoestelle wat gebruik word in hoe-spanningsgekykrigting, waarvan twee die SBG en die TRIAK is. Verduidelik hoe die TRIAK verskill van die SBG.
- (4) 6.2 Verduidelik kortlik die werkings van die DIAK.
- 6.3 Teken 'nenvolle benoemde simbool van die volgende:
- (2) 6.3.1 DIAK
- (3) 6.3.2 TRIAK

[30]

## VRAG 6 SKAKEL EN BEHEER

5.2

5.2.1 Weerstand

5.2.2 Induktieve reactansie


5.3

Verduidelik, met verwysing na  $X_L$  en  $X_C$ , hoe jy kan bepaal of 'n RLC-kring INDUKTIEF of KAPASITIEF is.

volgende het:

Bestudeer die bostande figuur engee die effek wat frekvensie op die

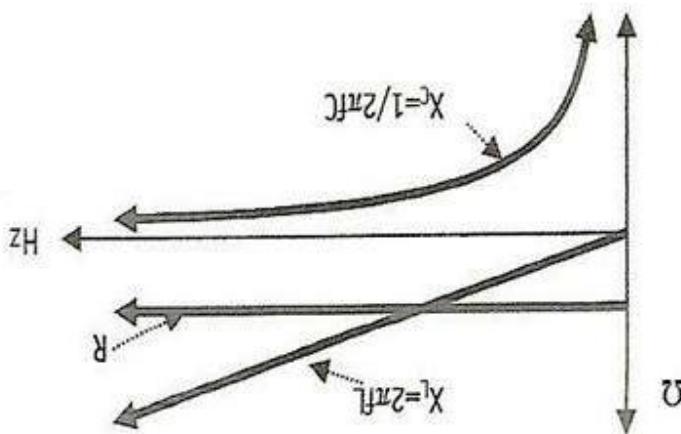Figuur 5.2 Reaktansie van  $R$ ,  $L$  en  $C$  teenoor frekvensie



5.2

5.1.6 Resonante Frekvensie

5.1.5 Fasehoek

5.1.4 Stroomvloei

5.1.3 Impedansie

5.1.2 Kapasitive Reaktansie

5.1.1 Induktieve Reaktansie

Bereken die volgende:

$$C = 160 \mu\text{F}, V = 150 \text{ V en } f = 100 \text{ Hz}.$$

In toeval van 150 V, 100 Hz. Gegee:  $R = 25 \Omega$ ,  $L = 0,3 \text{ H}$ ,

henry en 'n kapasitor van 160 mikrofarad. Die kring word gekoppel aan 0,3

5.1

## VRAG 5 BEGINSELS VAN RLC-KRINGE

		<b>VRAAG 3 BEROEPSVEILIGHED EN GESONDHEIDSWEET</b>
3.1	Wat ter DRIE elemente moet teenwoordig wees voor dat 'n brand kan uitbreek?	
3.2	'n Noem TWEE voorborgmaatreëls wat in berekening gebring moet word as 'n multimeter gebruik.	
3.3	'n Verduidelik watter veiligheidsmaatreëls ly in jou werkswinkel sal instel om te voorKom dat MILV/Vigs sal versprei.	
3.4	Noem EEN onveilige handeling wat in 'n elektriese tegnologie-werkswinkel kan plaasvind.	
3.5	Noem EEN onveilige toestand wat in 'n elektriese tegnologie-werkswinkel kan voorKom.	
3.6	Geen EEN goede interne huisregel.	
4.1	Geen TWEE voordele van driefase krag-opwekking bo enkel-fase krag-opwekking.	
4.2	In driefase motor wat in delta gekoppel is trek 25 A vanaf 'n 380 V toevoer met 'n naloopende faktor van 0,86. Gegee $I_L = 25 \text{ A}$ , $V_L = 380 \text{ V}$ en $\cos \phi = -0,86$ , bereken:	
4.2.1	Die insetdrywing	(3)
4.2.2	Die skyndrywing	(3)
4.3	Die wattmeter bestaan uit twee spoele. Verduidelik kortlik hoe hierdie spoele aan die las en toevoer gekoppel is.	(2)
		[10]

		<b>VRAAG 1 TECHNOLOGIE, GEMEENSCHAFT UND UMWELT</b>
1.1	Tegnologie beïnvloed die voordeiing van verskillende kultuur. Noem TWE.	Technologie beïnvloed die voordeiing van kultuur beïnvloed.
1.2	Tegnologie varidighedsontwikkeling is belangrik vir ekonomiese groei.	Geen DRIE eigenskappe wat benodig word om suksesvolle ondernemer te wees.
1.3	Noem EEN wye waarop sieltes in die werksplek versprei kan word.	Noem EEN wye waarop sieltes in die werksplek versprei kan word.
1.4	Noem TWE negatiewe invloede wat Elektriese Tegnologie op die omgewing het en gee h voorbeeld van elk.	Noem TWE negatiewe invloede wat Elektriese Tegnologie op die omgewing het en gee h voorbeeld van elk.
		<b>VRAAG 2 DIE TEGNOLGIESE PROSES</b>
2.1	Jou geliefde troetelidier, h klein fox terrier-hond, was betrokke in h ongeluk en die veerarts het albei sy agterbenne afgesit. Die hond kan nou nie meer loop nie en jy vole desperaat om hom te probeer help deur h apparaat, wat aan hom gekoppel kan word, te ontwerp, sodat hy rond kan beweeg deur slegs sy voorbeen te gebriuk. Die apparaat moet gebriuk maak van andrywing deur h type elektriese motor, wat aanskakel sodra beweging waargeneem word en die hand help om makliker te beweeg.	Jou geliefde troetelidier, h klein fox terrier-hond, was betrokke in h ongeluk wat sal voldoen om die probleem hierbo op te los.
2.1.1	Noem DRIE spesifikaasies vir die ontwerp van die voltoide produk wat sal voldoen om die probleem hierbo op te los.	Beskryf TWE metodes om inligting te versamel sodat jy die probleem better kan verstaan en sodende die ontwerpproblem makliker kan oplos.
2.1.2	Wat sal voldoen om die probleem hierbo op te los.	Beskryf TWE metodes om inligting te versamel sodat jy die ontwerp aan die evaluaasie van die oplossing?
2.1.3	Lys TWE gespesiale tegnologiese prosesse wat jy kan gebruik om jou ontwerp aan te bied en effektiel te kommunikeer.	Gedurende die ontwerp en bou van h projek, watter belangrike rol speel die evaluaasie van die oplossing?
2.1.4	(2)	(3)

## **INSTRUKSIES EN INLIGTING**

1. Beantwoord AL die vrae.
2. Sketsen en diagramme moet groot, netjies en ten volle benoem wees.
3. Alle berekening moet getoon en tot TWEE desimale plekke afgerond word.
4. Antwoord moet duidelik getoon word.
5. 'n Formule blad is aan die einde van die vraestel.
6. Nie-programmable sakrekenaars mag gebruik word.

Hierdie varestel bestaan uit 12 bladsye.



TYD: 3 uur

PUNTE: 200

## ELKTRIESE TEGNOLOGIE

SEPTEMBER 2010

GRAAD 12

SENIOR SERTIFIKAAT  
NASIONALE

EDUCATION  
PROVINCE OF THE  
EASTERN CAPE

