

**NATIONAL
SENIOR CERTIFICATE**

GRADE 11

NOVEMBER 2013

**ELECTRICAL TECHNOLOGY
MEMORANDUM**

MARKS: 200

This memorandum consists of 11 pages.


QUESTION 1: OCCUPATIONAL HEALTH AND SAFETY USE AND CARE OF TOOLS AND MEASURING INSTRUMENT

- 1.1 Safety is the main consideration behind all rules and regulations contained in the CODE of PRACTICE for the wiring of electrical installation. $\checkmark\checkmark$ (2)
- 1.2
- Not wearing safety clothing. \checkmark
 - Measuring current in series. \checkmark
 - Working at an unsafe speed. \checkmark
 - Horseplay in the workshop. \checkmark (Any 2) (2)
- 1.3 1.3.1 $F = \frac{\text{No of div}}{\text{Time/div}}$ \checkmark
- $$= \frac{8}{2,5 \times 10^{-6}} \checkmark$$
- $$= 3,2 \text{ MHz } \checkmark$$
- (3)
- 1.3.2 RMS value is the amount of DC value that is required for producing the same amount of power as the AC waveform. \checkmark (1)
- 1.3.3 $V_{\text{RMS}} = 0,707 \times \text{volt/div} \times \text{no of div.}$
- $$= 0,707 \times 5 \times 3 \checkmark$$
- $$= 10,61 \text{ V } \checkmark$$
- (2)
- [10]**

QUESTION 2: SINGLE-PHASE AC GENERATION SINGLE PHASE TRANSFORMERS

- 2.1 As the conductor loop is rotated through the magnetic field, \checkmark each of the two sides of the loop move through the magnetic field cutting the magnetic lines of flux. $\checkmark\checkmark$
- This action induces an alternating voltage across the conductor loop. \checkmark (4)

2.2

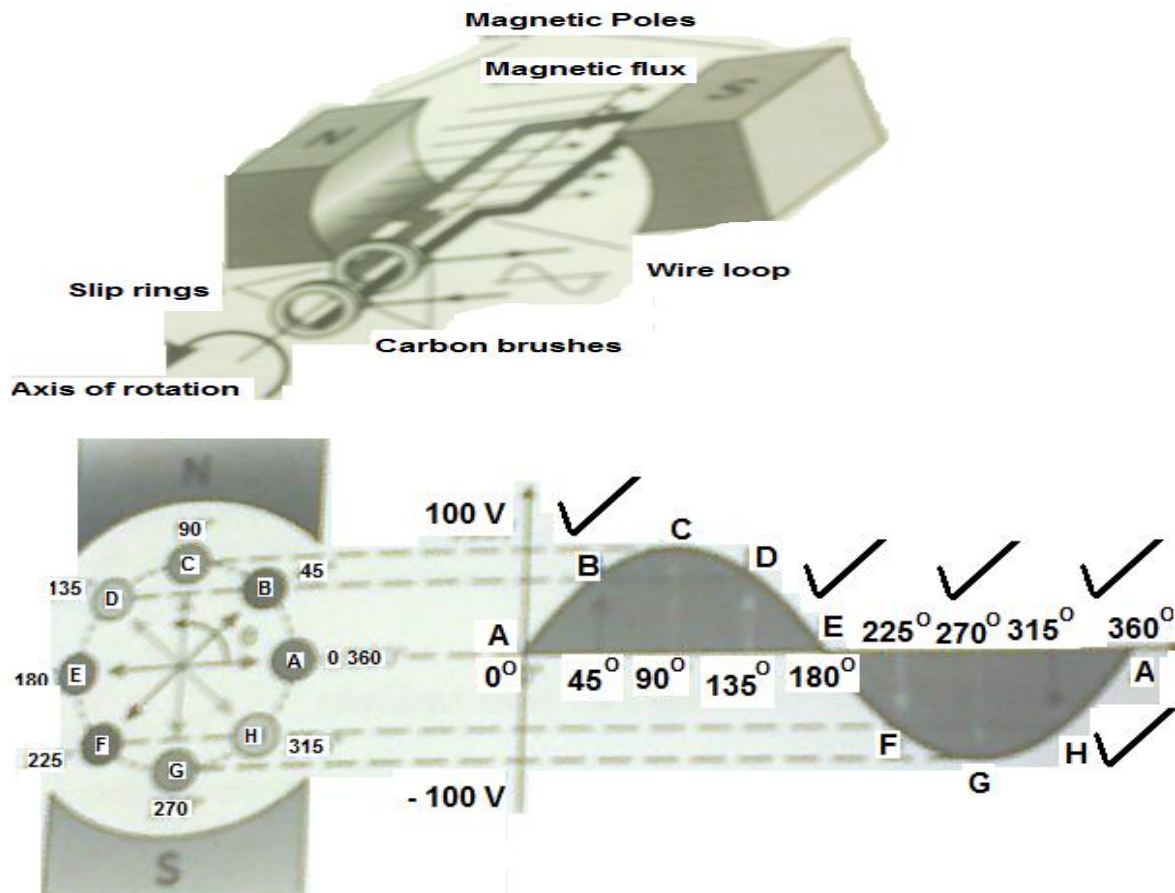

The mechanical rotation energy is transformed into electrical, ✓ which is then distributed to the point of consumption. ✓

(7)

2.3

When the wire loop is perpendicular to the field. ✓✓

(2)

2.4

- The rate of rotation ✓ i.e. if the rotation is faster, the induced *emf* increases, ✓ which in turn increases the current in the coil. ✓ This will be shown by a current detecting instrument called galvanometer. ✓
- The ends of the coil nearest to the pole become the same polarity as the pole in which direction the coil is rotating. ✓✓

(6)

2.5

$$2.5.1 \quad F = \frac{\text{rev}}{\text{sec}} \quad \checkmark$$

$$= \frac{1\,500}{60} \quad \checkmark$$

$$= 25 \text{ rev/sec} \quad \checkmark$$

(3)

$$\begin{aligned}
 2.5.2 \quad T &= \frac{1}{F} \sqrt{} \\
 &= \frac{1}{25} \sqrt{} \\
 &= 0,004 \text{ sec } \sqrt{}
 \end{aligned} \tag{3}$$

$$\begin{aligned}
 2.5.3 \quad \text{Emf} &= 2\pi B A n N \sin\theta \sqrt{} \\
 &= 2 \cdot \pi \cdot 0,05 \cdot 0,004 \cdot 25 \cdot 100 \cdot \sin 90^\circ \sqrt{} \\
 &= 3,14 \text{ V } \sqrt{}
 \end{aligned} \tag{3}$$

$$\begin{aligned}
 2.5.4 \quad e &= E \sin\theta \sqrt{} \\
 &= 3,14 \cdot \sin 60^\circ \sqrt{} \\
 &= 2,72 \text{ V } \sqrt{}
 \end{aligned} \tag{3}$$

$$\begin{aligned}
 2.5.5 \quad V_{\text{RMS}} &= 0,707 \cdot V_{\text{max}} \sqrt{} \\
 &= 0,707 \cdot 3,14 \sqrt{} \\
 &= 2,22 \text{ V } \sqrt{}
 \end{aligned} \tag{3}$$

2.6 2.6.1 It is used to lower or raise the voltage with the corresponding increase or decrease the current. $\sqrt{}$ (2)

- 2.6.2
- Iron losses $\sqrt{}$
 - Stray losses. $\sqrt{}$
- (2)

$$\begin{aligned}
 2.6.3 \quad N_s &= \frac{V_s N_p}{V_p} \sqrt{} \\
 &= \frac{230 \cdot 3\,600}{11\,000} \sqrt{} \\
 &= 75,27 \\
 &\approx 76 \text{ turns } \sqrt{}
 \end{aligned} \tag{3}$$

$$\begin{aligned}
 2.6.4 \quad I_p &= \frac{V_s I_s}{V_p} \sqrt{} \\
 &= \frac{230 \cdot 60}{11\,000} \sqrt{} \\
 &= 1,25 \text{ A } \sqrt{}
 \end{aligned} \tag{3}$$


$$\begin{aligned}
 2.6.5 \quad S &= VI \sqrt{} \\
 &= 230 \cdot 60 \sqrt{} \\
 &= 13800 \text{ VA} \\
 &= 13,8 \text{ kVA } \sqrt{}
 \end{aligned} \tag{3}$$

2.7 More insulation is need. $\sqrt{}$ (1)

2.8 PT-safely measures the voltage in a high voltage power lines. $\sqrt{}$
 CT-safely measures the current in a high current power lines. $\sqrt{}$ (2)

QUESTION 3: SINGLE-PHASE MOTORS AND PROTECTION DEVICES

3.1

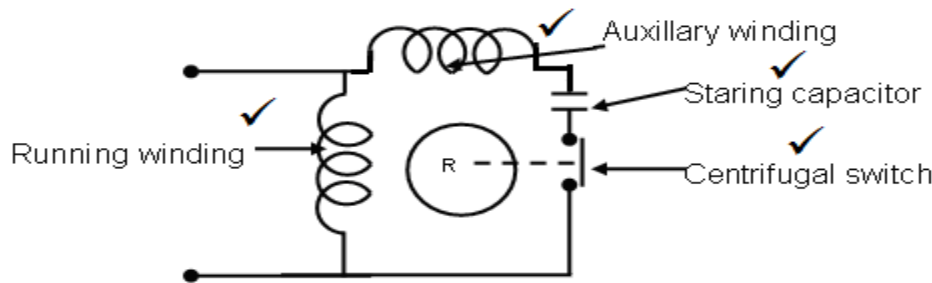

(4)

3.2

To open up at about 75% of operating speed and remove the starting capacitor and starting winding from the supply. ✓✓


(2)

3.3

The motor will not automatically start because the two phase effect has not been created. ✓✓

(2)

3.4

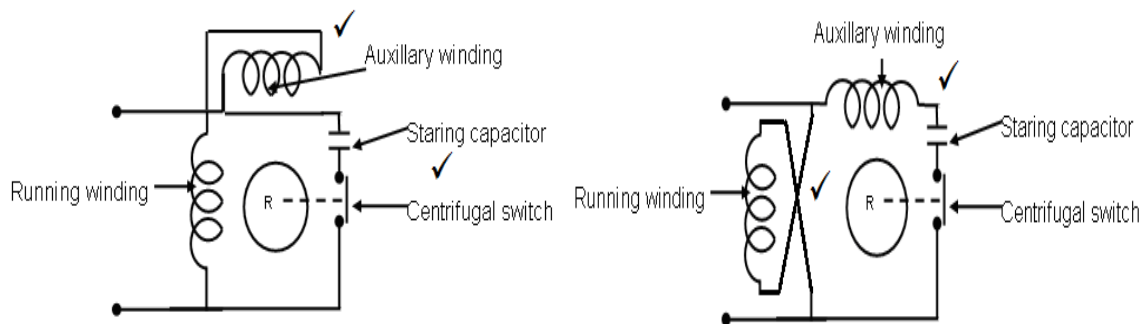

(4)

3.5

The two capacitors create a phase shift between the current in the main winding and the current in the starting winding. ✓✓✓

(3)

3.6

- Stop button: ✓ this is used to stop the motor we make use of a similar Spring-loaded push button. ✓
- Zero-volt coil: ✓ Starters using magnetic contactors usually derive their power supply for the contactor coil from the same source as the motor supply. ✓
- Overload protection: ✓ Overload protection is there to prevent the current drawn by the load from exceeding a certain value. ✓ Small grinders ✓

(6)

3.7

- Small grinders ✓
- Small fans ✓
- Blowers ✓
- Washing machine ✓
- Pumps ✓
- refrigerator ✓
- Compressors ✓

(Any 1)


(1)

3.8

The auxiliary winding cannot support high currents for more than a few seconds without being damaged because it is made of fine wire. ✓✓

(2)

3.9

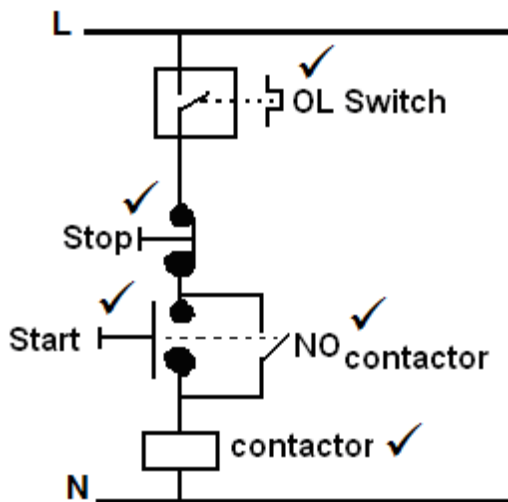

(5)

3.10 To ensure that there is no leakage between the windings and earth. ✓

(1)

[30]

QUESTION 4: SEMI-CONDUCTOR DEVICES POWER SUPPLIES AMPLIFIERS


- 4.1
- By increasing the current above the holding current. ✓
 - By applying small voltage to the gate. ✓
 - By applying the pulse to the gate of the SCR. ✓
 - By allowing the supply voltage to exceed the forward-breakover voltage. ✓

(4)

- 4.2 Firing angle is the angle when the SCR is turned off. ✓
Conducting angle is the angle when the SCR is conducting. ✓

(2)

4.3 4.3.1

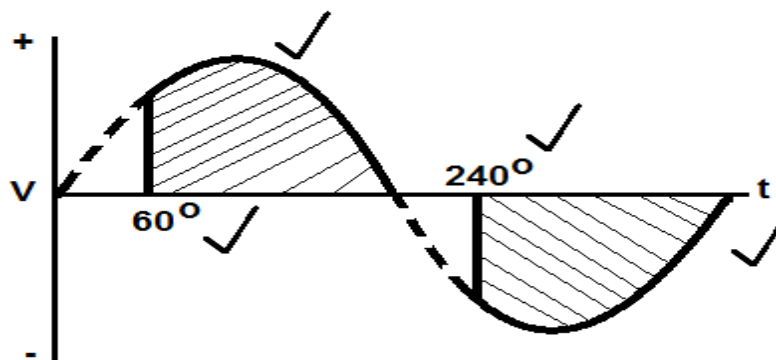


(4)

- 4.3.2 The capacitor will take longer time to charge and reach the required voltage to trigger the DIAC. ✓ This means the TRIAC will be triggered later and it will conduct for a shorter period, ✓ causing the lamp to dim. ✓ (3)
- 4.3.3 To limit the current when the value of R_2 is set to its minimum. ✓ (1)

- 4.4 The physical size of a TRIAC is dependent on the supply voltage it will be connected to as well as the maximum current that will flow through it. ✓✓ (2)


4.5

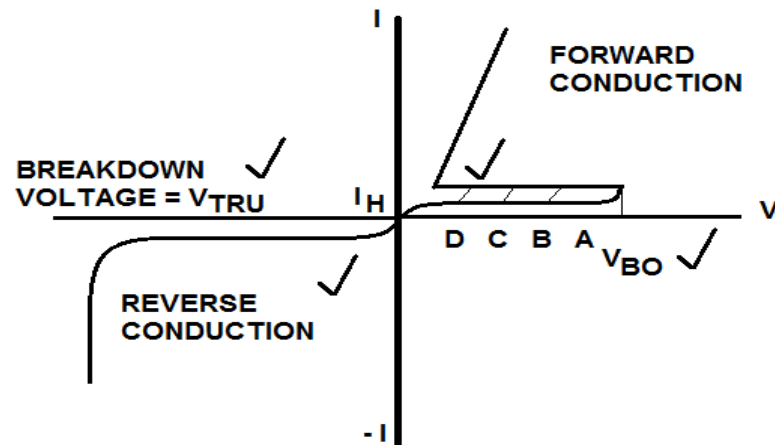

(4)

4.6

4.6.1

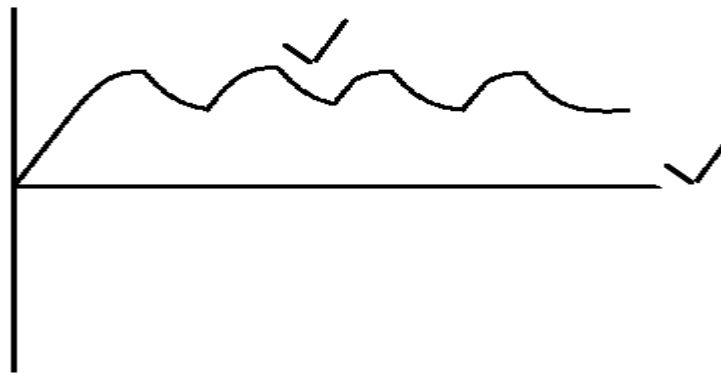


(2)

4.6.2 To smoothen the ripples to create a clean DC supply by storing the charge and releasing it when needed. ✓✓

(2)

4.7

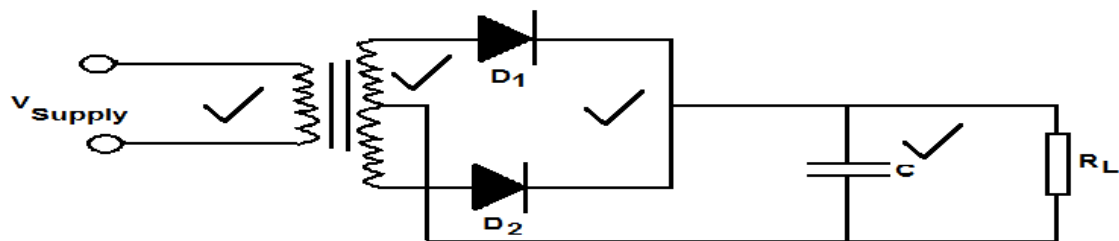

(4)

4.8




(2)

4.9

Biasing is the method of establishing predetermined voltage or current at various points of an electronic circuit for the purpose of establishing proper operating conditions in electronic component. ✓✓

(2)

4.10 4.10.1

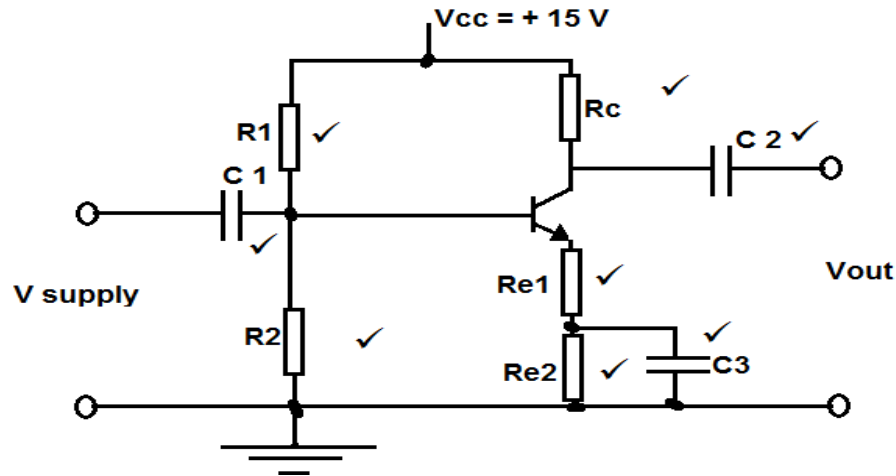

(8)

$$\begin{aligned}
 4.10.2 \quad \text{Current gain} &= \frac{\Delta I_c}{\Delta I_b} \checkmark \\
 &= \frac{6 \times 10^{-3}}{140 \times 10^{-6}} \checkmark \\
 &= 42,86 \checkmark
 \end{aligned}$$

(3)

- 4.11
- Common base. \checkmark
 - Common Collector \checkmark
 - Common emitter \checkmark

(Any 2) (2)

- 4.12
- The resistor of the LDR is high. \checkmark
 - Voltage across the LDR is also high. \checkmark
 - But $V_{be} = V_{LDR}$ so the $V_{be} \geq 0,6 \text{ V}$ \checkmark
 - Transistor will be switched on like a close switch. \checkmark
 - Maximum current flows through the LED and the transistor, switching the LED on. \checkmark

(5)

[50]**QUESTION 5: RLC SERIES CIRCUITS**


$$\begin{aligned}
 5.1 \quad 5.1.1 \quad X_L &= 2\pi fL \\
 &= 2 \cdot \pi \cdot 50 \cdot 75 \cdot 10^{-3} \checkmark \\
 &= 23,56 \, \Omega \checkmark \\
 X_C &= \frac{1}{2\pi fC} \\
 &= \frac{1}{2 \cdot \pi \cdot 50 \cdot 220 \cdot 10^{-6}} \checkmark \\
 &= 14,47 \, \Omega \checkmark \\
 Z &= \sqrt{R^2 + (X_L - X_C)^2} \checkmark \\
 &= \sqrt{22^2 + (23,56 - 14,47)^2} \checkmark \\
 &= 23,8 \, \Omega \checkmark
 \end{aligned}$$

(7)

$$\begin{aligned}
 5.1.2 \quad I &= \frac{V}{Z} \\
 &= \frac{24}{23.8} \\
 &= 1,01 \text{ A} \quad \checkmark
 \end{aligned} \tag{3}$$

$$\begin{aligned}
 5.1.3 \quad \theta &= \cos^{-1} (R/Z) \quad \checkmark \\
 &= \cos^{-1} (22/23,8) \quad \checkmark \\
 &= 22,43^\circ \quad \checkmark
 \end{aligned} \tag{3}$$

5.2

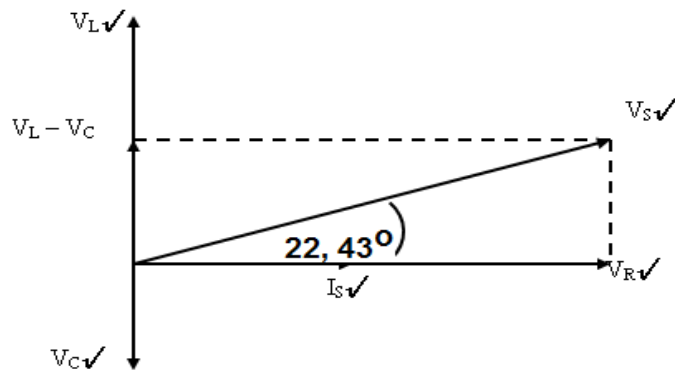

(5)


5.3 Impedance of the circuit is the total opposition a circuit offers to the flow of current. It depends entirely to the frequency of the supply when connected to the alternating voltage supply. $\checkmark\checkmark$

(2)

[20]**QUESTION 6: LOGIC**

$$6.1 \quad ((\overline{A + B}) \cdot C) + (A \cdot (\overline{B + C})) \quad \checkmark\checkmark\checkmark \tag{3}$$

6.2

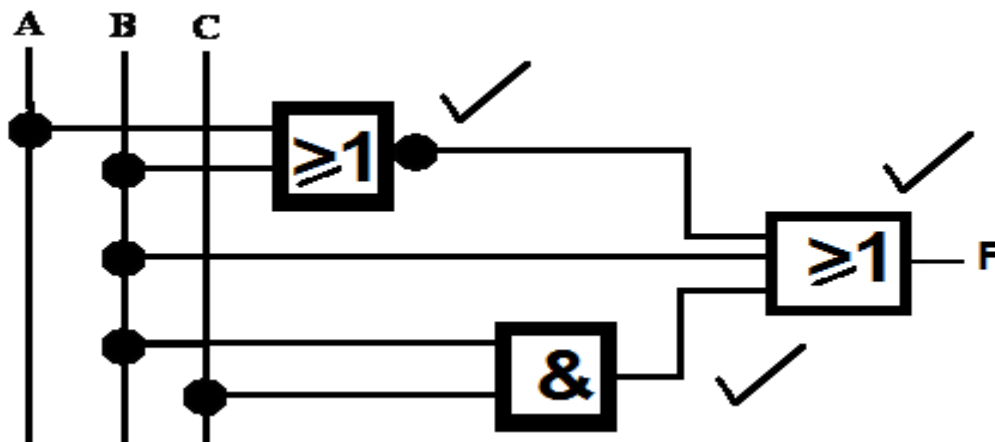

(3)

6.3

$$\begin{aligned}
 F &= A + B + B.C \\
 &= A + B \sqrt{. BC} \\
 &= (A + B)(\overline{B} + \overline{C}) \sqrt{
 \end{aligned}
 \tag{3}$$


6.4

$$6.4.1 \quad Q = \overline{X}YZ + X\overline{Y}Z + XY\overline{Z} + XYZ \tag{3}$$

6.4.2


$$\begin{aligned}
 Q &= \overline{X}YZ + X\overline{Y}Z + XY\overline{Z} + XYZ \\
 &= YZ(\overline{X} + X) + X\overline{Y}Z + XY\overline{Z} \sqrt{ \\
 &= YZ(1) + X\overline{Y}Z + XY\overline{Z} \\
 &= YZ + X\overline{Y}Z + XY\overline{Z} \\
 &= Z(Y + X\overline{Y}) + XY\overline{Z} \sqrt{ \\
 &= Z(Y + X) + XY\overline{Z} \\
 &= YZ + XZ + XY\overline{Z} \\
 &= YZ + X(Z + Y\overline{Z}) \sqrt{ \\
 &= YZ + X(Z + Y) \\
 &= YZ + XZ + XY \sqrt{
 \end{aligned}
 \tag{4}$$

6.4.3

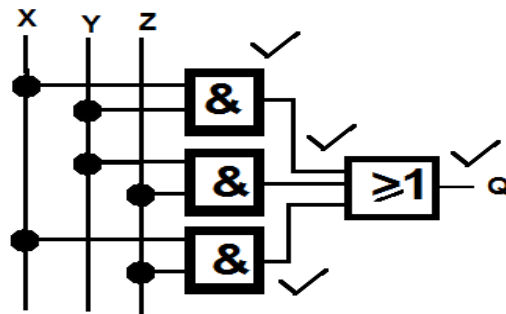(4)
[20]

QUESTION 7: COMMUNICATIONS

7.1

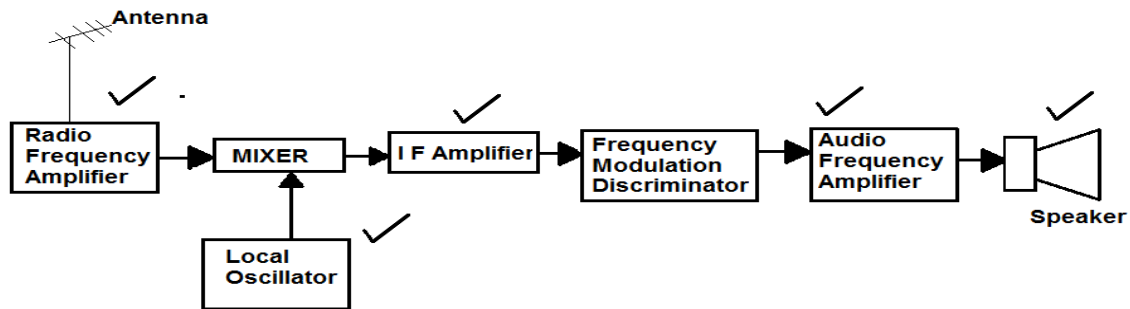

(5)

7.2

- Forestry agencies and utility services. ✓
- Police services ✓
- Ambulance services. ✓

(3)

7.3

Antenna, as a transmitter, it will produce a large radio frequency current that may be applied to the terminals of the same antenna in order to convert it into an electromagnetic wave radiated into free space. ✓✓

(2)

7.4

7.4.1 AM Transmitter ✓

(1)

7.4.2 1 – Audio amplifier ✓

2 – Radio frequency power amplifier ✓

3 – Antenna ✓

(3)

7.5

The higher the frequency, the shorter the wavelength. ✓✓

(2)

7.6

- Large coverage area. ✓
- Reduced interference from other signal. ✓
- Reduced power use. ✓
- Increase capacity. ✓

(Any 2)

(2)

7.7

FM transmitter uses FM Modulator. ✓

AM transmitter uses AM Modulator. ✓

(2)

[20]**TOTAL: 200**