



basic education

Department:
Basic Education
REPUBLIC OF SOUTH AFRICA

ELECTRICAL TECHNOLOGY (ELECTRONICS)

GUIDELINES FOR PRACTICAL ASSESSMENT TASKS (PAT)

GRADE 12

2024

These guidelines consist of 52 pages.

TABLE OF CONTENTS

	PAGE
1. INTRODUCTION	3
2. TEACHER GUIDELINES	5
2.1 How to administer PATs	5
2.2 How to mark/assess PATs	5
2.3 PAT Programme of Assessment (PAT PoA)	6
2.4 Moderation of PATs	7
2.5 Absence/Non-submission of tasks	7
2.6 Simulations	8
2.7 Projects	8
2.8 Working mark sheet	9
3. LEARNER GUIDELINES	10
3.1 PAT 2024 cover page	10
3.2 Instructions to the learner	11
3.3 Declaration of Authenticity (COMPULSORY)	11
4. SIMULATIONS	12
4.1 Simulation 1: RLC parallel circuit	12
4.2 Simulation 2: Inverting op amp	16
4.3 Simulation 3: Switching circuits using a 741 op amp	21
4.4 Simulation 4: Common Emitter Amplifier	29
5. SECTION B: DESIGN AND MAKE	34
5.1 Design and Make: Part 1	35
5.2 Assessment of the Design and Make Phase: Part 1	37
5.3 Design and Make: Part 2	39
5.4 Assessment of the Design and Make Phase: Part 2	40
6. PROJECTS	41
6.1 Practical Project 6.1: Sound-to-light Controller	41
6.2 Practical Project 6.2: Automatic Battery Charger with Battery-voltage Bar-graph Display	44
6.3 Practical Project 6.3: Sine-wave Inverter Circuit Diagram	47
6.4 Practical Project 6.4: Square-wave Inverter 100 W 12 VDC TO 230 VAC BY IC 4047 – IRF540	52
7. CONCLUSION	52

1. INTRODUCTION

The 18 Curriculum and Assessment Policy Statements subjects which contain a practical component all include a practical assessment task (PAT). These subjects are:

- **AGRICULTURE:** Agricultural Management Practices, Agricultural Technology
- **ARTS:** Dance Studies, Design, Dramatic Arts, Music, Visual Arts
- **SCIENCES:** Computer Applications Technology, Information Technology, Technical Sciences; Technical Mathematics
- **SERVICES:** Consumer Studies, Hospitality Studies, Tourism
- **TECHNOLOGY:** Civil Technology, Electrical Technology, Mechanical Technology and Engineering Graphics and Design

A practical assessment task (PAT) mark is a compulsory component of the final promotion mark for all candidates offering subjects that have a practical component and counts 25% (100 marks) of the end-of-the-year examination mark. The PAT is implemented across the first three terms of the school year. This is broken down into different phases or a series of smaller activities that make up the PAT. The PAT allows for learners to be assessed on a regular basis during the school year and it also allows for the assessment of skills that cannot be assessed in a written format, e.g. test or examination. It is therefore important that schools ensure that all learners complete the practical assessment tasks within the stipulated period to ensure that learners are resulted at the end of the school year. The planning and execution of the PAT differs from subject to subject.

Practical assessment tasks are designed to develop and demonstrate a learner's ability to integrate a variety of skills in order to solve a problem. The PAT also makes use of a technological process to inform the learner what steps needs to be followed to derive a solution for the problem.

The PAT consists of four simulations and a practical project. The teacher may choose any ONE of the practical projects and any TWO simulations available for ELECTRONICS. For the first simulation to be completed in term 1, the teacher must choose between Simulation 1 and Simulation 2. For the second Simulation to be completed in term 2, the teacher must choose between Simulation 3 and Simulation 4.

The teacher must apply assessment on an ongoing basis at the same time that the learner is developing the required skills. TWO simulations should be completed by the learners, in addition to the manufacturing of a practical project.

The PAT incorporates all the skills the learner has developed throughout the year. The PAT ensures that all the different skills will be acquired by learners on completion of practical work, as well as the correct use of tools and instruments.

Requirements for presentation

A learner must present the following:

- PAT file with all the evidence of simulations, design and prototyping. A copy of the PAT 2024 cover page. The relevant simulations and assessment sheets should be copied and handed to each learner to include in the file.
- Practical project with:
 - Enclosure:
 - The file must include a design.
 - The enclosure and the design must match.
 - No cardboard boxes are allowed.
 - Plastic wooden and metal enclosures are acceptable.
 - Enclosures that are manufactured and/or assembled by the learners are preferred.
 - The enclosure should be accessible for scrutiny inside.
 - Lids that are secured are preferred.
 - Circuit board:
 - The file should include the PCB design.
 - The PCB must be mounted inside the enclosure in such a manner that it can be removed for scrutiny. Alternatively, inspection can be made from the bottom in cases where translucent (see-through) enclosures are used.
 - Switches, potentiometers, connectors and other items must be mounted.
 - Wiring must be neat and bound/wrapped.
 - Wiring must be long enough to allow for the PCB to be removed and inspected with ease.
 - Logo and name:
 - The file should contain the logo and name design and specification plate.
 - Logo, specification plate and name must be prominent on the enclosure.
 - The logo/specification plate must be affixed in a permanent manner – painted, glued or stuck on with vinyl.

The PAT will have a financial impact on the school's budget and school management teams are required to make provision to accommodate this particular expense.

PAT components and other items must be acquired timeously, for use by the learners, before the end of the first term at the start of the academic year.

It is the responsibility of the HOD to ensure that the teacher is progressing with the PAT from the start of the school year.

Provincial departments are responsible for setting up moderation timetables and consequently PATs should be completed in time for moderation.

2. TEACHER GUIDELINES

2.1 How to administer PATs

Teachers must ensure that learners complete the simulations required for each term. The project should be started in January in order to ensure its completion by August. In instances where formal assessments take place, the teacher has to assume the responsibility thereof.

The PAT should be completed during the FIRST THREE TERMS and must be ready at the start of PAT moderation. Teachers must make copies of the relevant simulations and hand them to learners at the beginning of each term.

The PAT must NOT be allowed to leave the workshop and must be kept in a safe place at all times when learners are not working on them.

The weightings of the PAT must be adhered to and teachers are not allowed to change weightings for the different sections.

2.2 How to mark/assess the PATs

The PAT for Grade 12 will be set and assessed internally, but moderated externally. All formal assessment will be done by the teacher.

The teacher is required to produce a working model and model answer file that sets the baseline for assessment at a Highly Competent Level for every project choice exercised by the learners. This file must include all the simulations with answers the teacher has done him/herself. The teacher will use the model answers and project to assess the simulations and projects of the learners.

Once a facet sheet has been completed by the teacher, assessment will be deemed to be complete. No re-assessment will be done once the facet sheets have been completed and captured by the teacher. Learners must ensure that the work is done to the required standard before the teacher finally assesses the PAT during each stage of completion.

2.3 PAT Programme of Assessment (PAT PoA)

The programme of assessment (PoA) of the PAT is as follows:

TIME FRAME	ACTIVITY	RESPONSIBILITY
	Preparation for PAT 2024	Teacher – Builds the models and works out the model answers for the simulations. Identifies shortages in tools, equipment and consumable items for simulations that must be procured. SMT – Receives procurement requests from teachers and processes payments for the acquisition of required items
January–March 2024	Simulation 1	Teacher – Copies and hands out simulations Learners – Complete simulations Teacher – Assesses simulations HOD – Checks if tasks have been completed and marked by the teacher before the holidays
January 2024	PAT project – procurement	Teacher – Obtains quotations for PAT projects Principal – Approves PAT procurement for PAT projects Teacher – Ensures that PAT projects are ordered and delivered HOD – Checks in on teacher to see if the process is adhered to
February 2024	PAT project – learners commence with project	Teacher – Ensures that there is secure storage for PAT projects Teacher – Hands out and takes in PAT projects Teacher – Includes practical sessions for learners to complete the PAT project every week Learners – Commence with completion of the PAT project HOD – Checks in on teacher to ensure that practical workshop sessions take place on a weekly basis
April–June 2024	Simulation 2	Teacher – Copies and hands out simulations Learners – Complete simulations Teacher – Assesses simulations HOD – Checks if tasks have been completed and marked by the teacher before the holidays
April–June 2024	Moderation of Simulation 1	District subject facilitator/subject specialist will visit the school and moderate Simulation 1 10% of learners' work is moderated
April–June 2024	PAT project – learners continue with project	Teacher – Ensures that there is secure storage for PAT projects Teacher – Hands out and takes in PAT projects Teacher – Includes practical sessions every week for learners to complete the PAT project Learners – Continue with completion of the PAT project HOD – Checks in on teacher to ensure that practical workshop sessions take place on a weekly basis
July holidays 2024	PAT intervention	Learners that are behind on the PAT are required to complete the project during these holidays.
July–August 2024	Moderation of Simulation 2	District subject facilitator/subject specialist will visit the school and moderate Simulation 2 – different learners from the previous term 10% of learners' work is moderated
July–August 2024	PAT project – completion	Teacher – Ensures that there is secure storage for PAT projects Teacher – Hands out and takes in PAT projects Teacher – Completes the PAT project with learners and compiles the PAT file Learners – Complete the PAT project and file HOD – Checks to see that 100% of the PAT files and projects are completed and assessed
September–October 2024	PAT moderation	PAT projects are moderated by subject facilitators/subject specialists from the province and learners are available to demonstrate skills 10% of learners are moderated randomly

2.4 Moderation of PATs

Provincial moderation of each term's simulations will start as early as the following term. Simulation 1 should be moderated as soon as the second term starts. Similarly, Simulation 2 will be moderated in July. The project will, however, only be moderated on completion.

During moderation of the PAT, the learner's file and project must be presented to the moderator.

The moderation process is as follows:

- During moderation, learners are randomly selected to demonstrate the different simulations. All four simulations will be moderated.
- The teacher is required to build an exemplar model of each project type chosen for the school.
- This model must be on display during moderation.
- The teacher's model forms the standard of the moderation at Level 4 (Highly Competent).
- Level 5 assessments must exceed the model of the teacher in skill and finishing.
- Learners who are moderated will have access to their files during moderation and may refer to the simulations they completed earlier in the year.
- Learners may NOT ask assistance from other learners during moderation.
- All projects and files must be on display for the moderator.
- If a learner is unable to repeat the simulation or cannot produce a working circuit during moderation, marks will be deducted and circuits assessed as not being operational.
- The moderator will randomly select no fewer than two projects (not simulations) and the learners involved will have to explain how the project was manufactured.
- Where required, the moderator should be able to call on the learner to explain the function and principles of operation, and request the learner to exhibit the skills acquired through the simulations for moderation purposes.
- On completion the moderator will, if needed, adjust the marks of the group upwards or downwards, depending on the outcome of moderation.
- Normal examination protocols for appeals will be adhered to, if a dispute arises from adjustments made.

2.5 Absence/Non-submission of tasks

The absence of a PAT mark in Electrical Technology without a valid reason: The learner will be given three weeks before the commencement of the final end-of-year examination to submit the outstanding task. Should the learner fail to fulfil the outstanding PAT requirement, such a learner will be awarded a zero (0) for that PAT component.

2.6 Simulations

Simulations are circuits, experiments and tests/tasks which the learner will have to build, test and measure and practically do as part of the development of practical skills. These skills have to be illustrated to the external moderator that visits the school at intervals during the school year.

Teachers who make use of simulation programs on a computer may use them for the learners to practise on. However, it is required that the circuit be built using real components and that measurements be made with actual instruments for the purposes of assessment and moderation.

The correct procedure for completing simulations is outlined below for teachers and school management teams who are responsible for the implementation of the PAT in Electrical Technology.

- STEP 1: The teacher will choose simulations from simulations that are provided.
- STEP 2: Compile a list of the components needed for every simulation. Add extra components which might be needed as these items are very small and get lost/damaged very easily when learners work with them.
- STEP 3: Contact three different electronics component suppliers for comparative quotations.
- STEP 4: Submit the quotations to the SMT for approval and procurement of the items.
- STEP 5: Place the components in storage. Collate items for each simulation, thus making it easier to distribute and use during practical sessions. Ensure that different values of components do not mix, as this would lead to components being used incorrectly and this could damage the component and in extreme cases, the equipment used.
- STEP 6: Copy the relevant simulations and hand them out to learners at the start of the term.

Teachers are allowed to adjust circuits and component values to suit their environment/resource availability.

Teachers are required to develop a set of model answers in the teacher's file. Moderators will use the teacher's model answers and artefacts when moderating.

2.7 Projects

The projects are construction projects teachers can choose for their learners. These projects are based on proven circuits provided by schools and subject advisors. The projects are based on working prototypes and require careful construction in order for it to operate correctly.

Projects vary in cost and teachers must ensure that the projects chosen fall within the scope of the school's budget.

Once the teacher has decided on a circuit, he/she must construct the prototype. Thereafter, copies of the provided circuit can be made and distributed to learners. They **MUST** redraw these circuits in their files correctly.

The description of the operation of the circuits is **NOT** complete. Learners are required to interrogate the function of the components in the provided circuit. Learners should elaborate on the purpose of components in the circuit. It is recommended that learners investigate similar circuits available on the internet and in the school library or workshop reference books.

2.8 Working mark sheet

(A working Excel file is provided with this PAT.)

PAT mark sheet		Term 1	Term 2	Project		Total = Term 1 + Term 2 + Project	Mark out of 100	Moderated Mark
No.	Name of Learner	Simulation 1	Simulation 2	Design and Make Part 1	Design and Make Part 2			
		50	50	120	30	250		
1.								
2.								
3.								
4.								
5.								
6.								
7.								
8.								
9.								
10.								
11.								
12.								
13.								
14.								
15.								
	Total							
	Average							

Teacher Name: _____

Principal Name: _____

Moderator Name: _____

Signature: _____

Signature: _____

Signature: _____

Date: _____

Date: _____

Date: _____

3. LEARNER GUIDELINES**3.1 PAT 2024 COVER PAGE**

(Place this page at the front of the PAT.)

Department of Basic Education Grade 12 CAPS for Technical High Schools Practical Assessment Task – Electrical Technology																												
Time allowed: Terms 1–3 (2024)																												
Learner Name:		<hr/>																										
Class:		<hr/>																										
School:		<hr/>																										
Specialisation: ELECTRONICS Complete Simulation 1 or 2 in the first term and Simulation 3 or 4 in the second term. Project (Write the name of the project): <hr/>																												
Evidence of moderation: NOTE: When the learner evidence selected has been moderated at school level, the table will contain evidence of moderation. Provincial moderators will sign the provincial moderation and only sign if re-moderation is needed.																												
<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 35%;">Moderation</th> <th style="width: 20%;">Signature</th> <th style="width: 15%;">Date</th> <th style="width: 20%;">Signature</th> <th style="width: 10%;">Date</th> </tr> </thead> <tbody> <tr> <td>School-based</td> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <td>District moderation</td> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <td>Provincial moderation</td> <td></td> <td></td> <td>Re-moderation</td> <td></td> </tr> </tbody> </table>					Moderation	Signature	Date	Signature	Date	School-based					District moderation					Provincial moderation			Re-moderation					
Moderation	Signature	Date	Signature	Date																								
School-based																												
District moderation																												
Provincial moderation			Re-moderation																									
Mark allocation <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 40%;">PAT Component</th> <th style="width: 20%;">Maximum Mark</th> <th style="width: 20%;">Learner Mark</th> <th style="width: 20%;">Moderated Mark</th> </tr> </thead> <tbody> <tr> <td>Simulation 1</td> <td style="text-align: center;">50</td> <td></td> <td></td> </tr> <tr> <td>Simulation 2</td> <td style="text-align: center;">50</td> <td></td> <td></td> </tr> <tr> <td>Design and Make Project – Circuit</td> <td style="text-align: center;">120</td> <td></td> <td></td> </tr> <tr> <td>Design and Make Project – Enclosure</td> <td style="text-align: center;">30</td> <td></td> <td></td> </tr> <tr> <td>Total</td> <td style="text-align: center;">250</td> <td></td> <td></td> </tr> </tbody> </table>					PAT Component	Maximum Mark	Learner Mark	Moderated Mark	Simulation 1	50			Simulation 2	50			Design and Make Project – Circuit	120			Design and Make Project – Enclosure	30			Total	250		
PAT Component	Maximum Mark	Learner Mark	Moderated Mark																									
Simulation 1	50																											
Simulation 2	50																											
Design and Make Project – Circuit	120																											
Design and Make Project – Enclosure	30																											
Total	250																											

3.2 Instructions to the learner

- The practical assessment task counts 25% of your final promotion mark.
- All work produced by you must be your own effort. Group work and co-operative work are NOT allowed.
- The practical assessment task must be completed over three terms.
- The PAT file must contain TWO simulations and a practical project.
- Calculations should be clear and include units. Calculations should be rounded off to TWO decimals. SI units should be used.
- Circuit diagrams can be hand-drawn or drawn on CAD. NO photocopies or scanned files are allowed.
- Photos are allowed and may be in colour or greyscale. Scanned photos and photocopies are allowed.
- This document must be placed inside your PAT file together with the other evidence.
- Learners with identical photos will be penalised and receive zero for that section.

3.3 Declaration of Authenticity (COMPULSORY)

Declaration:

I _____ (name) herewith declare that the work represented in this evidence is entirely my own effort. I understand that if proven otherwise, my final results may be withheld.

Signature of learner

Date

4. SIMULATIONS**4.1 Simulation 1: RLC parallel circuit**

Name of learner: _____	Mark	<div style="border: 1px solid black; padding: 5px; text-align: center;">50</div>
Class: _____ Date Completed: _____		
Date Assessed: _____	Assessor Signature: _____	
Date Moderated: _____	Moderator Signature: _____	

4.1.1 Purpose:

- To build an RLC parallel circuit using discrete components and to compare the measured and calculated values of the RLC parallel circuit
- To observe the effect of changing the frequency in the circuit

4.1.2 Required resources:

COMPONENTS	TOOLS AND EQUIPMENT
$R_1 = 22\ \Omega$ resistor $C_1 = 10\ \mu\text{F}$ capacitor 220- 6- 0- 6 V transformer OR $L_1 = 30\text{-}45\ \text{mH}$ Inductor	Multimeter Function generator Leads Breadboard Side cutters Pair of pliers Oscilloscope

4.1.3 Procedure:

Build the RLC parallel circuit in FIGURE 4.1.4 on the breadboard using the components provided.

Connect the circuit to a function generator.

Set the input signal voltage of the function generator to 2,5 V with a frequency of 50 Hz.

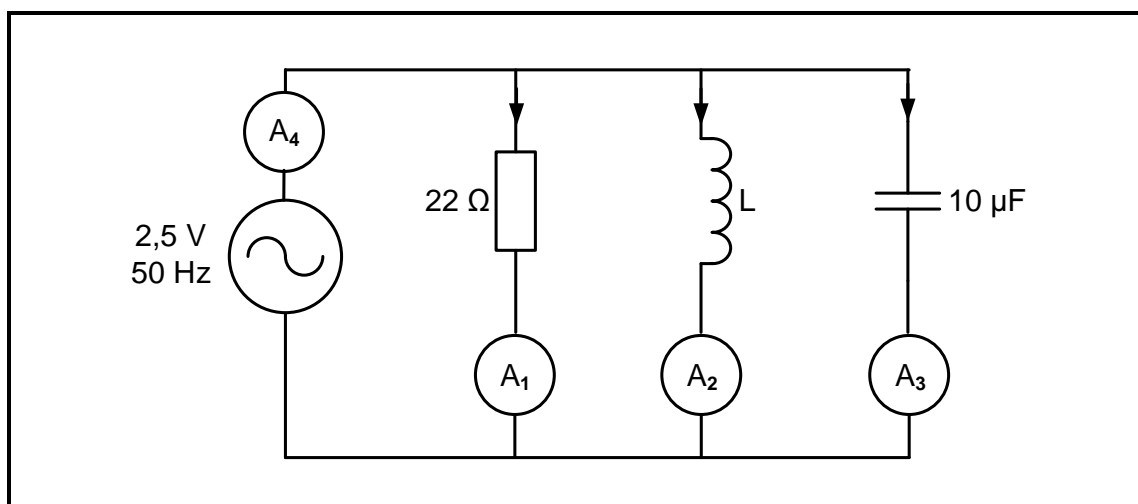
4.1.4 Circuit diagram:

FIGURE 4.1.4: PARALLEL RLC CIRCUIT DIAGRAM

4.1.5 Measure the current through the:

- (a) Resistor_____ (Ammeter 1) (1)
- (b) Inductor_____ (Ammeter 2) (1)
- (c) Capacitor _____ (Ammeter 3) (1)
- (d) Circuit _____ (Ammeter 4) (1)

4.1.6 Calculate the total current through the circuit using the measured values.

(3)

4.1.7 Calculate the following, using the appropriate formulae, when the frequency is 50 Hz.

- (a) Capacitive current (I_C)

(3)

- (b) Inductive current (I_L)

(3)

- (c) Current through the resistor (I_R)

(3)

- (d) Power factor

(3)

- 4.1.8 Draw the phasor diagram of the circuit in FIGURE 4.1.4. Use the space provided below. (5)

- 4.1.9 Increase the frequency of the signal generator and measure the values of I_R , I_L and I_C as shown in the table below.

F(Hz)	I_R	I_L	I_C
700			
900			
1 100			
1 300			

(12)

- 4.1.10 Write your observation when the frequency is increased. (2)

- 4.1.11 Is the circuit capacitive or inductive? _____
Motive your answer.

_____ (2)

Theory Simulation 1: [40]

**NOTE: Learner competency in this context will mean the following:
(This is done for easy assessment when using a rubric.)**

Not yet competent	Have not met the requirements and will be given another opportunity for reassessment. <ul style="list-style-type: none"> Be precise about what they did wrong, or the areas they need to improve in. Clearly explain the level of skill they need to achieve to be assessed as 'competent'. Indicate whether part or all of the assessment events will need to be repeated.
Competent	Have the necessary ability, knowledge or skill to complete the task successfully. <ul style="list-style-type: none"> Acceptable and satisfactory, though not outstanding.
Outstanding	Went beyond expectation (neatness, proficiency – high degree of skills, expertise)

FACET SHEET FOR SIMULATION 1

Task description	Mark allocation (tick the appropriate level next to the task indicated)				Allocation of marks
	Competent after reassessment of certain/all parts of the task	Not yet competent after reassessment of certain/all parts of the task	Competent	Outstanding (Highly competent)	
Building the RLC Circuit	The learner was given opportunities to rebuild the circuit after the teacher intervened in identifying and rectifying more mistakes. (1)	The learner was given an opportunity to rebuild part of the circuit after the teacher intervened in identifying and rectifying a few mistakes. (2–3)	The learner correctly built the circuit without the guidance of the teacher. (4–5)	The learner correctly built the circuit without the guidance of the teacher and went beyond expectations and with high proficiency. (6)	<u>6</u>
Safety aspects	The learner was timeously reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (0)	The learner was sometimes reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (1)	The learner applied safety rules, regulation and correct procedure when using tools and instruments to wire the circuits without being reminded by the teacher. (2)		<u>2</u>
Attitude/ Behaviour/ Conduct	The learner was reluctant to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice even after being cautioned/reprimanded. (0)	The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (1)	The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (2)		<u>2</u>
Rubric Theory Total Simulation 1					/10 + /40 = /50

4.2 Simulation 2: Inverting op amp

Name of learner: _____		Mark <div style="border: 1px solid black; width: 100px; height: 30px; margin: 0 auto; display: flex; align-items: center; justify-content: center;">50</div>
Class: _____	Date completed: _____	
Date Assessed: _____		Assessor Signature: _____
Date Moderated: _____		Moderator Signature: _____

4.2.1 Purpose:


- To build an inverting operational amplifier circuit using a 741 op-amp integrated circuit (IC)
- To display the output waveforms on an oscilloscope
- To observe how a change in the value of R_F affects the gain and output voltage of the circuit by either increasing or decreasing the value of R_F

4.2.2 Required resources:


TOOLS/INSTRUMENTS	MATERIALS
Analogue/Digital trainer	1 x LM 741 op-amp
Analogue/Digital oscilloscope (dual trace)	1 x 10 k Ω for R_{IN}
Function generator	1 x 22 k Ω for R_F
Multimeter	1 x 47 k Ω
Variable DC power supply (split supply)	1 x 100 k Ω
Side cutters	Connecting wires
Wire strippers	
Long-nose pliers	
Breadboard	

4.2.3 Procedure:

Construct the circuit in FIGURE 4.2.3 on a breadboard.

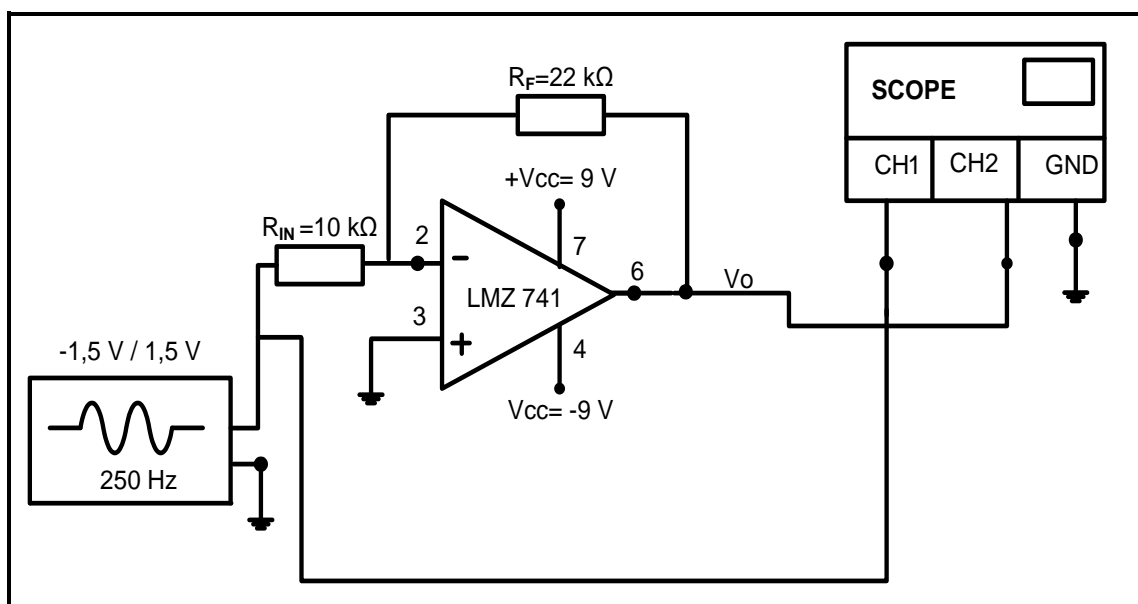**FIGURE 4.2.3: INVERTING OP AMP**

- 4.2.4 Set up the oscilloscope to display at least TWO complete cycles for CH1 and CH2 with the voltage settings to display 2/3rd of the screen.
- 4.2.5 Draw and label both the input (from CH1) and output (from CH2) waveforms for TWO complete cycles on the table below.
- 4.2.6 Write down the peak values of the input and output voltage readings from CH1 and CH2 with $R_F = 22 \text{ k}\Omega$.

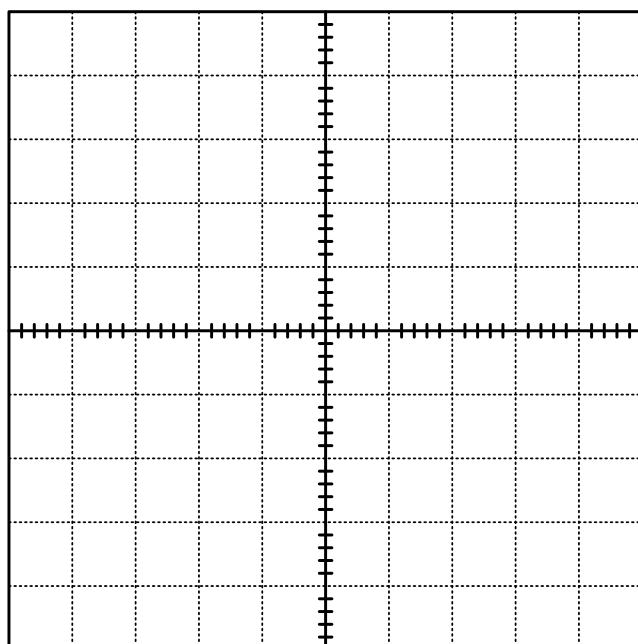**TABLE 4.2.6**

CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

 V_{IN} : _____ V_{OUT} : _____

NOTE: 1 mark for each correct waveform = 2
 1 mark for each oscilloscope setting = 3
 1 mark for each voltage measurement = 2

(7)

- 4.2.7 Explain the relationship between the input and output waveforms with reference to gain and amplitude.

(3)

- 4.2.8 Use the peak values in QUESTION 4.2.4 to calculate the gain below.
(All values measured with the oscilloscope are peak values.)

$A_V =$ _____
 = _____
 = _____ (3)

- 4.2.9 Calculate the voltage gain of the circuit by using the formula below.

$A_V =$ _____
 = _____
 = _____ (3)

- 4.2.10 Measure and record the voltages across V_{OUT} in the table below. Also calculate the voltage gain values in the table below as you change the value of R_F in the circuit.


Use $A_V = - \left(\frac{V_{OUT}}{V_{IN}} \right)$

RESISTOR R_F	V_{IN}	V_{OUT}	VOLTAGE GAIN (A_V)
(a) 10 k Ω	1,5 V	_____	
(c) 47 k Ω	1,5 V	_____	
(d) 100 k Ω	1,5 V	_____	

TABLE 4.2.10

NOTE: 1 mark for each correct voltage value = 3 (3)
 2 marks for each correct gain calculation = 6 (6)

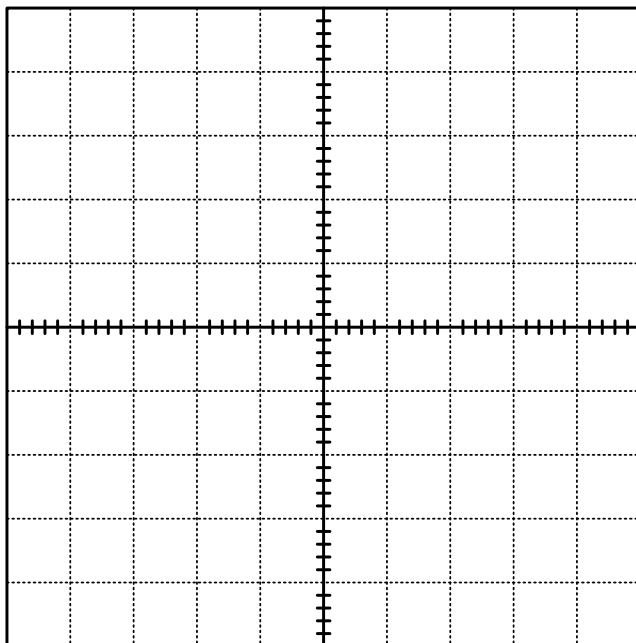- 4.2.11 Draw and label the input and output waveforms for at least two complete cycles in the table below. Indicate the voltage settings for CH 1 and CH 2 with $R_F = 100 \text{ k}\Omega$.



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

 V_{IN} : _____ V_{OUT} : _____**TABLE 4.2.11**

NOTE: 1 marks for each correct waveform = 2
 1 mark for each oscilloscope setting = 3
 1 mark for each voltage measurement = 2

(7)

- 4.2.12 Calculate the gain of the amplifier by using resistance values when $R_F = 22 \text{ k}\Omega$.

$$A_V = \underline{\hspace{2cm}}$$

$$= \underline{\hspace{2cm}}$$

$$= \underline{\hspace{2cm}}$$

(3)

- 4.2.13 Refer to the following:

- TABLES 4.2.6 and 4.2.11, i.e. the waveforms on the oscilloscope
- The calculations in QUESTIONS 4.2.8 and 4.2.9.

Compare the gain in TABLE 4.2.6 to the gain in TABLE 4.2.11 above and write a conclusion on the findings.

(5)
Theory: (40)

FACET SHEET FOR SIMULATION 2

Task description	Mark allocation (tick the appropriate level next to the task indicated)				Allocation of marks
	Not yet competent after reassessment of certain/all parts of the task	Competent after reassessment of certain/all parts of the task	Competent	Outstanding (Highly competent)	
Building the inverting op-amp using LM 741 IC	The learner was given opportunities to rebuild the circuit after the teacher intervened in identifying and rectifying more mistakes. (1)	The learner was given an opportunity to rebuild part of the circuit after the teacher intervened in identifying and rectifying a few mistakes. (2–3)	The learner correctly built the circuit without the guidance of the teacher. (4–5)	The learner correctly built the circuit without the guidance of the teacher and went beyond expectations and with high proficiency. (6)	$\frac{6}{}$
Safety aspects	The learner was timeously reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (0)	The learner was sometimes reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (1)	The learner applied safety rules, regulation and correct procedure when using tools and instruments to wire the circuits without being reminded by the teacher. (2)		$\frac{2}{}$
Attitude/ Behaviour/ Conduct	The learner was reluctant to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice even after being cautioned/reprimanded. (0)	The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (1)	The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (2)		$\frac{2}{}$
Rubric Theory Total Simulation 2					/10 + /40 = /50

4.3 **Simulation 3: Switching circuits using a 741 op amp**

Name of learner: _____		Mark <div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto; text-align: center; line-height: 20px;">50</div>
Class: _____	Date Completed: _____	
Date Assessed: _____		Assessor Signature: _____
Date Moderated: _____		Moderator Signature: _____

4.3.1 **Purpose:**

- To build an electronic piano (astable multivibrator) circuit using a 555 IC on a breadboard as shown in FIGURE 4.3.3
- To display the output waveforms on an oscilloscope
- To calculate the output frequency
- To investigate how a change in R_F and C_1 affects the frequency and tone of the output

4.3.2 **Resources:**

TOOLS/INSTRUMENTS	MATERIALS
Analogue/Digital trainer	1 x 741 IC
Analogue/Digital oscilloscope	1 x 0,68 μ F (25 V capacitor)
Dual rail DC power supply (-5 V - 0 - +5 V)	1 x 150 k Ω resistor
Side cutters	1 x 10 k Ω resistor
Wire stripper	1 x 5,6 k Ω speaker
Long-nose plier	1 x LED
Breadboard	Connecting wires

4.3.3 **Procedure:**

- (a)
- Build the circuit in FIGURE 4.3.3 on the breadboard.
 - Connect channel 1 of the oscilloscope across the capacitor.
 - Connect channel 2 of the oscilloscope across the LED.
 - Switch the circuit ON and observe.
 - Answer the questions that follow.


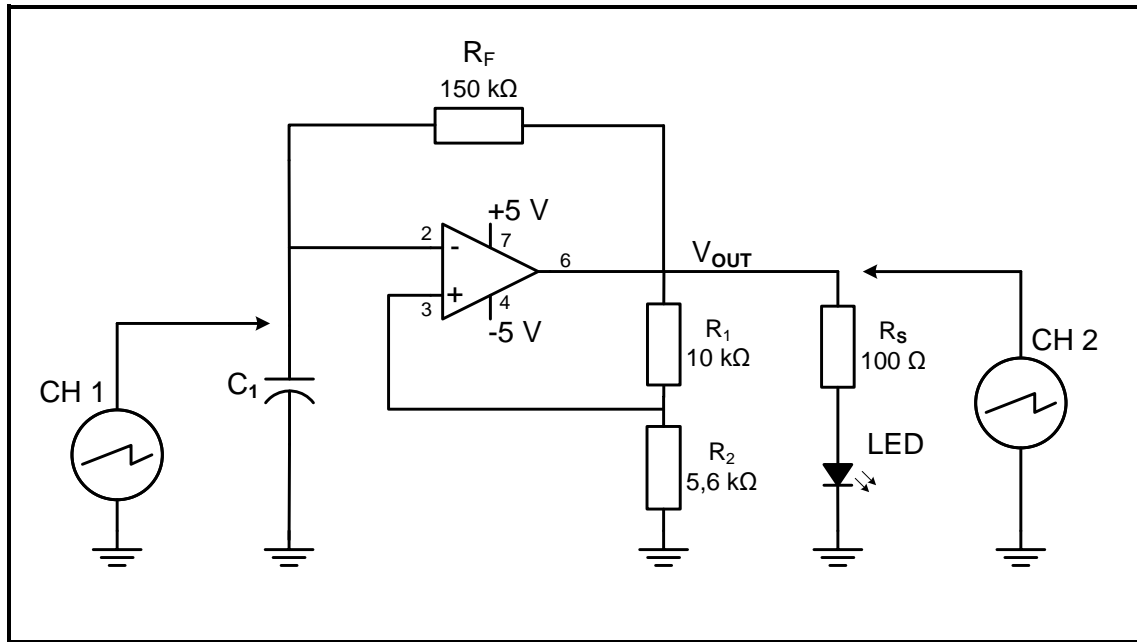


FIGURE 4.3.3: ASTABLE MULTIVIBRATOR CIRCUIT DIAGRAM

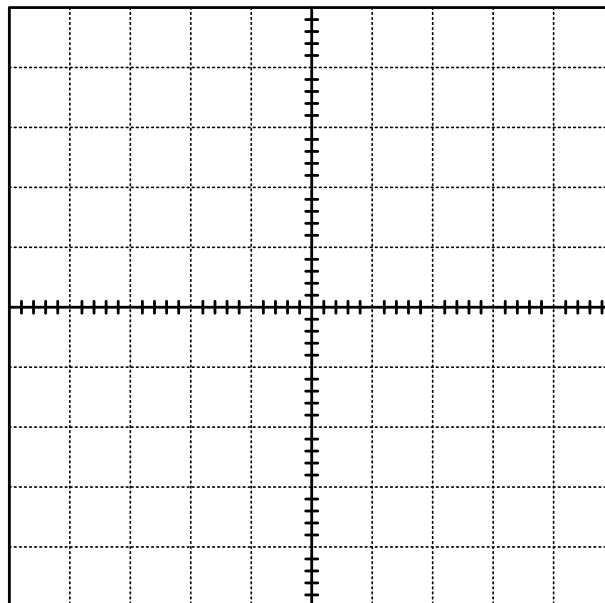- (b) Set the oscilloscope to display at least four complete cycles of the input and output waveforms with the amplitudes not smaller than 6 divisions. Draw the output waveforms on the oscillogram below.



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

NOTE: 1 mark for each correct waveform (i/p and o/p) (2)

1 mark for each correct oscilloscope setting (3)

(5)


- (c) Make use of the oscilloscope settings and determine the frequency of the of the output signal.

Output frequency

(2)

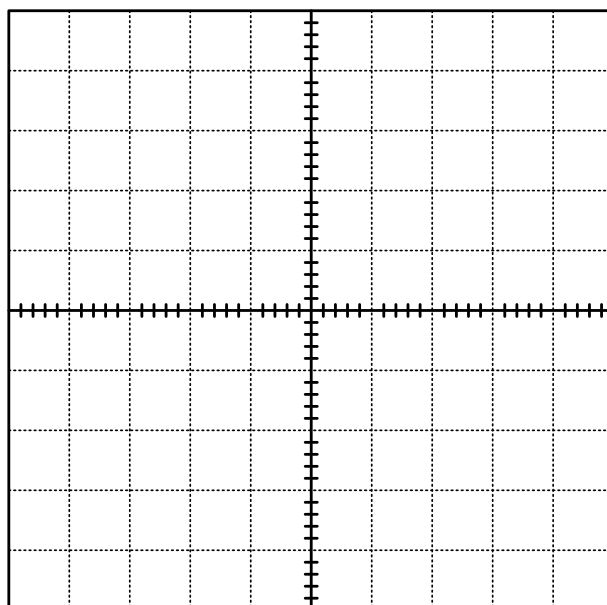- (d) Change the value of C_1 to $1\ \mu\text{F}$ and observe. Draw the output waveforms on the oscillogram below.

NOTE: Keep the oscilloscope setting the same as in (b).



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

NOTE: 1 mark for each correct waveform (i/p and o/p) (2)

(2)

- (e) Make use of the oscilloscope settings and determine the frequency of the output signal.

Output frequency

(2)

- (f) Explain how an increase in the value of C_1 affects the frequency of the circuit.

(2)

- (g) Name TWO components that affect the frequency of the circuit.

(2)

Simulation 3A: (15)

FACET SHEET FOR SIMULATION 3A

Task description	Mark allocation (tick the appropriate level next to the task indicated)				Allocation of marks
	Competent after reassessment of certain/all parts of the task	Not yet competent after reassessment of certain/all parts of the task	Competent	Outstanding (Highly competent)	
Building the astable multivibrator using 741 IC	The learner was given opportunities to rebuild the circuit after the teacher intervened in identifying and rectifying more mistakes. (1)	The learner was given an opportunity to rebuild part of the circuit after the teacher intervened in identifying and rectifying a few mistakes. (2–3)	The learner correctly built the circuit without the guidance of the teacher. (4–5)	The learner correctly built the circuit without the guidance of the teacher and went beyond expectations and with high proficiency. (6)	<u>6</u>
Safety aspects	The learner was timeously reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (0)	The learner was sometimes reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (1)	The learner applied safety rules, regulation and correct procedure when using tools and instruments to wire the circuits without being reminded by the teacher. (2)		<u>2</u>
Attitude/ Behaviour/ Conduct	The learner was reluctant to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice even after being cautioned/ reprimanded. (0)	The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (1)	The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (2)		<u>2</u>
					Rubric Theory /10
					+ /15
					= /25
					Total Simulation 3A

Simulation 3 B: Op-amp integrator using 741 IC**4.3.4 Purpose:**

- To build the integrator circuit in FIGURE 4.3.6 using a 741 op amp and display the input and output waveforms on an oscilloscope
- To investigate the effect of the R_F to R_{IN} ratio on the trigger voltage and output of the circuit

4.3.5 Required resources:

TOOLS/INSTRUMENTS	MATERIALS
Function generator	1 x LM741 op amp
Dual trace oscilloscope	1 x 100 k Ω resistor
+9 V 0 V -9 V DC power supply	1 x 10 k Ω resistor
Side cutters	1 x 0,01 μ F capacitor (103)
Wire stripper	1 x 1 nF capacitor (102)
Calculator	Connecting wires

4.3.6 Procedure:

- Set the dual voltage power supply to +9 V / -9 V.
- Set the function generator to deliver 2 V_{p-p} 1 kHz square wave.
- Build the circuit in FIGURE 4.3.6(a) on your experiment board and connect it to the supply and input.
- Connect channel 1 of the oscilloscope across the input to display at least TWO complete cycles.
- Connect channel 2 of the oscilloscope across the output to display at least TWO complete cycles.
- Ensure that the V/div settings for channel 1 and channel 2 are set so that the waveforms are at least 2/3rd of the screen.
- Set the T/div setting to display at least TWO complete cycles of the input and output.
- Disconnect the function generator and replace capacitor C_1 as indicated.
- After replacing capacitor C_1 , repeat bullets 4 and 5 above.
- Answer the questions and draw the input and output waveforms.

- (a) Build the circuit in FIGURE 4.3.6(a) on the experiment board.


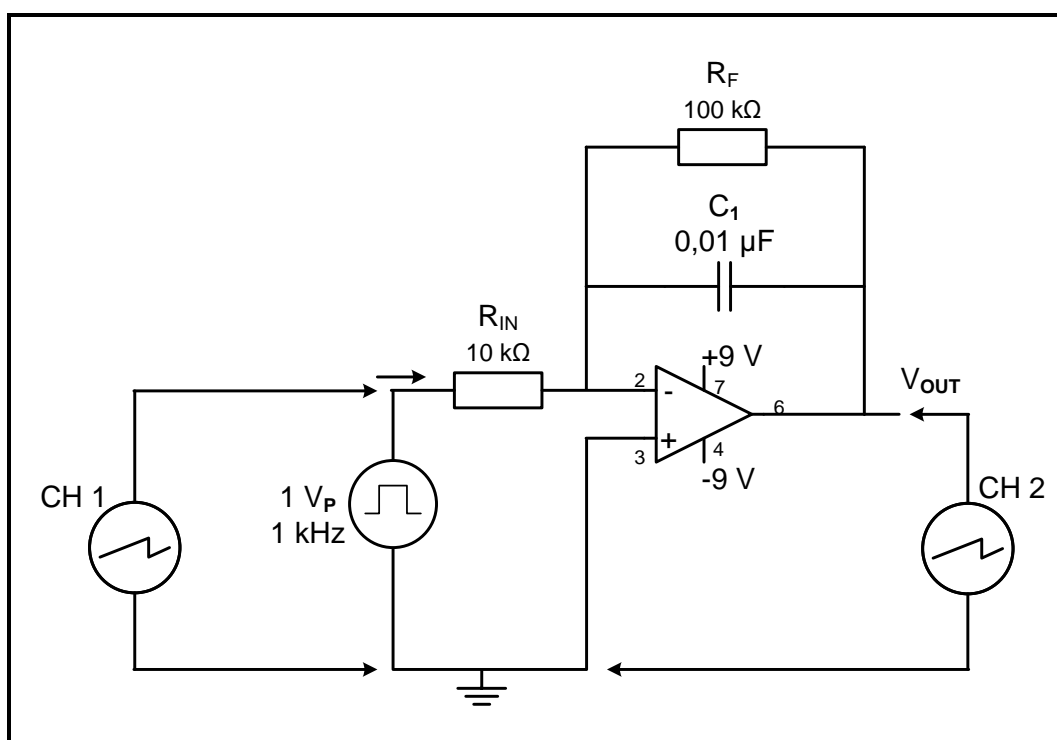


FIGURE 4.3.6(a): 741 OP-AMP INTEGRATOR CIRCUIT

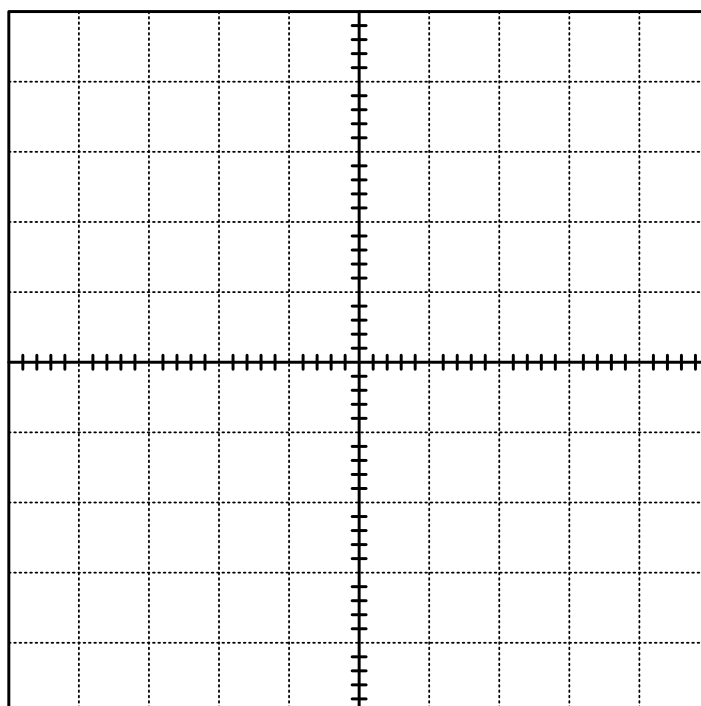- (b) Draw and label the input waveforms from pin 2 and pin 6 on the oscilloscope grid below.

NOTE: Set the oscilloscope to display at least two complete cycles.



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

NOTE: 1 mark for each correct waveform = 2
1 mark for each correct oscilloscope setting = 3


(5)

- (c) Explain the relationship between the input and the output waveforms with reference to the polarity, slope, pulse width and shape.

(3)

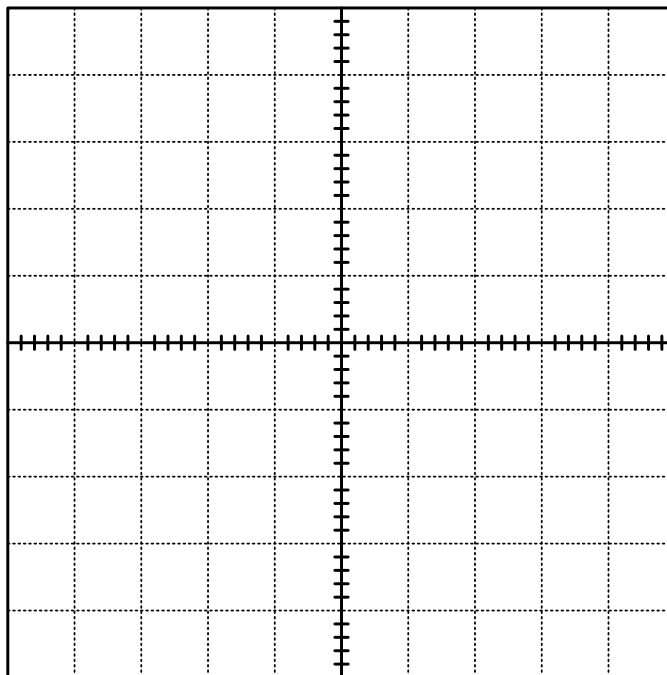- (d) Replace capacitor C_1 with a 1 nF capacitor and observe. Draw the input and output waveforms on the oscilloscope grid below.

NOTE: Keep the oscilloscope setting the same as in QUESTION 4.3.6 (b).



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

NOTE: 1 mark for each correct waveform = 2

Oscilloscope settings remain the same (no marks awarded)

(2)

- (e) Name ONE component, other than C_1 , responsible for the slope of the output signal.

(1)

- (f) Compare the shape of the output waveform on the oscilloscope for QUESTION 4.3.6 (b) to the output waveform for QUESTION 4.3.6 (d) above and write down your findings.

(4)

Theory 3B: (15)

FACET SHEET FOR SIMULATION 3B

Task description	Mark allocation (tick the appropriate level next to the task indicated)				Allocation of marks
	Competent after re-assessment of certain/all parts of the task	Not yet competent after re-assessment of certain/all parts of the task	Competent	Outstanding (Highly competent)	
Building the astable multivibrator using a 741 IC	The learner was given opportunities to re-build the circuit after the teacher intervened in identifying and rectifying more mistakes (1)	The learner was given an opportunity to re-build part of the circuit after the teacher intervened in identifying and rectifying few mistakes (2–3)	The learner correctly build the circuit without the guidance of the teacher (4–5)	The learner correctly build the circuit without the guidance of the teacher and went beyond expectations and with high proficiency (6)	$\overline{6}$
Safety aspects	The learner was timeously reminded to apply safety rules, regulation, and correct procedure when using tools and instruments (0)	The learner was sometimes reminded to apply safety rules, regulation, and correct procedure when using tools and instruments (1)	The learners applied safety rules, regulation, and correct procedure when using tools and instruments to wire the circuits without been reminded by the teacher. (2)		$\overline{2}$
Attitude/ Behaviour/ Conduct	The learner was reluctant at all to work, cooperate, take responsibility of their own conduct, and follow instructional, regulation and workshop practice even after been cautioned/reprimanded (0)	The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct, and follow instructional, regulation and workshop practice (1)	The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct, and follow instructions, regulation and workshop practice. (2)		$\overline{2}$
					Rubric
					Theory
					Total Simulation 3B
					Total Simulation 3A
					TOTAL:
					/10
					+ /15
					= /25
					+ /25
					= /50

4.4 Simulation 4: Common emitter amplifier

Name of learner: _____		Mark <div style="border: 1px solid black; width: 100px; height: 30px; margin: 0 auto; display: flex; align-items: center; justify-content: center;">50</div>
Class: _____	Date completed: _____	
Date Assessed: _____	Assessor Signature: _____	
Date Moderated: _____	Moderator Signature: _____	

Activity 4.4: Push-pull amplifier**4.4.1 Purpose:**

To build a common emitter amplifier circuit using discrete components and display the input and output waveforms on an oscilloscope

4.4.2 Required resources:

TOOLS/INSTRUMENTS	MATERIALS
Analogue /Digital trainer (breadboard)	Transistor BC546/ BC182B/2N3904
Analogue/Digital oscilloscope (dual beam oscilloscope)	$R_1 = 47\text{ k}\Omega$ resistor
Function generator	$R_2 = 10\text{ k}\Omega$ resistor
Breadboard	$R_C = 4\text{K}7\ \Omega$
Multimeter	$R_E = 1\text{ k}\Omega$ resistor
Variable DC power supply	$C_1 = 25\ \mu\text{F}$ (input)
(+10 V DC supply)	$C_2 = 100\ \mu\text{F}$ (output)
Side cutters	$C_E = 25\ \mu\text{F}$
Pair of pliers	
Wire strippers	

4.4.3 **Procedure:**

Build the circuit as shown below on the breadboard or digital trainer and switch it on without connecting the signal generator.

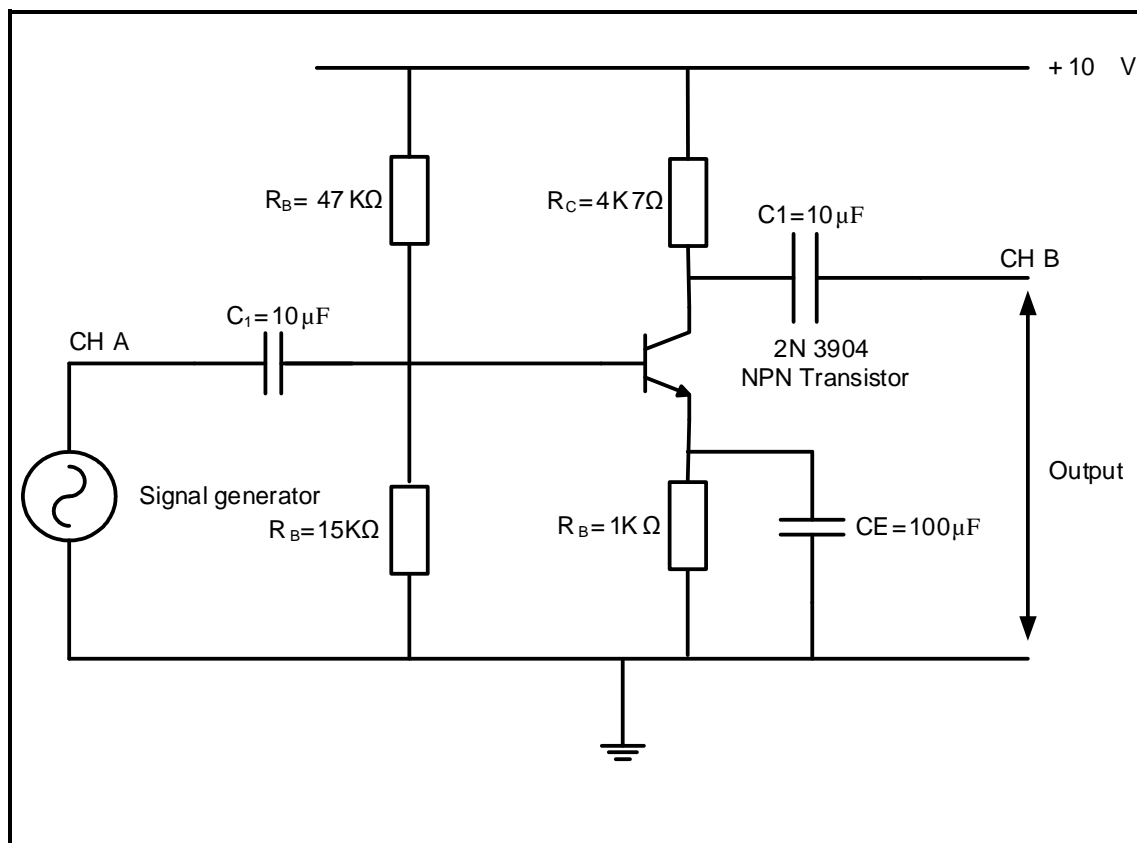


FIGURE 4.4.3: COMMON EMITTER AMPLIFIER

4.4.4 Measure the DC voltages between the following:

(a) Base and the ground: _____ (1)

(b) Emitter and the ground: _____ (1)


4.4.5 Determine the value of the base voltage. _____ (1)

- 4.4.6
- Connect the function generator at 1 kHz and adjust the level of the signal for an undistorted signal at the output channel (input AC, 2 V/division, time base 1 ms/division).
 - Connect channel 2 to the input at the input terminal (input AC, 50 mV/division).

(a) Calculate the voltage gain of the circuit.

(3)

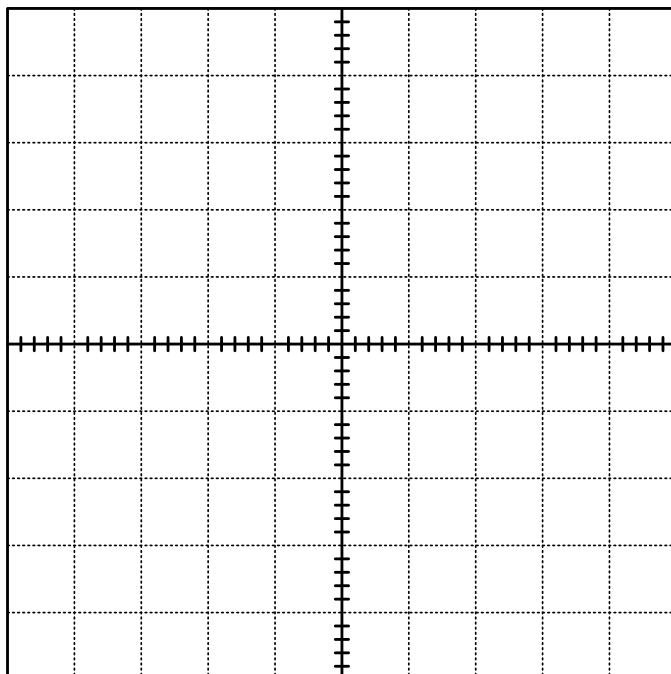- (b) Measure the peak-to-peak amplitude of the input waveform. _____
- (c) Measure the peak-to-peak amplitude of the output waveform. _____
- (d) Draw the two waveforms on the grid below.




CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

(6)

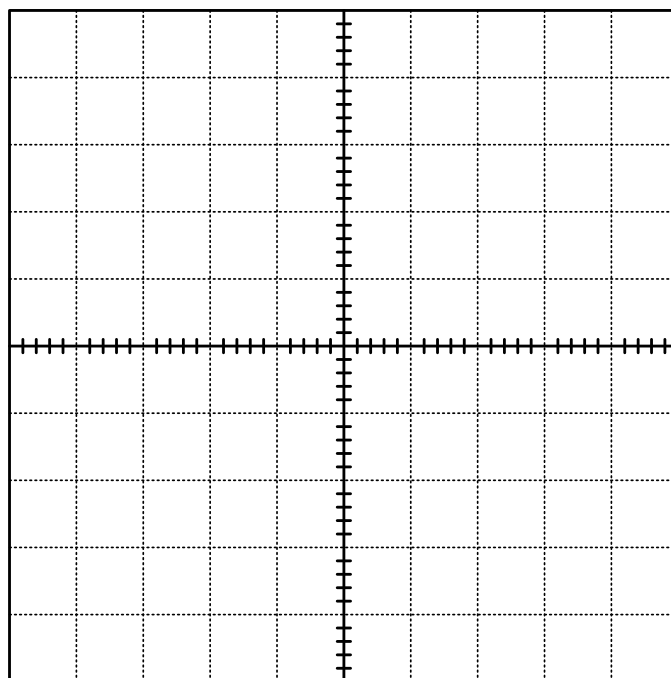- 4.4.7 Slowly increase the amplitudes of the signal generator. Observe the output waveform and draw this waveform on the grid below.



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

(6)


4.4.8 Readjust the amplitude of the signal generator for an undistorted output. Do not change the setting of the signal generator. Remove the capacitor across the emitter and observe the change on the oscilloscope.

(a) Measure the peak-to-peak voltage of the output waveform. _____ (2)

(b) Calculate the voltage gain of the circuit.

(3)

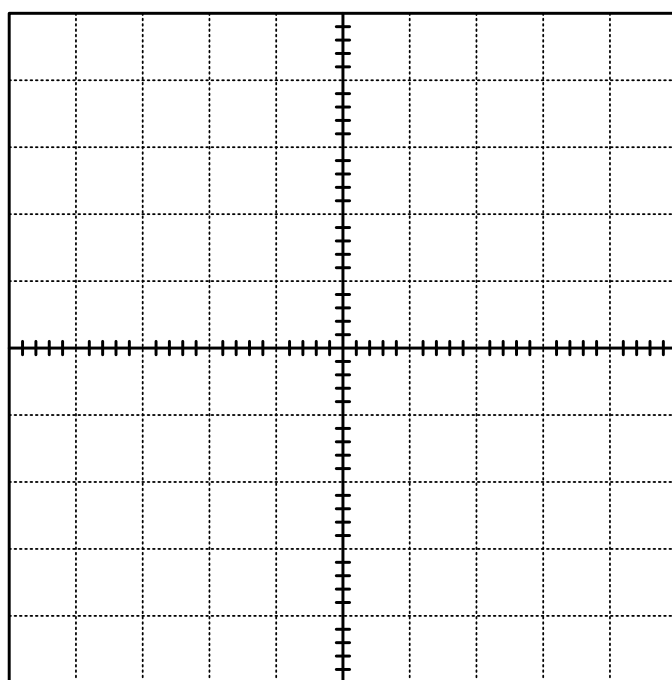(c) Draw the output waveform on the grid below.



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

(6)

4.4.9 Explain in your own words why the circuit is called a common emitter amplifier.


(2)

Theory: (35)

FACET SHEET FOR SIMULATION 4

Task description	Mark allocation (tick the appropriate level next to the task indicated)				Allocation of marks
	Competent after reassessment of certain/all parts of the task	Not yet competent after reassessment of certain/all parts of the task	Competent	Outstanding (Highly competent)	
Building the astable push pull amplifier	The learner was given opportunities to rebuild the circuit after the teacher intervened in identifying and rectifying more mistakes. (1)	The learner was given an opportunity to rebuild part of the circuit after the teacher intervened in identifying and rectifying a few mistakes. (2–5)	The learner correctly built the circuit without the guidance of the teacher. (6–8)	The learner correctly built the circuit without the guidance of the teacher and went beyond expectations and with high proficiency. (9)	<u>9</u>
Safety aspects	The learner was timeously reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (0)	The learner was sometimes reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (1)	The learner applied safety rules, regulation and correct procedure when using tools and instruments to wire the circuits without being reminded by the teacher. (2–3)		<u>3</u>
Attitude/ Behaviour/ Conduct	The learner was reluctant to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice even after being cautioned/reprimanded. (0)	The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (1)	The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (2–3)		<u>3</u>
Rubric Theory Total Simulation 4					/15 + /35 = /50

5. SECTION B: DESIGN AND MAKE

Design and Make Project		
Time: January to August 2024		
Learner Name:		
School:		
Class:		
Title/Type of Project: _____		

INSTRUCTIONS

- This section is **COMPULSORY** for all learners.
- The teacher will choose a circuit for the project.
- Any project constructed must include at least (but is not limited to):
 - Seven components
 - A variety of components (both active and passive)
 - PCB making in some form
 - Soldering
 - An enclosure with a switch and protection
- The checklist below must be used to ensure that all the required tasks for the PAT have been completed.

PAT CHECKLIST

The learner **MUST** fill in this checklist **BEFORE** marking of the section takes place.

NO.	DESCRIPTION	TICK (☑)	
		NO	YES
Design and Make: Part 1			
1.	Circuit diagram drawn	<input type="checkbox"/>	<input type="checkbox"/>
2.	Circuit description filled in	<input type="checkbox"/>	<input type="checkbox"/>
3.	Component list completed	<input type="checkbox"/>	<input type="checkbox"/>
4.	Tools list for circuitry populated	<input type="checkbox"/>	<input type="checkbox"/>
5.	Measuring instrument list filled in	<input type="checkbox"/>	<input type="checkbox"/>
Design and Make: Part 2			
1.	Enclosure design completed and included in the file	<input type="checkbox"/>	<input type="checkbox"/>
2.	Unique name written down and on the enclosure	<input type="checkbox"/>	<input type="checkbox"/>
3.	Logo designed and on the enclosure	<input type="checkbox"/>	<input type="checkbox"/>
Miscellaneous			
1.	Enclosure included in the project	<input type="checkbox"/>	<input type="checkbox"/>
2.	Enclosure prepared and drilled according to the design	<input type="checkbox"/>	<input type="checkbox"/>
3.	Enclosure finished off and completed with name and logo	<input type="checkbox"/>	<input type="checkbox"/>
4.	PCB securely mounted in the enclosure using acceptable techniques	<input type="checkbox"/>	<input type="checkbox"/>
5.	Circuit inside the enclosure accessible	<input type="checkbox"/>	<input type="checkbox"/>
6.	Internal wiring neat and ready for inspection	<input type="checkbox"/>	<input type="checkbox"/>
7.	File and project completed and ready for moderation at the workshop/room	<input type="checkbox"/>	<input type="checkbox"/>

5.1 Design and Make: Part 1

5.1.1 Circuit diagram

Draw a circuit diagram of the project chosen and paste it on the next page.

5.1.2 Project: Description of operation

Use the space below to describe how the project operates. Do research and use your own words.

This image shows a full page of blank white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page, providing a template for writing or drawing. There are no margins, text, or other markings present.

5.2 Assessment of the Design and Make Phase: Part 1

NO.	FACET DESCRIPTION	Mark	Achieved mark
Circuit Diagram			
1.	The circuit diagram was drawn using <ul style="list-style-type: none"> EGD equipment (4) CAD/Any electronic design software (6) 	6	
2.	The circuit diagram was drawn using correct symbols.	3	
3.	The circuit diagram has all labels, e.g. R1, C1, Tr1	3	
4.	The circuit diagram has all component values, e.g. 100 Ω , 220 μF	4	
5.	The circuit diagram has a name/title.	2	
6.	The circuit diagram has a frame and title block.	2	
	Circuit Diagram Subtotal:	20	
Component List			
7.	Labels correlate with circuit diagram.	2	
8.	Description and values correlate with circuit diagram.	2	
9.	Quantities are correct.	1	
	Component List Subtotal:	5	
Description of Operation			
10.	Basic function of the circuit is described correctly. The purpose/role/function of each component is described.	11	
11.	All subcircuits in the circuit diagram and component list are included in the description.	4	
12.	Purposes of subcircuits in the circuit diagram are described correctly.	5	
13.	Learner used own interpretation and did not copy from another source verbatim.	3	
14.	Sources are acknowledged.	2	
	Description of Operation Subtotal:	25	
Tools/Instrument List			
15.	The tools/instrument list has been completed.	4	
16.	The tools/instruments listed all have a purpose for being used.	1	
	Tools/Instrument List Subtotal:	5	

NO.	FACET DESCRIPTION	Mark	Achieved mark
Circuit Board Manufacturing			
17.	Transfer of the PCB design onto the blank board is correct. Not over-exposed or under-exposed.	5	
18.	Circuit board is etched neatly according to the PCB design.	10	
19.	The learner's name is etched onto the circuit design.	4	
20.	All burrs are removed.	2	
21.	Axial and radial components are placed neatly and flush with the board.	5	
22.	Component orientation is aligned between similar components (e.g. the gold band of all resistors are placed on the same side).	2	
23.	Soldered components – leads are cut off, flush and neat on the solder side.	5	
24.	More than 60% of the solder joints are shiny (not dry joints).	5	
25.	Wire insulation is stripped to the correct length (no extra copper showing).	3	
26.	Wiring is long enough to allow for dismantling and inspection.	2	
27.	Wiring is wrapped neatly.	2	
28.	A power switch is included and fitted to the enclosure.	2	
29.	A fuse/protection is included and fitted correctly where applicable.	2	
30.	Wiring entering/exiting the enclosure is provided with a grommet/applicable fittings/sockets where applicable.	2	
31.	Batteries/Transformer is mounted using a battery housing/mounting bracket and battery clip (NO double-sided tape).	2	
32.	The project has a pilot light/LED installed in the enclosure showing when the circuit is operational. LED is mounted with a grommet or applicable fitting. (Switch is on – must go out when fuse is blown.)	2	
33.	The project is fully operational and commissioned/installed in the enclosure.	10	
	Circuit Board Manufacturing Subtotal:	65	
	Circuit Diagram Subtotal:	20	
	Component List Subtotal:	5	
	Description of Operation Subtotal:	25	
	Tools/Instrument List Subtotal:	5	
	Circuit Board Manufacturing Subtotal:	65	

TOTAL (PART 1 = 120 marks)	
---	--

NOTE: In projects where facets are not applicable, the projects should be marked and the totals adjusted accordingly.

5.3 Design and Make: Part 2**5.3.1 Enclosure design**

- Design an enclosure for your project.
- NO FREEHAND DRAWINGS.
- Draw using EGD equipment **OR** use a CAD program.
- Draw in first-angle orthographic projection.
- Add your drawings after this page.
- Use colour to enhance your drawing.

5.3.2 Manufacture the enclosure neatly according to your design. You may use pre-cut panels from metal, wood and/or Perspex/Plexiglas. You must, however, construct/assemble these parts. Injection-moulded enclosures are also acceptable. It is important that your enclosure and the placement of the parts align with your design.

5.3.3 Choose a name for your device.
Write down the name of the device below.

5.3.4 Design a unique logo for your device, as well as a specification plate and attach it after this page.

5.4 Assessment of the Design and Make Phase: Part 2

NO.	FACET DESCRIPTION	Mark	Achieved mark
Enclosure Design			
1.	Enclosure design is included in first-angle orthographic projection.	2	
2.	Drawn design includes a title box and page border.	1	
3.	Isometric drawing included additionally.	2	
4.	Dimensions are included.	2	
5.	The name of the device is written in the PAT document.	1	
6.	The logo design and specification plate design is in the PAT document.	2	
	Enclosure Design Subtotal:	10	
Enclosure Manufacturing			
7.	Enclosure matches the design. Dimensions and placement correlate.	1	
8.	Name of the device is attached on the enclosure.	1	
9.	The logo design is attached on the enclosure.	2	
10.	The logo design on the enclosure is durable and not merely a paper pasted on the enclosure (painted/used decoupage/screen printed/sublimation printed).	2	
11.	The enclosure is manufactured from scratch/pre-cut parts. Does NOT include: cardboard, paper, margarine container Does include: sheet metal, Perspex, Plexiglas, wood, glass and other raw materials, injection-moulded plastic boxes	5	
12.	Holes/Cut-outs in the enclosure are made with the appropriate tools.	3	
13.	Specification plate with the learner's name, operating voltage, fuse rating and additional information on the project.	2	
14.	Enclosure is neatly prepared, painted and aesthetically pleasing.	2	
15.	The circuit board is mounted using appropriate methods inside the enclosure. (NO double-sided tape, Prestik, glue, chewing gum, masking tape, etc.)	2	
	Enclosure Manufacturing Subtotal:	20	

TOTAL (PART 2 = 30 marks)
--

6. PROJECTS

6.1 Practical Project 6.1: Sound-to-light Controller

This sound-controlled lights circuit design is used to control the brightness of the lights attached to it in sync with the sound that is being captured by its microphone. This electronic circuit design is very common in disco houses, bars, parties, etc.

Usually, sound-controlled lights are just connected in parallel with the loudspeakers. This configuration has two disadvantages: first, a very powerful amplifier can destroy the lights, or worse, a defective light can destroy the amp. This problem is avoided by the circuit by not connecting directly to the amp. Instead, it picks up the sound with its microphone.

The power-supply part is on the left of the electret microphone amplifier and the light controller part is on the right. The capacitors C2 and C3 are the capacitive voltage dividers and reduce the power supply level. Diodes D1 and D2 rectify the positive swing of the AC voltage. The network, composed of L1 and C1, protects the power line from voltage surges. In this circuit design, an electret microphone is being used. Take note that there are two types of electret mics. The first type has three pins for power, ground and output. The second type has only two pins. The second type is used for this circuit.


WARNING: Some parts in the circuit board are subject to lethal potential because the device is connected to 230 V AC. When plugging in the project, place it in a plastic or wooden box to prevent the circuit from shocking you. Avoid connecting this circuit to other appliances (e.g. to the output of an amplifier by means of a cable) because of the absence of a mains transformer. Use only the microphone in the main case to pick up the sound.

COMPONENT LIST

R1	560 k Ω /1 W	C8, C10,C12	0,047 μ F
R2, R3	15 k Ω ¼ W	C9	22 μ F 16 V
R4	33 k Ω /¼ W	C11	47 μ F 16 V
R5, R6, R9	1 k Ω ¼ W	D1, D2	1N4004
R7	18 k Ω ¼ W	D3	1N4742 12v/1 W
R8	560 Ω ¼ W	F1	10 A fuse 220 V
R10, R11, R12	100 k Ω	F2	100 mA fuse 220 V
R13, R14, R15	5 k Ω Pot	F3, F4, F5	220 V 3 A fuse
C1	0,47 μ F 630 V	L1	40 μ H 6 A 10-15 turns on a ferrite core
C2, C5	0,1 μ F/220 V	B1, B2, B3	60 W incandescent lamp
C3	1 000 μ F/16 V electrolytic	Mic	Low-impedance microphone
C4	100 μ F/16 V	S1A & S1B	Double-pole switch
C6	25 μ F/6 V	T1,T2	BC 547
C7	1 μ F 16 V	T3,T4,T5	TIC 106 or BT 136



SOUND-TO-LIGHT CONTROLLER CIRCUIT

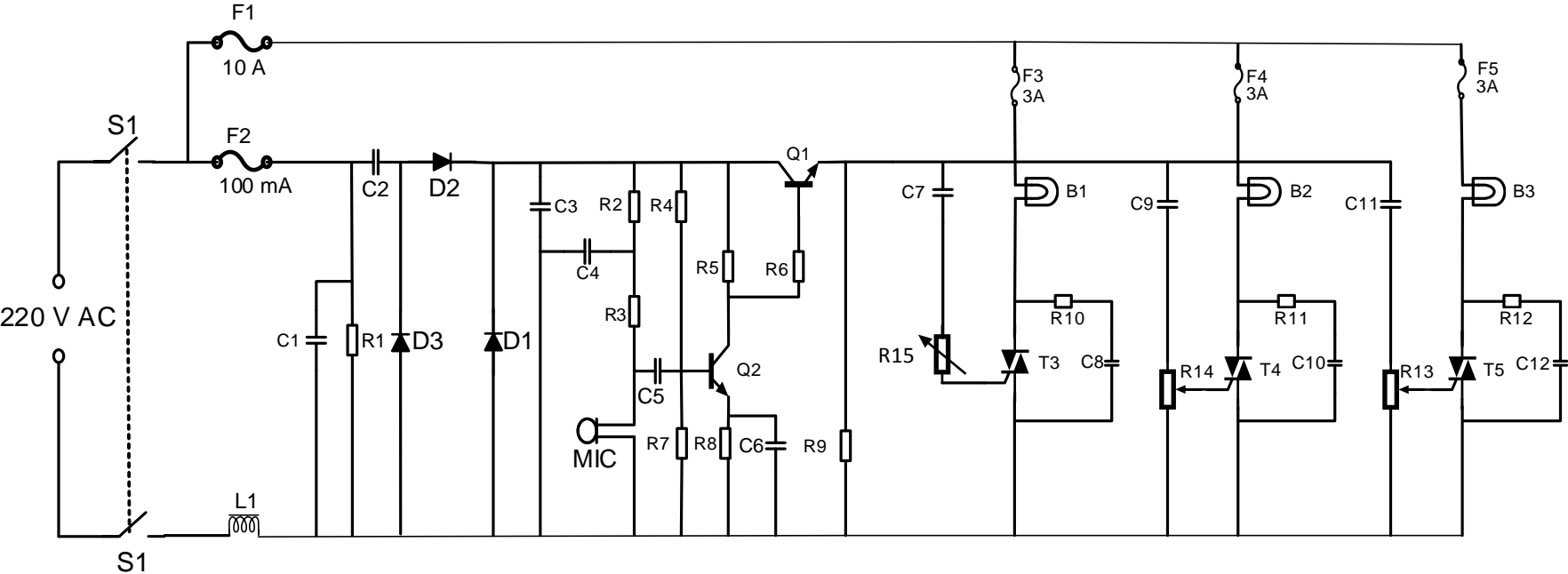

ALTERNATIVE CIRCUIT


6.2 Practical Project 6.2: Automatic battery charger with battery-voltage bar-graph display

This automatic battery charger project is based on the National Semiconductor LM350 3 A adjustable regulator. It is designed to charge 12 V lead-acid batteries. When the switch SW1 is pushed, the output of the charger will go up to 14,5 V. The initial charging current is limited to 2 A. As the charge of the battery continues to rise, the charging current decreases to 150 mA and the output voltage is reduced to 12,5 V. At this stage the charging is terminated and the light-emitting diode lights up to indicate that the charging process has been completed.

The schematic diagram below shows how the various components are connected. The first part of the diagram shows how the DC power supply to LM350 is achieved. The combined use of varistor V1 and fuse F1 is to protect the circuit from overcurrent and power surge of the mains supply.

Transformer T1 is used to step down the input voltage from the mains to 16 V AC. Diode bridge DB and electrolytic capacitor E1 are used to rectify the AC voltage to DC voltage. This rectified DC power supply is fed into the input of the second circuit where LM350 and operational amplifier LM301A are used to control the charging current and voltage of the lead-acid battery. Once the charge is full, transistor Q1 will turn ON and LED L1 will be ON to indicate that the charging has been completed. A heat sink is attached to LM350 to transfer the heat generated from the regulator to the ambient.

This bar-graph LED-battery-level-indicator project is based on the LM3914 monolithic IC of the National Semiconductor that senses the voltage levels of the battery and drives the 10 light-emitting diodes based on the voltage level that is detected. It provides a linear analogue display output and has a pin that can be configured to display the output in moving dot or bar graph. The current driving the LEDs is regulated and programmable, hence limiting resistors are not required. The schematic diagram below shows how the various components are connected. Switch S1 is used to change the display type from moving dot to bar graph type. When S1 is ON, the display type is bar graph, but when it is OFF, the display changes to the moving dot type. R3 is used to set the lower limit of the display. Use a variable DC power supply and set the VBAT to 10,5 V. Adjust VR1 until the LED L1 turns ON. Next, set the VBAT to 15 V; adjust VR2 until all the LEDs turn ON (when S1 is ON).

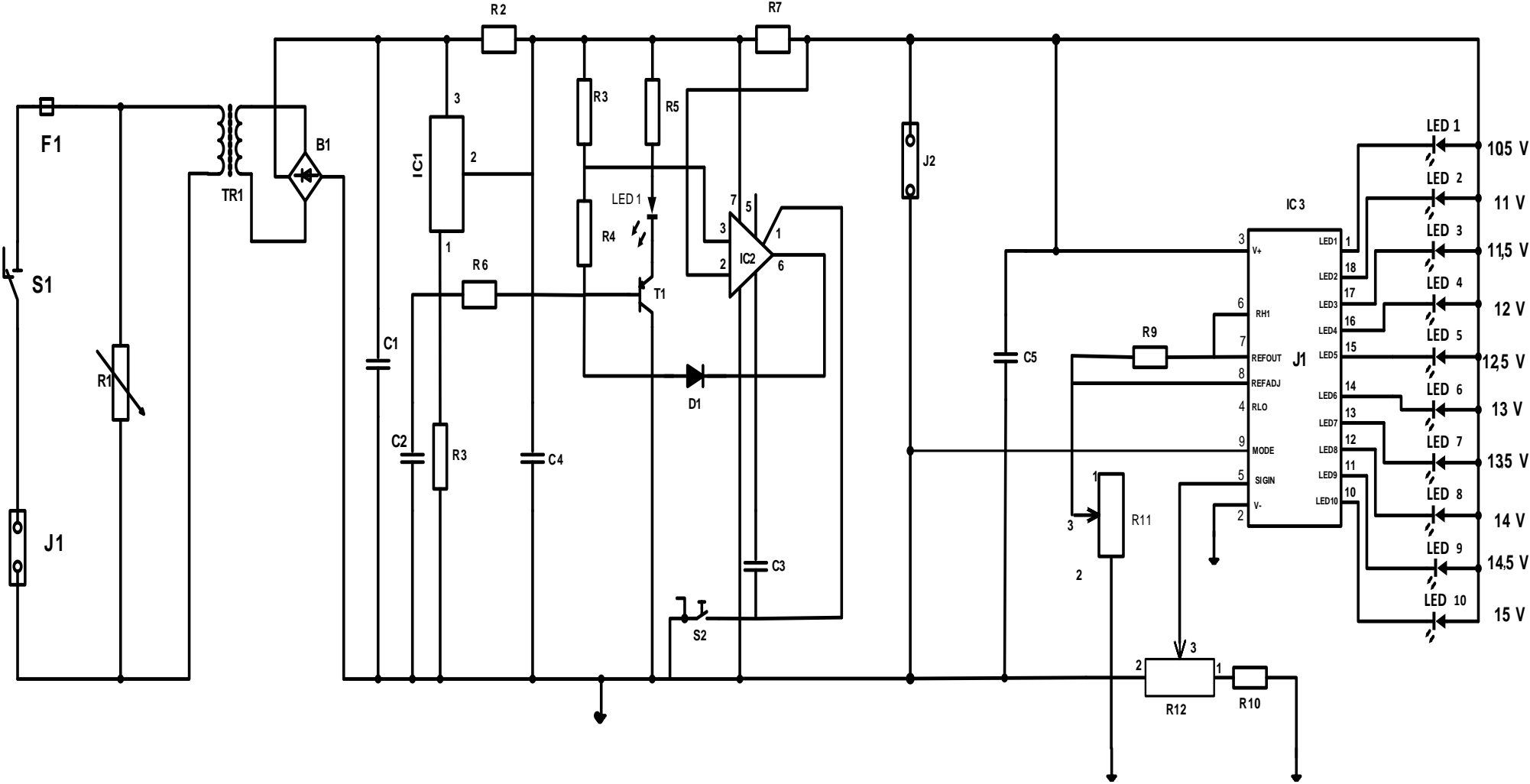

COMPONENT LIST			
R1	varistor 14 mm	B1	5 A diode bridge
R2	500 ohm, 5 W	C1	6 800 uF 35 V electrolytic capacitor (battery charger)
R3, R6	15 K $\frac{1}{4}$ W	C2	0,1 uF ceramic 104
R4	230 ohm $\frac{1}{4}$ W	C3	1 nF ceramic 102
R5	1k	C4	1 uF electrolytic 25 volt
R7	0,2 ohm, 5 W	D1	1N 4148 diode
R8	3k3 $\frac{1}{4}$ W	IC1	LM350 16 volt positive voltage regulator
J1	mains supply	IC2	LM301 H operational amplifier
J2	12 V connector for battery/battery clamps	S1	On/Off switch for mains voltage SPST toggle switch
F1	500 mA fast-blow fuse	S2	push-to-make switch
TR1	240 V–16 V transformer 3 A (+/-50 VA)	LED 1	red LED 5 mm
R9	1k2 $\frac{1}{4}$ W 5%	IC 3	LM3914 N bar-graph display driver
R10	4k7 $\frac{1}{4}$ W 5%	C5	10 μ F 25 volt electrolytic capacitor (Bargraph voltage indicator)
R11	5k potentiometer	T1	PN2907 alternative (BC527 or BC 528)
LED 1,10	red		
LED 4,5,6,7	green		
LED 2,3,8,9	amber		
R12	5k potentiometer		


6.3 Practical Project 6.3: Sine-wave Inverter Circuit Diagram

PLEASE NOTE: The sine-wave inverter has been included to keep up with the current load shedding trends. If this project is too expensive, the **SQUARE WAVE INVERTER** can be built. Schools can purchase one transformer and a set of batteries to demonstrate the workings of this project.

An inverter provides power backup for mains-based appliances in the event of a power failure. Most of the inverters available in the market have complicated circuit designs and are not very economical. Some of them produce a square-wave output, which is undesirable for inductive loads.

Here we designed a simple sine wave inverter circuit that produces 50Hz quasi-sine wave output using a single IC CD4047 and some discrete components, which makes it a very cost-effective solution.

COMPONENT LIST	
SEMICONDUCTORS	
IC1	CD4047 multivibrator
SCR1	2P4M SCR
T1 – T8	IRF 250 MOSFET
T9 – T11	BS548 NPN transistor
ZD1	5,1 V, 1W zener diode
ZD2 – ZD5	5,1 V zener diode
D1 – D6	1N4007 rectifier diode
LED1, LED2	5 mm LED
RESISTORS (all 0,25 W, $\pm\%$ carbon)	
R1	560 Ω
R2, R3	1,2 k Ω
R4,R5,R6, R8, R9, R11	1 k Ω
R12	2,2 k Ω
R7	220 Ω
R10	5,6 k Ω
VR1	470 k Ω pre-set
VR2 – VR4	10 k Ω pre-set
CAPACITORS	
C1	0,2 μ F, 100 V ceramic disk
C2,C3	100 μ F, 35 V electrolytic
C4	1000 μ F, 35 V electrolytic
C5-C7	0,47 μ F, 600 V polyester
MISCELLANEOUS	
PZ1	Piezo Buzzer
S1	SPST switch
X1	18-0-18V, 40 A primary to 0-230V-600 V secondary inverter transformer
BATT1, BATT2	12 V (Ah determined by the size transformer)

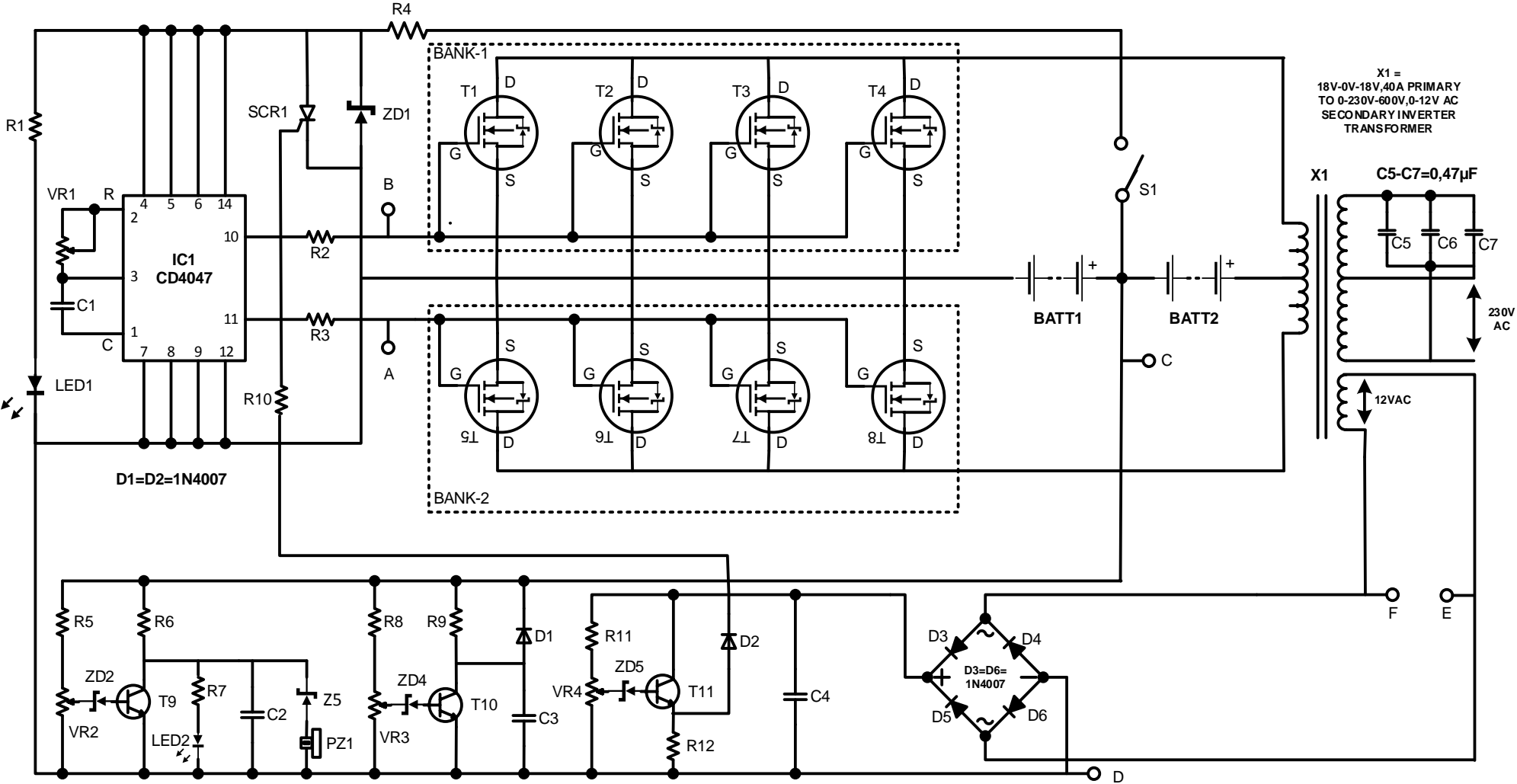

SINE WAVE INVERTER CIRCUIT DIAGRAM

It comprises a CD4047 multivibrator (IC1), MOSFET, IRF250 MOSFETs (T1 through T8), transistors, and a few discrete components.

IC CD4047 has built-in facilities for a stable and bistable multivibrator. The inverter application requires two outputs that are 180 degrees out of phase. Therefore, IC1 is wired to produce two square-wave output signals at pins 10 and 11 with 50 Hz frequency, 50% duty cycle, and 180-degree phase shift. The oscillating frequency is decided by external pre-set VR1 and capacitor C1.


These two signals drive the two MOSFET banks (bank-1 and bank-2) alternatively. When pin 10 of IC1 is high and pin 11 low, MOSFETs of bank-1 (T1 through T4) conduct, while MOSFETs of bank-2 (T5 through T8) remain in the non-conducting state.

Therefore, a large swing of current flows through the first half of the primary winding of inverter transformer X1 and 230V AC develops across the secondary winding. During the next half cycle, the voltage at pin 10 of IC1 goes low, while the voltage at pin 11 is high. Thus, MOSFETs of bank-2 conduct, while the MOSFETs of bank-1 remain non-conducting. Therefore current flows through the other half of the primary winding and 230 V AC develops across the secondary winding. This way an alternating output voltage is obtained across the secondary winding.

The sine wave output is obtained by forming a tank circuit with the secondary winding of the inverter transformer in parallel with capacitors C5 through C7. Two 2,2 μF capacitors are connected to the gates of the MOSFETs in both banks with respect to the ground if a proper sine wave is not produced.

The natural frequency of the tank circuit is adjusted to 50 Hz. Current consumption with no load is only 500 mA due to the 50% duty cycle of the square-wave signal. As the load is increased, current consumption increases. The supply voltage to IC1 is limited to 5,1 volts by using Zener ZD1 and resistor R4 with the external battery.

LOW-BATTERY INDICATOR CIRCUIT

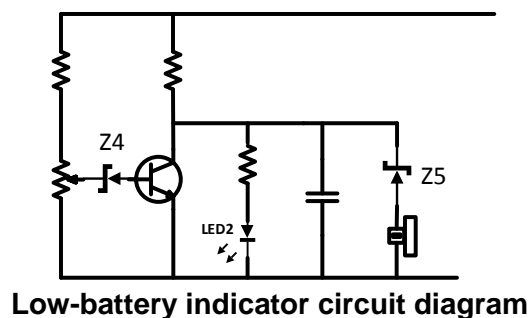


Low-battery indicator circuit diagram

The low-battery indication circuit consists of transistor T9, pre-set VR2, Zener diode ZD2, resistors R5, R6, and R7, LED2, and capacitor C2. The 12 V supply voltage from BATT.1 is applied to the low-battery indicator circuit with a full load (not more than 1 000 watts) connected to the inverter output.

The voltage across the load is 230 V AC. At this instant, adjust pre-set VR2 such that Zener diode ZD2 and transistor T9 conduct to drop the collector voltage to 0.7 volt keeping LED2 'off.' If the supply voltage goes below 10.5 volts, the voltage across the load decreases from 230 V AC to 210 V AC.

At this instant, Zener diode ZD2 and transistor T9 do not conduct, and hence the collector voltage increases to about 10.5 volts and LED2 glows to indicate the low voltage of the battery.

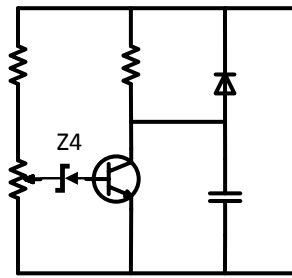LOW-BATTERY CUT-OFF CIRCUIT**Low-battery cut-off circuit diagram**


If the battery is discharged to zero volts repeatedly, the battery life will decrease. The low-battery cut-off circuit consists of transistor T10, pre-set VR3, Zener diode ZD4, resistors R8 and R9, capacitor C3, and diode D1.

Adjust pre-set VR3 such that when the voltage across the load is above 200 volts, Zener diode ZD4 and transistor T10 conduct. The collector voltage of T10 is about 0.7 volts in this case and hence the SCR (SCR1) will not conduct. However, if the voltage across the load goes below 200 volts, Zener diode ZD4 and transistor T10 will not conduct and the collector voltage of T10 will increase, causing the SCR to conduct. Once the SCR conducts, the supply voltage to IC1 (CD4047) will be 0.7 volts, due to which IC1 will be unable to produce the voltage pulses at output pins 10 and 11 and the inverter will turn off automatically. During this state, the SCR remains conducted.

The low cut-off of the inverter can be set at the load voltage of 170 volts for the tube light, fan, etc. So the tube light and fan will not be switched off until the voltage goes below 170 volts.

NO-LOAD CUT-OFF CIRCUIT

If there is no load connected to the output of the inverter, the output voltage is 270 to 290 volts. This voltage is sensed by the 0-12V tap at the secondary winding of inverter transformer X1, which is connected to the no-load cut-off circuit comprising Zener diode ZD5, transistor T11, pre-set VR4, resistors R12 and R11, and capacitor C4.

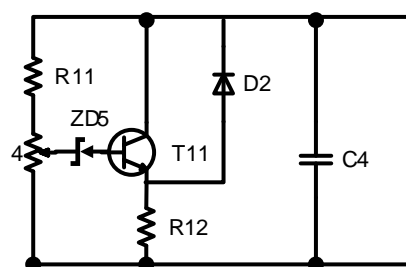**No-load cut-off circuit diagram**

When no load is connected, the voltage at the 12 V tap will also increase. This voltage is rectified by the full-wave bridge rectifier comprising diodes D3 through D6, filtered by capacitor C4 and given to transistor T11.

Adjust pre-set VR4 such that if the inverter voltage goes above 250 volts, Zener diode ZD5 and transistor T11 conduct. This increases the emitter voltage; hence the SCR fires to switch the inverter 'off.' When a proper load is connected, the inverter will automatically turn on.

SINE-WAVE INVERTER PCB DESIGN

An actual size, single-side PCB for the pure sine wave inverter circuit is shown below.

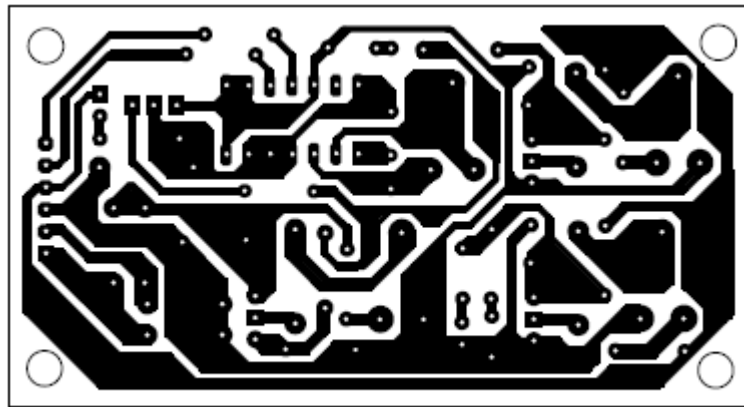


Fig. 2: An actual-size, single-side PCB for the sinewave inverter

A PCB for the sine-wave inverter circuit

A suitable connector CON1 is provided on the PCB to connect the MOSFET banks and the transformer externally. Connector CON1 pins A through F are also marked on the schematic. Assemble the circuit on a PCB as it saves time and minimizes assembly errors. Carefully assemble the components and double-check for any overlooked errors. MOSFETs should be mounted over heat sinks using mica spacers as the insulators between them.

SINE-WAVE INVERTER PCB LAYOUT

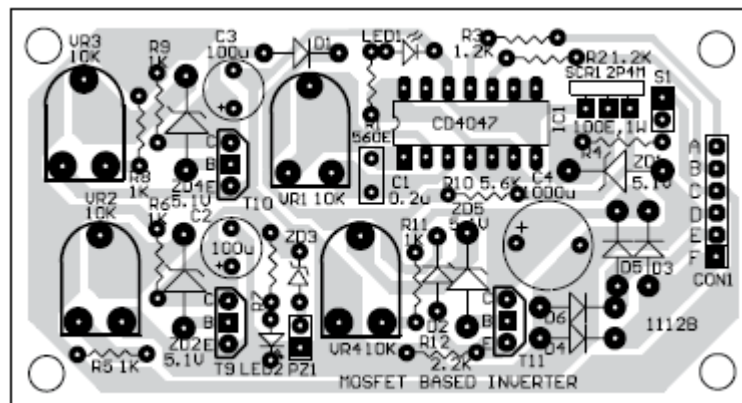


Fig. 3: Component layout for the PCB

Sine-wave inverter PCB layout

Connect the 24V supply terminal directly to the centre tap of the primary winding of the inverter transformer, which carries a maximum current of more than 50 amperes with 1 000 watts.


The current depends on the load applied. There is no need to add a switch in the high-current path to make the inverter turn on and off. The inverter can be switched on and off by low-current switch S1.

OR

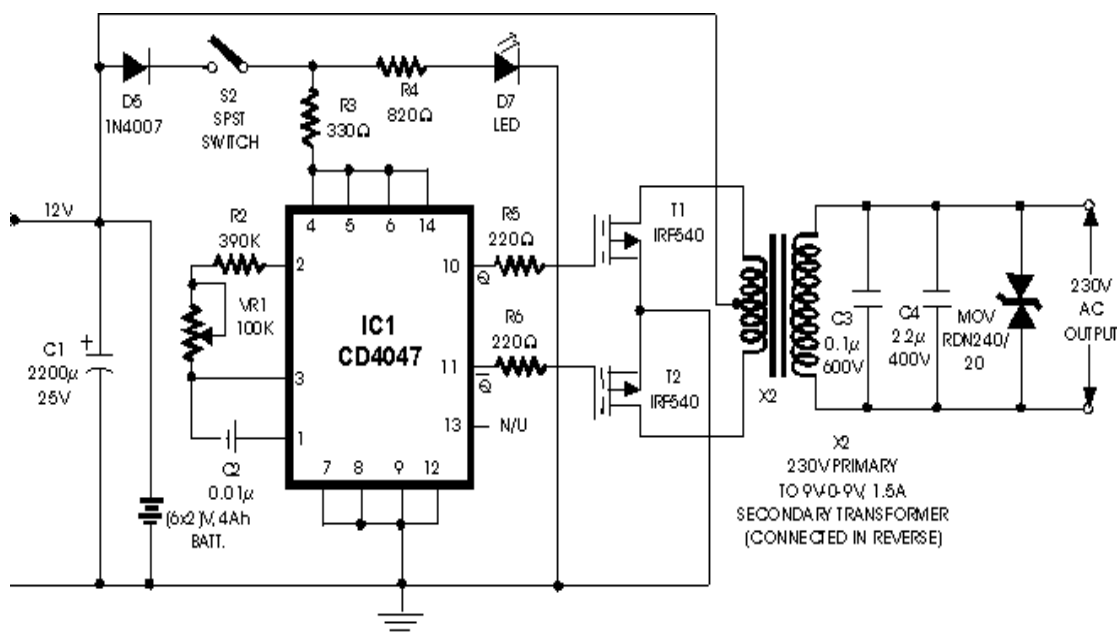6.4 Practical Project 6.4: SQUARE-WAVE INVERTER 100 W 12 VDC TO 230 VAC BY IC 4047 – IRF540

A 100 W inverter circuit converts 12 VDC to 230 VAC with IRF540. The circuit applied IC 4047 to generate a continuous wave signal and IRF540 to amplify the signal to be stepped up by the transformer.

NOTE: You will need a 2–3 A centre-tapped transformer to handle/supply a 100 W load.



INVERTER 100 W 12 VDC TO 230 VAC BY IC 4047 – IRF540

COMPONENT LIST			
Diode	1N4007	VR1	100 KΩ
C1	2 200 μF	R2	390 KΩ
C2	0,01 μF	R3	330 Ω
C3	0,1 μF	R4	820 Ω
C4	2,2 μF	R5	220 Ω – 330 Ω
D5	1N4007	R6	220 Ω – 330 Ω
D7	LED		
MOV	RDN240/20		
IC 4047 – IRF540		2 x D MOSFET (T1) IRF540	
LED		S2 SPST switch	
Supply 12 V or 12 V DC supply for testing			
TRANSFORMER on circuit diagram optional; a smaller one can be used for testing.			

NOTE: All circuits MUST include an On/Off switch with an ON indicator and fuse protection.

7. CONCLUSION

On completion of the practical assessment task, learners should be able to demonstrate their understanding of the industry, enhance their knowledge, skills, values and reasoning abilities as well as establish connections to life outside the classroom and address real-world challenges. The PAT furthermore develops learners' life skills and provides opportunities for learners to engage in their own learning.