



basic education

Department:
Basic Education
REPUBLIC OF SOUTH AFRICA

ELECTRICAL TECHNOLOGY (DIGITAL ELECTRONICS)

GUIDELINES FOR PRACTICAL ASSESSMENT TASKS (PAT)

GRADE 12

2024

These guidelines consist of 54 pages.

TABLE OF CONTENTS

| | PAGE |
|---|-------------|
| 1. INTRODUCTION | 3 |
| 2. TEACHER GUIDELINES | 5 |
| 2.1 How to administer PATs | 5 |
| 2.2 How to mark/assess PATs | 5 |
| 2.3 PAT Programme of Assessment (PAT PoA) | 6 |
| 2.4 Moderation of PATs | 7 |
| 2.5 Absence/Non-submission of tasks | 7 |
| 2.6 Simulations | 8 |
| 2.7 Projects | 8 |
| 2.8 Working mark sheet | 9 |
| 3. LEARNER GUIDELINES | 10 |
| 3.1 PAT 2024 cover page | 10 |
| 3.2 Instructions to the learner | 11 |
| 3.3 Declaration of Authenticity (COMPULSORY) | 11 |
| 4. SIMULATIONS | 12 |
| 4.1 Simulation 1: Inverting op amp | 12 |
| 4.2 Simulation 2A: Switching circuits using a 741 op amp | 18 |
| Simulation 2B: Op-amp integrator using 741 IC | 22 |
| 4.3 Simulation 3: Connecting a 7-segment display to a 4-bit BCD 7-segment driver | 26 |
| 4.4 Simulation 4A: S-R flip-flop circuit | 29 |
| Simulation 4B: PICAXE | 33 |
| 5. SECTION B: DESIGN AND MAKE | 35 |
| 5.1 Design and Make: Part 1 | 36 |
| 5.2 Assessment of the Design and Make Phase: Part 1 | 38 |
| 5.3 Design and Make: Part 2 | 40 |
| 5.4 Assessment of the Design and Make Phase: Part 2 | 41 |
| 6. PROJECTS | 42 |
| 6.1 Practical Project 6.1: Sound-to-light Controller | 42 |
| 6.2 Practical Project 6.2: Automatic Battery Charger with Battery-voltage Bar-graph Display | 46 |
| 6.3 Practical Project 6.3: Sine-wave Inverter Circuit Diagram | 49 |
| 6.4 Practical Project 6.4: Square-wave inverter 100 W 12 VDC TO 230 VAC BY IC 4047 – IRF540 | 54 |
| 7. CONCLUSION | 54 |

1. INTRODUCTION

The 18 Curriculum and Assessment Policy Statements subjects which contain a practical component all include a practical assessment task (PAT). These subjects are:

- **AGRICULTURE:** Agricultural Management Practices, Agricultural Technology
- **ARTS:** Dance Studies, Design, Dramatic Arts, Music, Visual Arts
- **SCIENCES:** Computer Applications Technology, Information Technology, Technical Sciences; Technical Mathematics
- **SERVICES:** Consumer Studies, Hospitality Studies, Tourism
- **TECHNOLOGY:** Civil Technology, Electrical Technology, Mechanical Technology and Engineering Graphics and Design

A practical assessment task (PAT) mark is a compulsory component of the final promotion mark for all candidates offering subjects that have a practical component and counts 25% (100 marks) of the end-of-the-year examination mark. The PAT is implemented across the first three terms of the school year. This is broken down into different phases or a series of smaller activities that make up the PAT. The PAT allows for learners to be assessed on a regular basis during the school year and it also allows for the assessment of skills that cannot be assessed in a written format, e.g. test or examination. It is therefore important that schools ensure that all learners complete the practical assessment tasks within the stipulated period to ensure that learners are resulted at the end of the school year. The planning and execution of the PAT differs from subject to subject.

Practical assessment tasks are designed to develop and demonstrate a learner's ability to integrate a variety of skills in order to solve a problem. The PAT also makes use of a technological process to inform the learner what steps needs to be followed to derive a solution for the problem.

The PAT consists of four simulations and a practical project. The teacher may choose any ONE of the practical projects and any TWO simulations available for DIGITAL ELECTRONICS.

The teacher must apply assessment on an ongoing basis at the same time that the learner is developing the required skills. TWO simulations should be completed by the learners, in addition to the manufacturing of a practical project.

The PAT incorporates all the skills the learner has developed throughout the year. The PAT ensures that all the different skills will be acquired by learners on completion of practical work, as well as the correct use of tools and instruments.

Requirements for presentation

A learner must present the following:

- PAT file with all the evidence of simulations, design and prototyping. A copy of the PAT 2023 cover page. The relevant simulations and assessment sheets should be copied and handed to each learner to include in the file.
- Practical project with:
 - Enclosure:
 - The file must include a design.
 - The enclosure and the design must match.
 - No cardboard boxes are allowed.
 - Plastic wooden and metal enclosures are acceptable.
 - Enclosures that are manufactured and/or assembled by the learners are preferred.
 - The enclosure should be accessible for scrutiny inside.
 - Lids that are secured are preferred.
 - Circuit board:
 - The file should include the PCB design.
 - The PCB must be mounted inside the enclosure in such a manner that it can be removed for scrutiny. Alternatively, inspection can be made from the bottom in cases where translucent (see-through) enclosures are used.
 - Switches, potentiometers, connectors and other items must be mounted.
 - Wiring must be neat and bound/wrapped.
 - Wiring must be long enough to allow for the PCB to be removed and inspected with ease.
 - Logo and name:
 - The file should contain the logo and name design and specification plate.
 - Logo, specification plate and name must be prominent on the enclosure.
 - The logo/specification plate must be affixed in a permanent manner – painted, glued or stuck on with vinyl.

The PAT will have a financial impact on the school's budget and school management teams are required to make provision to accommodate this particular expense.

PAT components and other items must be acquired timeously, for use by the learners, before the end of the first term at the start of the academic year.

It is the responsibility of the HOD to ensure that the teacher is progressing with the PAT from the start of the school year.

Provincial departments are responsible for setting up moderation timetables and consequently PATs should be completed in time for moderation.

2. TEACHER GUIDELINES

2.1 How to administer PATs

Teachers must ensure that learners complete the simulations required for each term. The project should be started in January in order to ensure its completion by August. In instances where formal assessments take place, the teacher has to assume the responsibility thereof.

The PAT should be completed during the FIRST THREE TERMS and must be ready at the start of PAT moderation. Teachers must make copies of the relevant simulations and hand them to learners at the beginning of each term.

The PAT must NOT be allowed to leave the workshop and must be kept in a safe place at all times when learners are not working on them.

The weightings of the PAT must be adhered to and teachers are not allowed to change weightings for the different sections.

2.2 How to mark/assess the PATs

The PAT for Grade 12 will be set and assessed internally, but moderated externally. All formal assessment will be done by the teacher.

The teacher is required to produce a working model and model answer file that sets the baseline for assessment at a Highly Competent Level for every project choice exercised by the learners. This file must include all the simulations with answers the teacher has done him/herself. The teacher will use the model answers and project to assess the simulations and projects of the learners.

Once a facet sheet has been completed by the teacher, assessment will be deemed to be complete. No re-assessment will be done once the facet sheets have been completed and captured by the teacher. Learners must ensure that the work is done to the required standard before the teacher finally assesses the PAT during each stage of completion.

2.3 PAT Programme of Assessment (PAT PoA)

The programme of assessment (PoA) of the PAT is as follows:

| TIME FRAME | ACTIVITY | RESPONSIBILITY |
|------------------------|--|---|
| | Preparation for PAT 2024 | Teacher – Builds the models and works out the model answers for the simulations. Identifies shortages in tools, equipment and consumable items for simulations that must be procured. SMT – Receives procurement requests from teachers and processes payments for the acquisition of required items |
| January–March 2024 | Simulation 1 | Teacher – Copies and hands out simulations Learners – Complete simulations Teacher – Assesses simulations HOD – Checks if tasks have been completed and marked by the teacher before the holidays |
| January 2024 | PAT project – procurement | Teacher – Obtains quotations for PAT projects Principal – Approves PAT procurement for PAT projects Teacher – Ensures that PAT projects are ordered and delivered HOD – Checks in on teacher to see if the process is adhered to |
| February 2024 | PAT project – learners commence with project | Teacher – Ensures that there is secure storage for PAT projects Teacher – Hands out and takes in PAT projects Teacher – Includes practical sessions for learners to complete the PAT project every week Learners – Commence with completion of the PAT project HOD – Checks in on teacher to ensure that practical workshop sessions take place on a weekly basis |
| April–June 2024 | Simulation 2 | Teacher – Copies and hands out simulations Learners – Complete simulations Teacher – Assesses simulations HOD – Checks if tasks have been completed and marked by the teacher before the holidays |
| April–June 2024 | Moderation of Simulation 1 | District subject facilitator/subject specialist will visit the school and moderate Simulation 1 10% of learners' work is moderated |
| April–June 2024 | PAT project – learners continue with project | Teacher – Ensures that there is secure storage for PAT projects Teacher – Hands out and takes in PAT projects Teacher – Includes practical sessions every week for learners to complete the PAT project Learners – Continue with completion of the PAT project HOD – Checks in on teacher to ensure that practical workshop sessions take place on a weekly basis |
| July holidays 2024 | PAT intervention | Learners that are behind on the PAT are required to complete the project during these holidays. |
| July–August 2024 | Moderation of Simulation 2 | District subject facilitator/subject specialist will visit the school and moderate Simulation 2 – different learners from the previous term 10% of learners' work is moderated |
| July–August 2024 | PAT project – completion | Teacher – Ensures that there is secure storage for PAT projects Teacher – Hands out and takes in PAT projects Teacher – Completes the PAT project with learners and compiles the PAT file Learners – Complete the PAT project and file HOD – Checks to see that 100% of the PAT files and projects are completed and assessed |
| September–October 2024 | PAT moderation | PAT projects are moderated by subject facilitators/subject specialists from the province and learners are available to demonstrate skills 10% of learners are moderated randomly |

2.4 Moderation of PATs

Provincial moderation of each term's simulations will start as early as the following term. Simulation 1 should be moderated as soon as the second term starts. Similarly, Simulation 2 will be moderated in July. The project will, however, only be moderated on completion.

During moderation of the PAT, the learner's file and project must be presented to the moderator.

The moderation process is as follows:

- During moderation, learners are randomly selected to demonstrate the different simulations. All four simulations will be moderated.
- The teacher is required to build an exemplar model of each project type chosen for the school.
- This model must be on display during moderation.
- The teacher's model forms the standard of the moderation at Level 4 (Highly Competent).
- Level 5 assessments must exceed the model of the teacher in skill and finishing.
- Learners who are moderated will have access to their files during moderation and may refer to the simulations they completed earlier in the year.
- Learners may NOT ask assistance from other learners during moderation.
- All projects and files must be on display for the moderator.
- If a learner is unable to repeat the simulation or cannot produce a working circuit during moderation, marks will be deducted and circuits assessed as not being operational.
- The moderator will randomly select no fewer than two projects (not simulations) and the learners involved will have to explain how the project was manufactured.
- Where required, the moderator should be able to call on the learner to explain the function and principles of operation, and request the learner to exhibit the skills acquired through the simulations for moderation purposes.
- On completion the moderator will, if needed, adjust the marks of the group upwards or downwards, depending on the outcome of moderation.
- Normal examination protocols for appeals will be adhered to, if a dispute arises from adjustments made.

2.5 Absence/Non-submission of tasks

The absence of a PAT mark in Electrical Technology without a valid reason: The learner will be given three weeks before the commencement of the final end-of-year examination to submit the outstanding task. Should the learner fail to fulfil the outstanding PAT requirement, such a learner will be awarded a zero (0) for that PAT component.

2.6 Simulations

Simulations are circuits, experiments and tests/tasks which the learner will have to build, test and measure and practically do as part of the development of practical skills. These skills have to be illustrated to the external moderator that visits the school at intervals during the school year.

Teachers who make use of simulation programs on a computer may use them for the learners to practise on. However, it is required that the circuit be built using real components and that measurements be made with actual instruments for the purposes of assessment and moderation.

The correct procedure for completing simulations is outlined below for teachers and school management teams who are responsible for the implementation of the PAT in Electrical Technology.

- STEP 1: The teacher will choose simulations from simulations that are provided.
- STEP 2: Compile a list of the components needed for every simulation. Add extra components which might be needed as these items are very small and get lost/damaged very easily when learners work with them.
- STEP 3: Contact three different electronics component suppliers for comparative quotations.
- STEP 4: Submit the quotations to the SMT for approval and procurement of the items.
- STEP 5: Place the components in storage. Collate items for each simulation, thus making it easier to distribute and use during practical sessions. Ensure that different values of components do not mix, as this would lead to components being used incorrectly and this could damage the component and in extreme cases, the equipment used.
- STEP 6: Copy the relevant simulations and hand them out to learners at the start of the term.

Teachers are allowed to adjust circuits and component values to suit their environment/resource availability.

Teachers are required to develop a set of model answers in the teacher's file. Moderators will use the teacher's model answers and artefacts when moderating.

2.7 Projects

The projects are construction projects teachers can choose for their learners. These projects are based on proven circuits provided by schools and subject advisors. The projects are based on working prototypes and require careful construction in order for it to operate correctly.

Projects vary in cost and teachers must ensure that the projects chosen fall within the scope of the school's budget.

Once the teacher has decided on a circuit, he/she must construct the prototype. Thereafter, copies of the provided circuit can be made and distributed to learners. They **MUST** redraw these circuits in their files correctly.

The description of the operation of the circuits is NOT complete. Learners are required to interrogate the function of the components in the provided circuit. Learners should elaborate on the purpose of components in the circuit. It is recommended that learners investigate similar circuits available on the internet and in the school library or workshop reference books.

2.8 Working mark sheet

(A working Excel file is provided with this PAT.)

| PAT mark sheet | | Term 1 | Term 2 | Project | | Total = Term 1 + Term 2 + Project | Mark out of 100 | Moderated Mark |
|----------------|-----------------|--------------|--------------|------------------------|------------------------|--------------------------------------|-----------------|----------------|
| No. | Name of Learner | Simulation 1 | Simulation 2 | Design and Make Part 1 | Design and Make Part 2 | | | |
| | | 50 | 50 | 120 | 30 | 250 | | |
| 1. | | | | | | | | |
| 2. | | | | | | | | |
| 3. | | | | | | | | |
| 4. | | | | | | | | |
| 5. | | | | | | | | |
| 6. | | | | | | | | |
| 7. | | | | | | | | |
| 8. | | | | | | | | |
| 9. | | | | | | | | |
| 10. | | | | | | | | |
| 11. | | | | | | | | |
| 12. | | | | | | | | |
| 13. | | | | | | | | |
| 14. | | | | | | | | |
| 15. | | | | | | | | |
| | Total | | | | | | | |
| | Average | | | | | | | |

Teacher Name: _____

Principal Name: _____

Moderator Name: _____

Signature: _____

Signature: _____

Signature: _____

Date: _____

Date: _____

Date: _____

3. LEARNER GUIDELINES**3.1 PAT 2024 COVER PAGE**

(Place this page at the front of the PAT.)

Department of Basic Education Grade 12
CAPS for Technical High Schools Practical Assessment Task – Electrical Technology

Time allowed: Terms 1–3 (2024)

Learner Name: _____

Class: _____

School: _____

Specialisation: DIGITAL ELECTRONICS

Complete simulation 1 or 2 in the first term and Simulation 3 or 4 in the second term.

Project (Write the name of the project): _____

Evidence of moderation:

NOTE:

When the learner evidence selected has been moderated at school level, the table will contain evidence of moderation. Provincial moderators will sign the provincial moderation and only sign if re-moderation is needed.

| Moderation | Signature | Date | Signature | Date |
|-----------------------|-----------|------|---------------|------|
| School-based | | | | |
| District moderation | | | | |
| Provincial moderation | | | Re-moderation | |

Mark allocation

| PAT Component | Maximum Mark | Learner Mark | Moderated Mark |
|-------------------------------------|--------------|--------------|----------------|
| Simulation 1 | 50 | | |
| Simulation 2 | 50 | | |
| Design and Make Project – Circuit | 120 | | |
| Design and Make Project – Enclosure | 30 | | |
| Total | 250 | | |

3.2 Instructions to the learner

- The practical assessment task counts 25% of your final promotion mark.
- All work produced by you must be your own effort. Group work and co-operative work are NOT allowed.
- The practical assessment task must be completed over three terms.
- The PAT file must contain TWO simulations and a practical project.
- Calculations should be clear and include units. Calculations should be rounded off to TWO decimals. SI units should be used.
- Circuit diagrams can be hand-drawn or drawn on CAD. NO photocopies or scanned files are allowed.
- Photos are allowed and may be in colour or greyscale. Scanned photos and photocopies are allowed.
- This document must be placed inside your PAT file together with the other evidence.
- Learners with identical photos will be penalised and receive zero for that section.

3.3 Declaration of Authenticity (COMPULSORY)

Declaration:

I _____ (name) herewith declare that the work represented in this evidence is entirely my own effort. I understand that if proven otherwise, my final results may be withheld.

Signature of learner

Date

4. SIMULATIONS**4.1 Simulation 1: Inverting op amp**

| | | |
|------------------------|----------------------------|--|
| Name of learner: _____ | | Mark <div style="border: 1px solid black; padding: 5px; text-align: center;">50</div> |
| Class: _____ | Date completed: _____ | |
| Date Assessed: _____ | Assessor Signature: _____ | |
| Date Moderated: _____ | Moderator Signature: _____ | |

4.1.1 Purpose:

- To build an inverting operational amplifier circuit using a 741 op-amp integrated circuit (IC)
- To display the output waveforms on an oscilloscope
- To observe how a change in the value of R_F affects the gain and output voltage of the circuit

4.2 Required resources:

| TOOLS/INSTRUMENTS | MATERIALS |
|--|------------------------------------|
| Analogue/Digital trainer | 1 x LM 741 op amp |
| Analogue/Digital oscilloscope (dual trace) | 1 x 10 k Ω for R_{IN} and |
| Function generator | 1 x 22 k Ω for R_F |
| Multimeter | 1 x 47 k Ω |
| Variable DC power supply (split supply) | 1 x 100 k Ω |
| Side cutters | Connecting wires |
| Wire stripper | |
| Long-nose pliers | |
| Breadboard | |

4.1.3 Procedure:

Construct the circuit on the breadboard as shown in FIGURE 4.1.3.


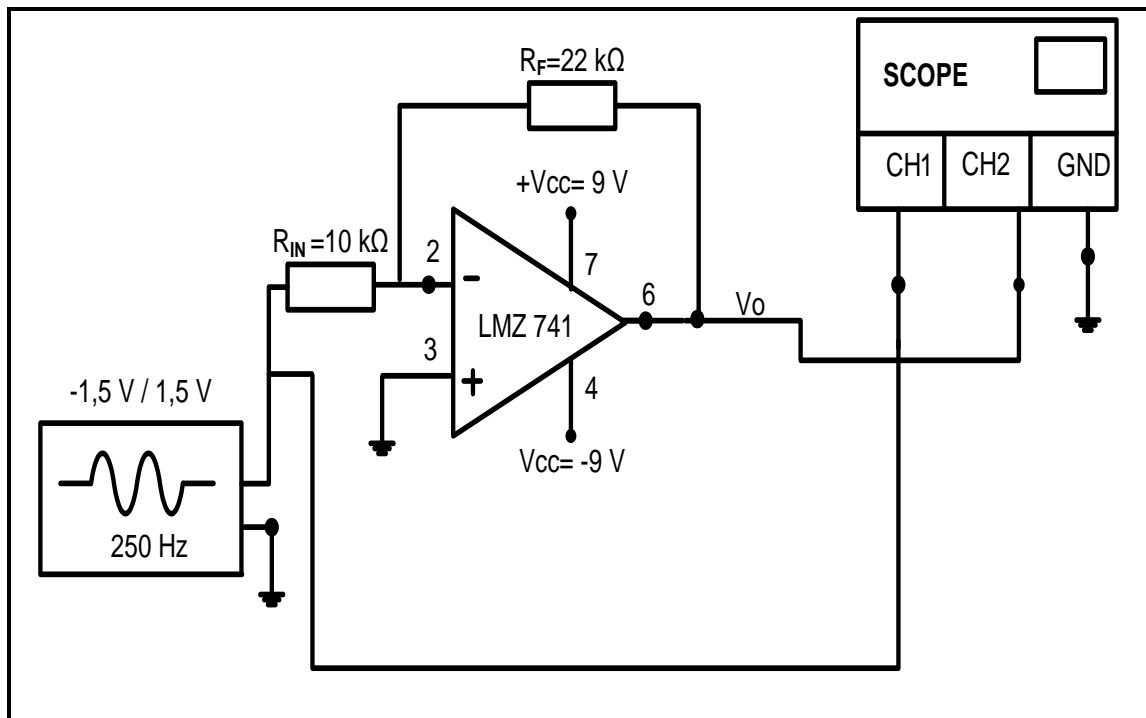


FIGURE 4.1.3: INVERTING OP AMP

- 4.1.4 Set up the oscilloscope to display at least TWO complete cycles for CH1 and CH2 with the voltage settings to display 2/3rd of the screen. (4)
- 4.1.5 Draw and label both the input (from CH1) and output (from CH2) waveforms for two complete cycles on the table on the next page.

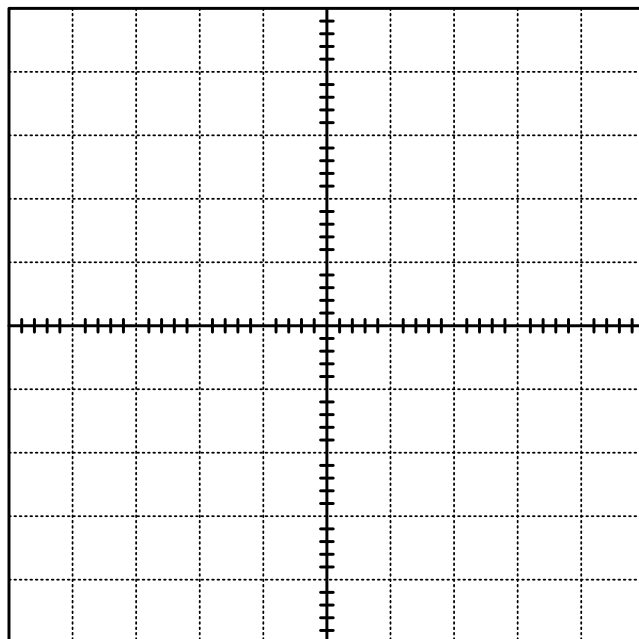- 4.1.6 Write down the peak values of the input and output voltage readings from CH1 and CH2 with $R_F = 22 \text{ k}\Omega$.



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

 V_{IN} : _____ V_{OUT} : _____**TABLE 4.1.6**

NOTE: 1 mark for each correct waveform = 2
 1 mark for each oscilloscope setting = 3
 1 mark for each voltage measurement = 2

(7)

- 4.1.7 Explain the relationship between the input and output waveforms with reference to gain and amplitude.

(3)

- 4.1.8 Use the peak values in QUESTION 4.1.6 to calculate the gain below.
 (All values measured with the oscilloscope are peak values.)

 $A_V =$ _____

= _____

= _____

(3)

- 4.1.9 Calculate the voltage gain of the circuit.

 $A_V =$ _____

= _____

= _____

(3)

- 4.1.10 Measure and record the voltages across V_{OUT} in the table below. Also calculate the voltage gain values in the table below as you change the value of R_F in the circuit. Use $A_V = - \left(\frac{V_{OUT}}{V_{IN}} \right)$


| Resistor R_F | V_{IN} | V_{OUT} | Voltage gain (A_V) |
|--------------------|----------|-----------|------------------------|
| (a) 10 k Ω | 1,5 V | _____ | |
| (b) 47 k Ω | 1,5 V | _____ | |
| (c) 100 k Ω | 1,5 V | _____ | |

TABLE: 4.1.10

NOTE: 1 mark for each correct voltage value = 3
2 marks for each correct gain calculation = 6

(9)

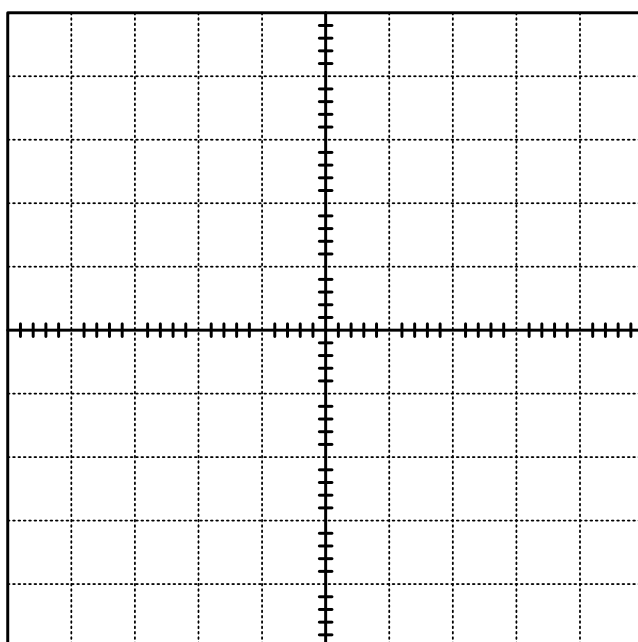- 4.1.11 Draw and label the input and output waveforms for at least two complete cycles in the table below. Indicate the voltage settings for CH 1 and CH 2 with $R_F = 100$ k Ω .



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

 V_{IN} : _____ V_{OUT} : _____**TABLE: 4.1.11**

NOTE: 1 marks for each correct waveform = 2
1 mark for each oscilloscope setting = 3
1 mark for each voltage measurement = 2

(7)

- 4.1.12 Calculate the gain of the amplifier by using resistance values when $R_F = 100 \text{ k}\Omega$.

$$A_V = \underline{\hspace{2cm}}$$

$$= \underline{\hspace{2cm}}$$

$$= \underline{\hspace{2cm}}$$

(3)

- 4.1.13 Refer to the following:

- TABLES 4.1.6 and 4.1.11, the waveforms on the oscilloscope
- The calculations in QUESTIONS 4.1.8 and 4.1.9
- Compare the gain in TABLE 4.1.6 to the gain in TABLE 4.1.11 and write a conclusion on the findings.

(5)

Theory: (40)

**NOTE: Learner competency in this context will mean the following:
(This is done for easy assessment when using a rubric.)**

| | |
|--------------------------|---|
| Not yet competent | Have not met the requirements and will be given another opportunity for reassessment. <ul style="list-style-type: none"> • Be precise about what they did wrong, or the areas they need to improve in. • Explain clearly the level of skill they need to achieve to be assessed as 'competent'. • Indicate whether part or all of the assessment event will need to be repeated. |
| Competent | Have the necessary ability, knowledge or skill to complete the task successfully. <ul style="list-style-type: none"> • Acceptable and satisfactory, though not outstanding. |
| Outstanding | Went beyond expectation (neatness, proficiency – high degree of skills, expertise) |

FACET SHEET FOR SIMULATION 1

| Task description | Mark allocation (tick the appropriate level next to the task indicated) | | | | Allocation of marks |
|--|--|---|--|--|-------------------------|
| | Competent after reassessment of certain parts of the task | Not yet competent after reassessment of certain/all parts of the task | Competent | Outstanding (Highly competent) | |
| Building the inverting op amp using LM 741 IC | The learner was given opportunities to rebuild the circuit after the teacher intervened in identifying and rectifying more mistakes. (1) | The learner was given an opportunity to rebuild part of the circuit after the teacher intervened in identifying and rectifying a few mistakes. (2–3) | The learner correctly built the circuit without the guidance of the teacher. (4–5) | The learner correctly built the circuit without the guidance of the teacher and went beyond expectations and with high proficiency. (6) | $\overline{6}$ |
| Safety aspects | The learner was timeously reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (0) | The learner was sometimes reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (1) | The learner applied safety rules, regulation and correct procedure when using tools and instruments to wire the circuits without being reminded by the teacher. (2) | | $\overline{2}$ |
| Attitude/ Behaviour/ Conduct | The learner was reluctant to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice even after being cautioned/reprimanded. (0) | The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (1) | The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (2) | | $\overline{2}$ |
| Rubric Theory Total Simulation 1 | | | | | + /10 + /40 = /50 |

4.2 Simulation 2: Switching circuits using a 741 op amp**Simulation 2A: Switching circuits using a 741 op amp**

| | | |
|------------------------|----------------------------|--|
| Name of learner: _____ | | Mark <div style="border: 1px solid black; padding: 5px; text-align: center;">50</div> |
| Class: _____ | Date completed: _____ | |
| Date Assessed: _____ | Assessor Signature: _____ | |
| Date Moderated: _____ | Moderator Signature: _____ | |

4.2.1 Purpose:


- To build a frequency changer circuit that can be used in a piano using a 555 IC in FIGURE 4.2.2 on a breadboard
- To display the output waveforms on an oscilloscope
- To calculate the output frequency
- To investigate how a change in R_{IN} affects the frequency and tone of the output

4.2.2 Required resources:


| TOOLS/INSTRUMENTS | MATERIALS |
|--|-----------------------------------|
| Analogue/Digital trainer | 1 1 x 741 IC |
| Analogue/Digital oscilloscope | 1 x 0,68 μ F (25 V capacitor) |
| Dual rail DC power supply (-5 V - 0 - +5 V) | 1 x 150 k Ω resistor |
| Side cutters | 1 x 10 k Ω resistor |
| Wire stripper | 1 x 5,6 k Ω speaker |
| Long-nose pliers | 1 x LED |
| Breadboard | Connecting wires |

4.2.3 Procedure:

- (a) Build the circuit in FIGURE 4.2.3 on the breadboard.
 Connect channel 1 of the oscilloscope across the capacitor.
 Connect channel 2 of the oscilloscope across the LED.
 Switch the circuit ON and observe.
 Answer the questions that follow.

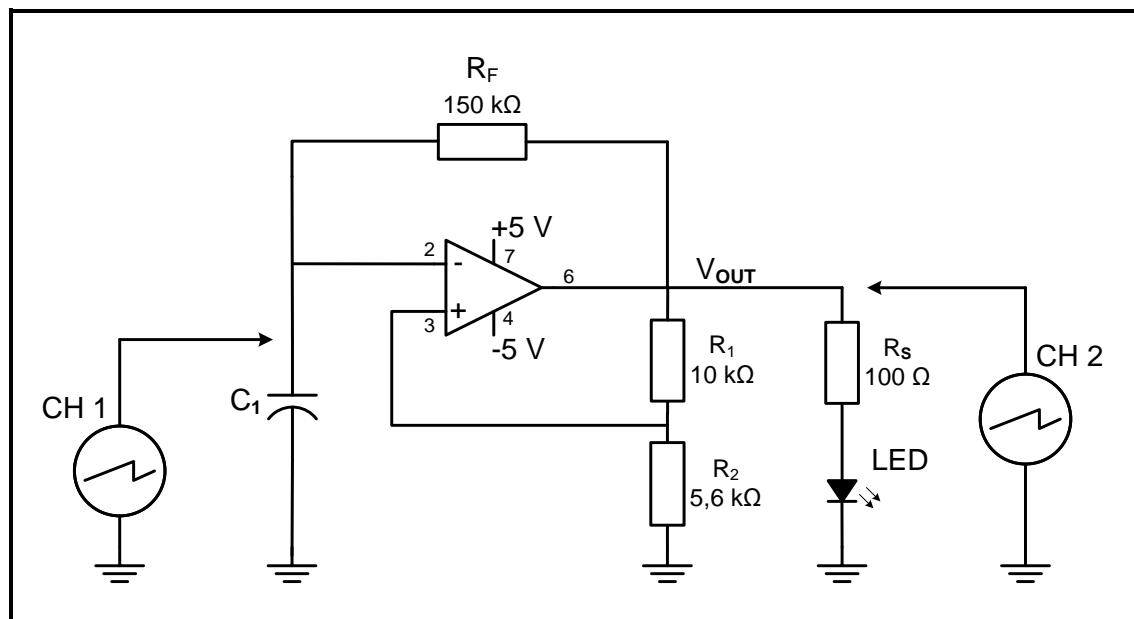**FIGURE 4.2.3: ASTABLE MULTIVIBRATOR**

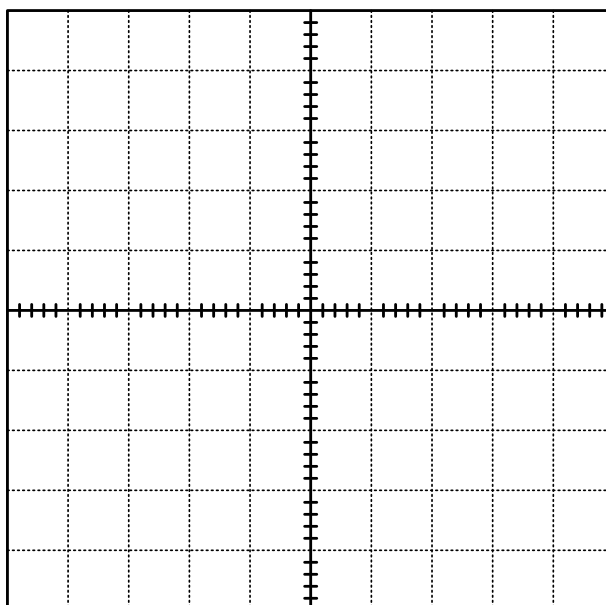- (b) Set the oscilloscope to display at least four complete cycles of the input and output waveforms with the amplitudes not smaller than 6 divisions. Draw the output waveforms on the oscillogram below.



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

NOTE: 1 mark for each correct waveform (i/p and o/p) (2)
1 mark for each correct oscilloscope setting (3)

(5)


- (c) Make use of the oscilloscope settings and determine the frequency of the output signal.

Output frequency

(2)

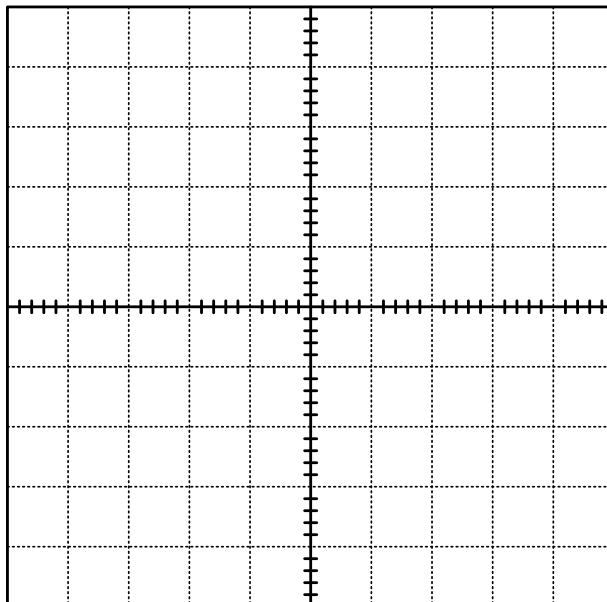- (d) Change the value of C_1 to $1\ \mu\text{F}$ and observe. Draw the output waveforms on the oscillogram below.

NOTE: Keep the oscilloscope setting the same as in (b).



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

NOTE: 1 mark for each correct waveform (i/p and o/p) (2) (2)

- (e) Make use of the oscilloscope settings and determine the frequency of the output signal.

Output frequency

(2)

- (f) Explain how an increase in the value of C_1 affects the frequency of the circuit.

(2)

- (g) Name TWO components other than C_1 that affect the frequency of the circuit.

(2)

Theory Simulation 2A (15)

FACET SHEET FOR SIMULATION 2A

| Task description | Mark allocation (tick the appropriate level next to the task indicated) | | | | Allocation of marks |
|--|---|--|---|---|--|
| | Competent after reassessment of certain parts of the task | Not yet competent after reassessment of certain/all parts of the task | Competent | Outstanding (Highly competent) | |
| Building the astable multivibrator using 741 IC | The learner was given opportunities to rebuild the circuit after the teacher intervened in identifying and rectifying more mistakes. (1) | The learner was given an opportunity to rebuild part of the circuit after the teacher intervened in identifying and rectifying a few mistakes. (2–3) | The learner correctly built the circuit without the guidance of the teacher. (4–5) | The learner correctly built the circuit without the guidance of the teacher and went beyond expectations and with high proficiency. (6) | $\overline{6}$ |
| Safety aspects | The learner was timeously reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (0) | The learner was sometimes reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (1) | The learner applied safety rules, regulation and correct procedure when using tools and instruments to wire the circuits without being reminded by the teacher. (2) | | $\overline{2}$ |
| Attitude/ Behaviour/ Conduct | The learner was reluctant to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice even after being cautioned/reprimanded. (0) | The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (1) | The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (2) | | $\overline{2}$ |
| Rubric Theory Total Simulation 2A | | | | | /10 + /10 = /25 |

Simulation 2B: Op-amp integrator using 741 IC**4.2.4 Purpose:**

- To build the integrator circuit in FIGURE 4.2.6 using a 741 op amp and displaying the input and output waveforms on an oscilloscope
- To investigate the effect of the R_F to R_1 ratio on the trigger voltage and output of the circuit

4.2.5 Required resources:

| TOOLS/INSTRUMENTS | MATERIALS |
|-------------------------------|----------------------------------|
| Function generator | 1 x LM741 op amp |
| Dual-trace oscilloscope | 1 x 100 k Ω resistor |
| +9 V 0 V -9 V DC power supply | 1 x 10 k Ω resistor |
| Side cutters | 1 x 0,01 μ F capacitor (103) |
| Wire stripper | 1 x 1 nF capacitor (102) |
| Calculator | Connecting wires |

4.2.6 Procedure:

- Set the dual voltage power supply to +9 V/-9 V.
- Set the function generator to deliver a 2 VP-P 1 kHz square wave.
- Build the circuit in FIGURE 4.2.6(a) on your experiment board and connect it to the supply and input.
- Connect channel 1 of the oscilloscope across the input to display at least TWO complete cycles.
- Connect channel 2 of the oscilloscope across the output to display at least TWO complete cycles.
- Ensure that the V/div settings for channel 1 and channel 2 are set so that the waveforms are at least 2/3rd of the screen.
- Set the T/div setting to display at least TWO complete cycles of the input and output.
- Disconnect the function generator and replace capacitor C1 as indicated.
- After replacing capacitor C1 repeat bullets 4 and 5 above.
- Answer the questions and draw the input and output waveforms.

- (a) Build the circuit in FIGURE 4.2.6(a) on the experiment board.


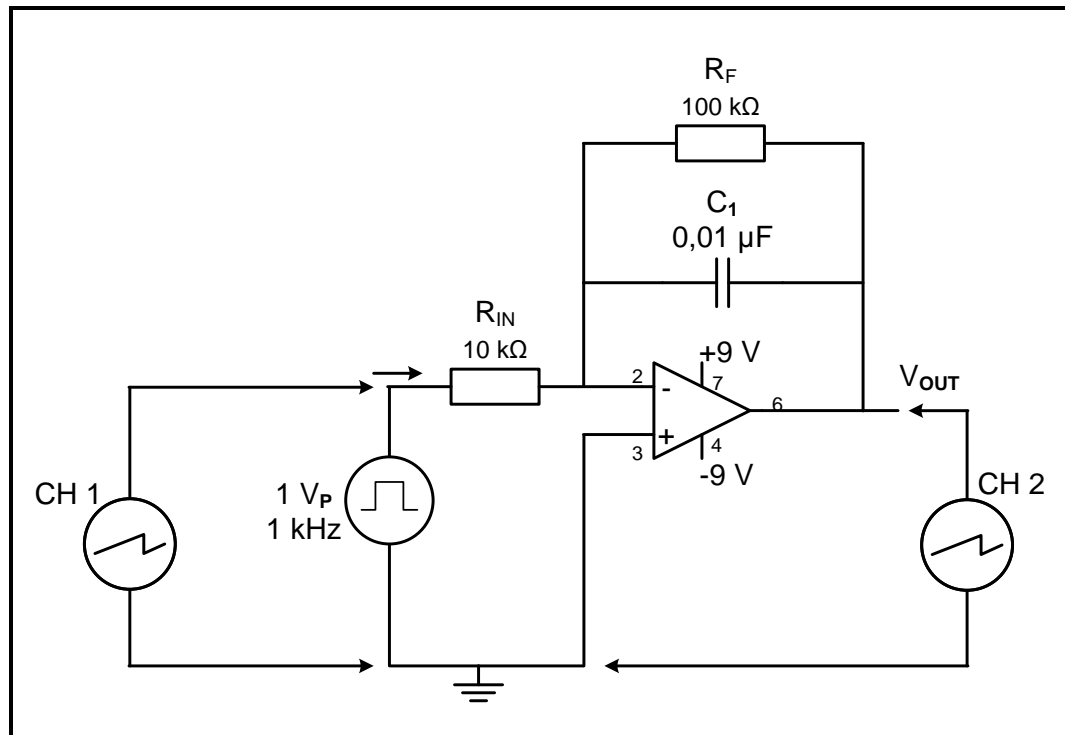


FIGURE 4.2.6(a): 741 OP-AMP INTEGRATOR CIRCUIT

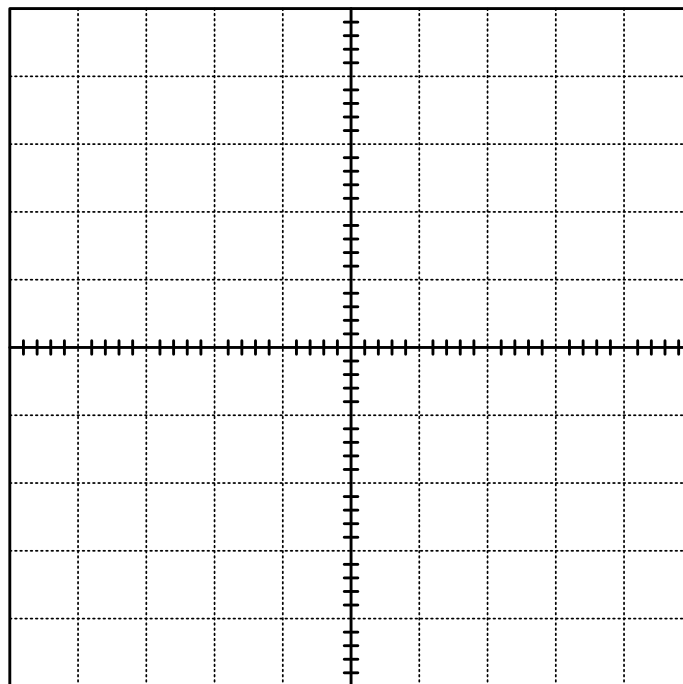- (b) Draw and label the input waveforms from pin 2 and pin 6 on the oscilloscope grid below.

NOTE: Set the oscilloscope to display at least 2 complete cycles.



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

NOTE: 1 mark for each correct waveform = 2
1 mark for each correct oscilloscope setting = 3


(5)

- (c) Explain the relationship between the input and the output waveforms with reference to the polarity, slope, pulse width and shape.

(3)

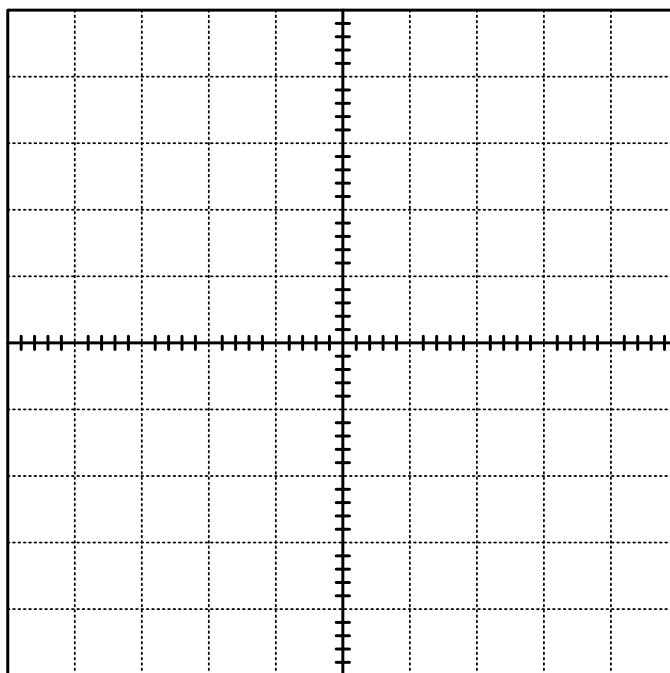- (d) Replace capacitor C_1 with a 1 nF capacitor and observe. Draw the input and output waveforms on the oscilloscope grid below.

NOTE: Keep the oscilloscope setting the same as in QUESTION 4.3.6 (b).



CH 1 V/div: _____

CH 2 V/div: _____

Time/div: _____

NOTE: 1 mark for each correct waveform = 2

Oscilloscope settings remain the same (no marks awarded)

(2)

- (e) Name ONE component other than C_1 responsible for the slope of the output signal.

(2)

- (f) Compare the shape of the output waveform on the oscilloscope for QUESTION 4.3.6 (d) above to the output waveform for QUESTION 4.3.6 (b) and write down your findings.

(

(4)

Theory Simulation 2B (10)

FACET SHEET FOR SIMULATION 2B

| Task description | Mark allocation (tick the appropriate level next to the task indicated) | | | | Allocation of marks |
|---|---|--|---|---|---|
| | Competent after reassessment of certain parts of the task | Not yet competent after reassessment of certain/all parts of the task | Competent | Outstanding (Highly competent) | |
| Building the astable op-amp by using a 741 IC | The learner was given opportunities to rebuild the circuit after the teacher intervened in identifying and rectifying more mistakes. (1) | The learner was given an opportunity to rebuild part of the circuit after the teacher intervened in identifying and rectifying a few mistakes. (2–3) | The learner correctly built the circuit without the guidance of the teacher. (4–5) | The learner correctly built the circuit without the guidance of the teacher and went beyond expectations and with high proficiency. (6) | $\overline{6}$ |
| Safety aspects | The learner was timeously reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (0) | The learner was sometimes reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (1) | The learner applied safety rules, regulation and correct procedure when using tools and instruments to wire the circuits without being reminded by the teacher. (2) | | $\overline{2}$ |
| Attitude/ Behaviour/ Conduct | The learner was reluctant to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice even after being cautioned/reprimanded. (0) | The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (1) | The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (2) | | $\overline{2}$ |
| Rubric Theory Total Simulation 2B Total Simulation 2A TOTAL: | | | | | + /10 = /15 + /25 = /25 = /50 |

4.3 Simulation 3: Connecting a 7-segment display to a 4-bit BCD 7-segment driver

| | | |
|------------------------|-----------------------|---|
| Name of learner: _____ | | Mark <div style="border: 1px solid black; padding: 5px; display: inline-block; width: 100px; text-align: center;">50</div> |
| Class: _____ | Date completed: _____ | |
| Date Assessed: _____ | | Assessor Signature: _____ |
| Date Moderated: _____ | | Moderator Signature: _____ |

4.3.1 Purpose:


- To connect a 7-segment display to a 4-bit BCD 7-segment display driver
- To observe the output on the 7-segment display after entering different digital inputs

4.3.2 Required resources:

| TOOLS/INSTRUMENTS | MATERIALS |
|--------------------------|--|
| Analogue/Digital trainer | 7 x 390 Ω to 750 Ω resistors |
| Breadboard | 4 x 1k resistors |
| Variable DC power supply | CD4511 IC |
| Side cutters | 4 x SPST switches |
| Breadboard wire | 7-segment display |

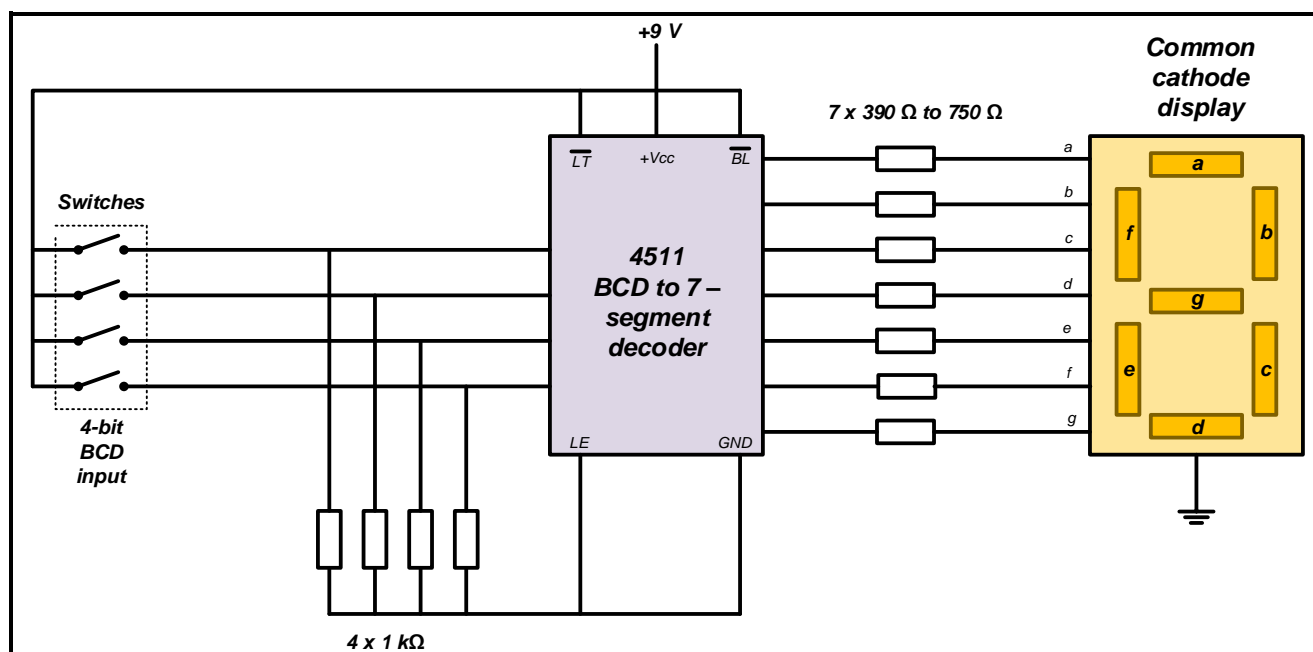4.3.3 Activity 3A

Connect the circuit as in the circuit given below.



FACET SHEET FOR SIMULATION 3

| Task description | Mark allocation (tick the appropriate level next to the task indicated) | | | | Allocation of marks |
|---|---|---|--|--|---------------------|
| | Competent after reassessment of certain parts of the task | Not yet competent after reassessment of certain/all parts of the task | Competent | Outstanding (Highly competent) | |
| Building the 7-segment display to a 4-bit BCD 7-segment display driver | The learner was given opportunities to rebuild the circuit after the teacher intervened in identifying and rectifying more mistakes. (1) | The learner was given an opportunity to rebuild part of the circuit after the teacher intervened in identifying and rectifying a few mistakes. (2-3) | The learner correctly built the circuit without the guidance of the teacher. (4-5) | The learner correctly built the circuit without the guidance of the teacher and went beyond expectations and with high proficiency. (6) | <u>6</u> |
| Safety aspects | The learner was timeously reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (1) | The learner was sometimes reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (2) | The learner applied safety rules, regulation and correct procedure when using tools and instruments to wire the circuits without being reminded by the teacher. (3) | | <u>3</u> |
| Hand tools | Used hand tools correctly (1) | | | | <u>1</u> |
| Preparation for insertion of components into breadboard | Checked the datasheet on the ICs (1) | Set supply voltage correct at +9 V (2) | | | <u>2</u> |
| Correct connection on breadboard – nodes and polarity | 8 nodes for correct connection of CD4511 IC (8) | 15 nodes for correct connection of CD4511 IC and the 7-segment display (15) | 20 nodes for correct connection of CD4511 IC and the 7-segment display (20) | | <u>20</u> |
| Attitude/ Behaviour/ Conduct | The learner was reluctant to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice even after being cautioned/ reprimanded. (0) | The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (1-2) | The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (3) | | <u>3</u> |
| Rubric | | | | | /35 |

Activity 3B

Conduct the following steps and answer the questions in the spaces provided.

| STEP | INPUTS | 7-SEGMENT DISPLAY |
|------|---|-------------------|
| (a) | Which segments on the 7-segment display will illuminate if the binary number 0111 is fed into the inputs? | |
| (b) | Which segments on the 7-segment display will illuminate if the binary number 1000 is fed into the inputs? | |
| (c) | Which segments on the 7-segment display will illuminate if the binary number 1001 is fed into the inputs? | |
| (d) | Which segments on the 7-segment display will illuminate when C and D are switched ON? | |
| (e) | Which segments on the 7-segment display will illuminate when B and D are switched ON? | |

(3)

(3)

(3)

(3)

(3)

[15]**Activity 3A: (35)****Activity 3B: (15)****TOTAL Simulation 3: [50]**

4.4 Simulation 4: S-R flip-flop circuit and PICAXE

| | | |
|------------------------|-----------------------|--|
| Name of learner: _____ | | Mark <div style="border: 1px solid black; width: 100px; height: 30px; margin: 0 auto; text-align: center; line-height: 30px;">50</div> |
| Class: _____ | Date completed: _____ | |
| Date Assessed: _____ | | Assessor Signature: _____ |
| Date Moderated: _____ | | Moderator Signature: _____ |

Simulation 4A: S-R flip-flop circuit**4.4.1 Purpose:**

- To demonstrate the operation of the S-R latching
- To connect the circuit on the breadboard
- To observe the change in the outputs after entering different inputs on S and R

4.4.2 Required resources:

| TOOLS/INSTRUMENTS | MATERIALS |
|-----------------------------|---------------------------|
| Breadboard | SN74HC00N IC |
| Voltmeter | Toggle switches x 4 |
| Dual power supply 9 V 0–9 V | 1 kΩ resistor x 3 |
| Dual power supply 5 V 0–5 V | 10 kΩ resistor x 1 |
| Side cutters | 1 x red and 1 x green LED |
| Wire stripper | Connecting wires |

4.4.3 Circuit diagram

Connect the circuit as in FIGURE 4.3.3 on the breadboard. After you switch on the circuit, press the reset switch. You will be assessed with the rubric that follows.

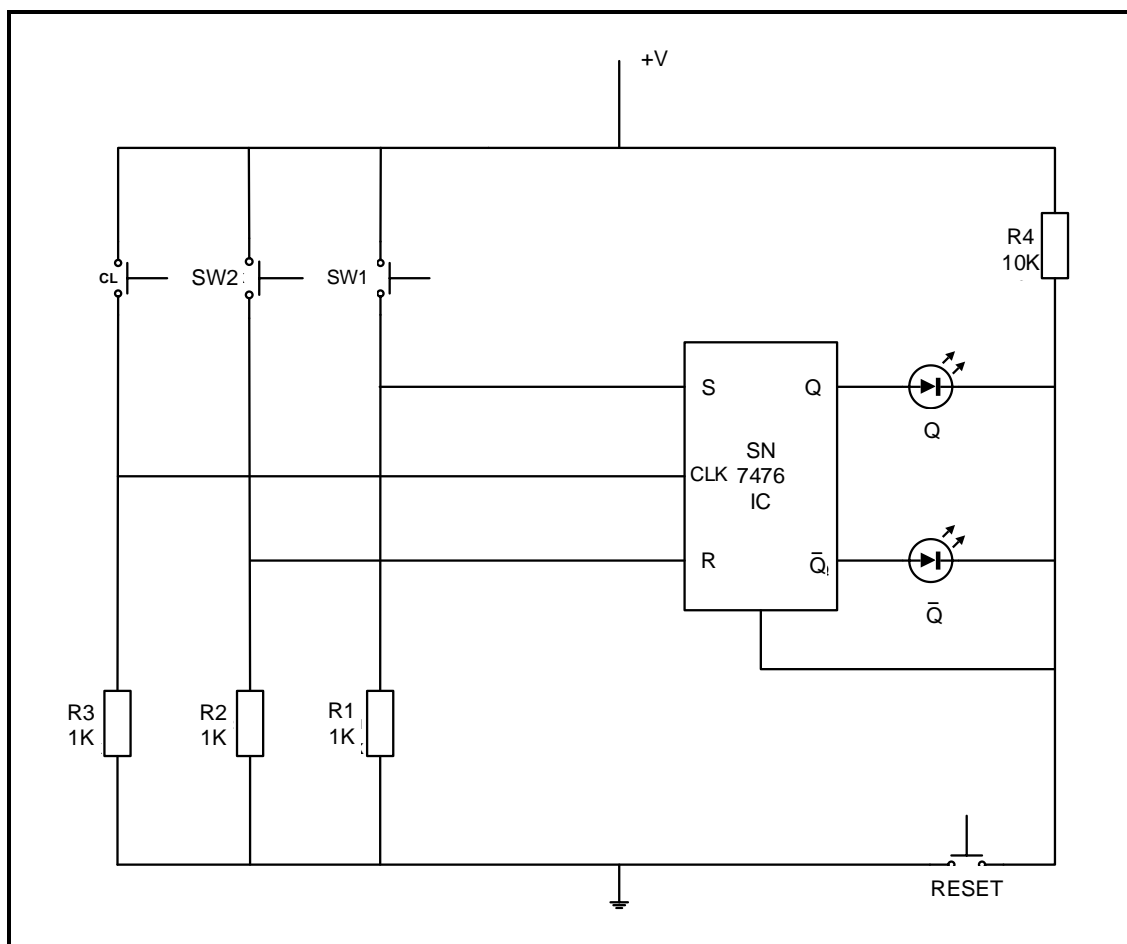


FIGURE 4.3.3: CIRCUIT DIAGRAM OF AN S-R FLIP-FLOP

4.4.4 Procedure:

- Apply logic 0 to S and R input and 1 to the CLK, and observe the Q and \bar{Q} output.
- Apply logic 0 to S and logic 1 to R input and 1 to the CLK, and observe the Q and \bar{Q} output.
- Apply logic 1 to S and logic 0 to R input and 1 to the CLK, and observe the Q and \bar{Q} output.
- Apply logic 1 to S and logic 1 to R input and 1 to the CLK, and observe the Q and \bar{Q} output.
- Apply logic 0 to S and R input and 0 to the CLK, and observe the Q and \bar{Q} output.
- Apply logic 0 to S and logic 1 to R input and 0 to the CLK, and observe the Q and \bar{Q} output.
- Apply logic 1 to S and logic 0 to R input and 0 to the CLK, and observe the Q and \bar{Q} output.
- Apply logic 1 to S and logic 1 to R input and 0 to the CLK, and observe the Q and \bar{Q} output.

4.4.5 Observations:

- (a) Press the S and R switches. Write down your observation.

 (1)

- (b) Press the clock and S switch simultaneously. Write down your observation.

 (1)

- 4.4.6**
- From the observation in QUESTION 4.4.4, complete the truth table of the circuit you built.

| INPUTS | | | OUTPUTS | |
|--------|-----|------|---------|-----------|
| S | R | CL | Q | \bar{Q} |
| 0 | 0 | 0 | | |
| 0 | 1 | 0 | | |
| 1 | 0 | 0 | | |
| 1 | 1 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 1 | | |

(8)

4.4.7 Housekeeping

When you have obtained all the measurements and the teacher has validated all your answers, you must tidy up your workplace as part of the safety in the workshop. You will be assessed on housekeeping with the rubric below.

FACET SHEET FOR SIMULATION 4A

| Task description | Mark allocation (tick the appropriate level next to the task indicated) | | | | Allocation of marks |
|--|---|--|---|---|-----------------------|
| | Competent after reassessment of certain parts of the task | Not yet competent after reassessment of certain/all parts of the task | Competent | Outstanding (Highly competent) | |
| Building the S-RK flip-flop circuit | The learner was given opportunities to rebuild the circuit after the teacher intervened in identifying and rectifying more mistakes. (1) | The learner was given an opportunity to rebuild part of the circuit after the teacher intervened in identifying and rectifying a few mistakes. (2–3) | The learner correctly built the circuit without the guidance of the teacher. (4–5) | The learner correctly built the circuit without the guidance of the teacher and went beyond expectations and with high proficiency. (6–9) | <u>9</u> |
| Safety aspects | The learner was timeously reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (1) | The learner was sometimes reminded to apply safety rules, regulation and correct procedure when using tools and instruments. (2) | The learner applied safety rules, regulation and correct procedure when using tools and instruments to wire the circuits without being reminded by the teacher. (3) | | <u>3</u> |
| Attitude/ Behaviour/ Conduct | The learner was reluctant to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice even after being cautioned/reprimanded. (0) | The learner was reluctant to a certain degree to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (1–2) | The learner demonstrated willingness to work, cooperate, take responsibility of their own conduct and follow instructional, regulation and workshop practice. (3) | | <u>3</u> |
| Rubric Theory Total Simulation 4A | | | | | /15 + /10 = /25 |

Simulation 4B: PICAXE**4.4.8 Purpose:**

- To test knowledge of flow diagrams and PICAXE

Study the scenario below and design a flow diagram for the PICAXE school access control system.

SCENARIO:

Your school has limited parking for visitors who enters the school. Design and simulate a PICAXE school access control system for 15 cars to enter the parking lot when a parking space is available. There will be an entrance and exit on each end of the parking lot.

This system will be set up at the single entrance and exit at your school.

This system will enable access control for student safety.

It will consist of a red light and a green light.

The green light informs the person entering the parking lot that a space is available.

The system will use two digital sensors.

Sensor 1 will increase the count when visitors enter the parking lot.

Sensor 2 will decrease the count when visitors exit the parking lot.


Sensor 1 will increase the count to 15 cars inside the parking lot and the program will toggle to the red light. This will indicate a full parking lot.

Sensor 2 will reduce the count when visitors leave. The green light switches on if the count is less than 15; therefore, indicating that a visitor may drive in to the parking lot.

FACET SHEET FOR SIMULATION 4B

| Task description | Mark allocation (tick the appropriate level next to the task indicated) | | | | Allocation of marks |
|--|---|---|---|--|--------------------------------|
| | Competent after reassessment of certain parts of the task | Not yet competent after reassessment of certain/all parts of the task | Competent | Outstanding (Highly competent) | |
| Inserting the Start/Stop element | | | Start element correctly placed (1) | Stop element correctly placed (1) | <u>1</u> |
| Inserting the decision element | | | Two decision elements correctly placed (1) | Four decision elements correctly placed (2) | <u>2</u> |
| Inserting the process element | No process element correctly placed (0) | | One process element correctly placed (1) | Three process elements correctly placed (2) | <u>2</u> |
| Inserting the data elements | One data element correctly placed (1) | Two data elements correctly placed (2) | Three data elements correctly placed (3) | Four data elements correctly placed (4–5) | <u>5</u> |
| Inserting the flow lines correctly | 0%–25% of flow lines correctly placed (0–2) | 25%–50% of flow lines correctly placed (3–4) | 50%–75% of flow lines correctly placed (5–6) | All flow lines correctly placed (9) | <u>9</u> |
| Labelling of elements | 0–3 labels correctly placed (0–1) | 4–6 labels correctly placed (2–3) | 7–9 labels correctly placed (4–5) | All labels correctly placed (6) | <u>6</u> |
| Rubric Total Simulation 4A Total Simulation 4B TOTAL: | | | | | /25 = /25 + /25 = /50 |

5. SECTION B: DESIGN AND MAKE

| | |
|---|-------|
| Design and Make Project <div style="text-align: right; padding-right: 20px;">  </div> | |
| Time: January to August 2024 | |
| Learner Name: | _____ |
| School: | _____ |
| Class: | _____ |
| Title/Type of Project: _____ | |

INSTRUCTIONS

- This section is **COMPULSORY** for all learners.
- The teacher will choose a circuit for the project.
- Any project constructed must include at least (but is not limited to):
 - Seven components
 - A variety of components (both active and passive)
 - PCB making in some form
 - Soldering
 - An enclosure with a switch and protection
- The checklist below must be used to ensure that all the required tasks for the PAT have been completed.

PAT CHECKLIST

The learner **MUST** fill in this checklist **BEFORE** marking of the section takes place.

| NO. | DESCRIPTION | TICK (☑) | |
|-------------------------|--|--------------------------|--------------------------|
| | | NO | YES |
| Design and Make: Part 1 | | | |
| 1. | Circuit diagram drawn | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. | Circuit description filled in | <input type="checkbox"/> | <input type="checkbox"/> |
| 3. | Component list completed | <input type="checkbox"/> | <input type="checkbox"/> |
| 4. | Tools list for circuitry populated | <input type="checkbox"/> | <input type="checkbox"/> |
| 5. | Measuring instrument list filled in | <input type="checkbox"/> | <input type="checkbox"/> |
| Design and Make: Part 2 | | | |
| 1. | Enclosure design completed and included in the file | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. | Unique name written down and on the enclosure | <input type="checkbox"/> | <input type="checkbox"/> |
| 3. | Logo designed and on the enclosure | <input type="checkbox"/> | <input type="checkbox"/> |
| Miscellaneous | | | |
| 1. | Enclosure included in the project | <input type="checkbox"/> | <input type="checkbox"/> |
| 2. | Enclosure prepared and drilled according to the design | <input type="checkbox"/> | <input type="checkbox"/> |
| 3. | Enclosure finished off and completed with name and logo | <input type="checkbox"/> | <input type="checkbox"/> |
| 4. | PCB securely mounted in the enclosure using acceptable techniques | <input type="checkbox"/> | <input type="checkbox"/> |
| 5. | Circuit inside the enclosure accessible | <input type="checkbox"/> | <input type="checkbox"/> |
| 6. | Internal wiring neat and ready for inspection | <input type="checkbox"/> | <input type="checkbox"/> |
| 7. | File and project completed and ready for moderation at the workshop/room | <input type="checkbox"/> | <input type="checkbox"/> |

5.1 Design and Make: Part 1

5.1.1 Circuit diagram

Draw a circuit diagram of the project chosen and paste it on the next page.

5.1.2 Project: Description of operation

Use the space below to describe how the project operates. Do research and use your own words.

[illegible]

5.2 Assessment of the Design and Make Phase: Part 1

| NO. | FACET DESCRIPTION | Mark | Achieved mark |
|---------------------------------|---|-----------|---------------|
| Circuit Diagram | | | |
| 1. | The circuit diagram was drawn using <ul style="list-style-type: none"> EGD equipment (4) CAD/Any electronic design software (6) | 6 | |
| 2. | The circuit diagram was drawn using correct symbols. | 3 | |
| 3. | The circuit diagram has all labels, e.g. R1, C1, Tr1 | 3 | |
| 4. | The circuit diagram has all component values, e.g. 100 Ω , 220 μF | 4 | |
| 5. | The circuit diagram has a name/title. | 2 | |
| 6. | The circuit diagram has a frame and title block. | 2 | |
| | | | |
| | Circuit Diagram Subtotal: | 20 | |
| | | | |
| Component List | | | |
| 7. | Labels correlate with circuit diagram. | 2 | |
| 8. | Description and values correlate with circuit diagram. | 2 | |
| 9. | Quantities are correct. | 1 | |
| | | | |
| | Component List Subtotal: | 5 | |
| | | | |
| Description of Operation | | | |
| 10. | Basic function of the circuit is described correctly. The purpose/role/function of each component is described. | 11 | |
| 11. | All subcircuits in the circuit diagram and component list are included in the description. | 4 | |
| 12. | Purposes of subcircuits in the circuit diagram are described correctly. | 5 | |
| 13. | Learner used own interpretation and did not copy from another source verbatim. | 3 | |
| 14. | Sources are acknowledged. | 2 | |
| | | | |
| | Description of Operation Subtotal: | 25 | |
| | | | |
| Tools/Instrument List | | | |
| 15. | The tools/instrument list has been completed. | 4 | |
| 16. | The tools/instruments listed all have a purpose for being used. | 1 | |
| | | | |
| | Tools/Instrument List Subtotal: | 5 | |

| NO. | FACET DESCRIPTION | Mark | Achieved mark |
|------------------------------------|---|-----------|---------------|
| Circuit Board Manufacturing | | | |
| 17. | Transfer of the PCB design onto the blank board is correct. Not over-exposed or under-exposed. | 5 | |
| 18. | Circuit board is etched neatly according to the PCB design. | 10 | |
| 19. | The learner's name is etched onto the circuit design. | 4 | |
| 20. | All burrs are removed. | 2 | |
| 21. | Axial and radial components are placed neatly and flush with the board. | 5 | |
| 22. | Component orientation are aligned between similar components (e.g. the gold band of all resistors are placed on the same side). | 2 | |
| 23. | Soldered components – leads are cut off, flush and neat on the solder side. | 5 | |
| 24. | More than 60% of the solder joints are shiny (not dry joints). | 5 | |
| 25. | Wire insulation is stripped to the correct length (no extra copper showing). | 3 | |
| 26. | Wiring is long enough to allow for dismantling and inspection. | 2 | |
| 27. | Wiring is wrapped neatly. | 2 | |
| 28. | A power switch is included and fitted to the enclosure. | 2 | |
| 29. | A fuse/protection is included and fitted correctly where applicable. | 2 | |
| 30. | Wiring entering/exiting the enclosure is provided with a grommet/applicable fittings/sockets where applicable. | 2 | |
| 31. | Batteries/Transformer is mounted using a battery housing/mounting bracket and battery clip (NO double-sided tape). | 2 | |
| 32. | The project has a pilot light/LED installed in the enclosure showing when the circuit is operational. LED is mounted with a grommet or applicable fitting. (Switch is on – must go out when fuse is blown.) | 2 | |
| 33. | The project is fully operational and commissioned/installed in the enclosure. | 10 | |
| | | | |
| | Circuit Board Manufacturing Subtotal: | 65 | |
| | | | |
| | Circuit Diagram Subtotal: | 20 | |
| | Component List Subtotal: | 5 | |
| | Description of Operation Subtotal: | 25 | |
| | Tools/Instrument List Subtotal: | 5 | |
| | Circuit Board Manufacturing Subtotal: | 65 | |

| | |
|---|--|
| TOTAL (PART 1 = 120 marks) | |
|---|--|

NOTE: In projects where facets are not applicable, the projects should be marked and the totals adjusted accordingly.

5.3 Design and Make: Part 2**5.3.1 Enclosure design**

- Design an enclosure for your project.
- NO FREEHAND DRAWINGS.
- Draw using EGD equipment **OR** use a CAD program.
- Draw in first-angle orthographic projection.
- Add your drawings after this page.
- Use colour to enhance your drawing.

5.3.2 Manufacture the enclosure neatly according to your design.

You may use pre-cut panels from metal, wood and/or Perspex/Plexiglas.

You must, however, construct/assemble these parts.

Injection moulded enclosures are also acceptable. It is important that your enclosure and the placement of the parts align with your design.

5.3.3 Choose a name for your device.

Write down the name of the device below.

5.3.4 Design a unique logo for your device, as well as a specification plate and attach it after this page.

5.4 Assessment of the Design and Make Phase: Part 2

| NO. | FACET DESCRIPTION | Mark | Achieved mark |
|--------------------------------|---|-----------|---------------|
| Enclosure Design | | | |
| 1. | Enclosure design is included in first-angle orthographic projection. | 2 | |
| 2. | Drawn design includes a title box and page border. | 1 | |
| 3. | Isometric drawing included additionally. | 2 | |
| 4. | Dimensions are included. | 2 | |
| 5. | The name of the device is written in the PAT document. | 1 | |
| 6. | The logo design and specification plate design is in the PAT document. | 2 | |
| | | | |
| | Enclosure Design Subtotal: | 10 | |
| Enclosure Manufacturing | | | |
| 7. | Enclosure matches the design. Dimensions and placement correlate. | 1 | |
| 8. | Name of the device is attached on the enclosure. | 1 | |
| 9. | The logo design is attached on the enclosure. | 2 | |
| 10. | The logo design on the enclosure is durable and not merely a paper pasted on the enclosure (painted/used decoupage/screen printed/sublimation printed). | 2 | |
| 11. | The enclosure is manufactured from scratch/pre-cut parts. Does NOT include: cardboard, paper, margarine container Does include: sheet metal, Perspex, Plexiglas, wood, glass and other raw materials, injection-moulded plastic boxes | 5 | |
| 12. | Holes/Cut-outs in the enclosure are made with the appropriate tools. | 3 | |
| 13. | Specification plate with the learner's name, operating voltage, fuse rating and additional information on the project. | 2 | |
| 14. | Enclosure is neatly prepared, painted and aesthetically pleasing. | 2 | |
| 15. | The circuit board is mounted using appropriate methods inside the enclosure. (NO double-sided tape, Prestik, glue, chewing gum, masking tape, etc.) | 2 | |
| | | | |
| | Enclosure Manufacturing Subtotal: | 20 | |

| | |
|--|--|
| TOTAL (PART 2 = 30 marks) | |
|--|--|

6. PROJECTS


6.1 Practical Project 6.1: Sound-to-light Controller


This sound-controlled light circuit design is used to control the brightness of the lights attached to it in sync with the sound that is being captured by its microphone. This electronic circuit design is very common in disco houses, bars, parties, etc.

Usually, sound-controlled lights are just connected in parallel with the loudspeakers. This configuration has two disadvantages: a very power amplifier can destroy the lights, or worse, a defective light can destroy the amp. This problem is avoided by the circuit by not connecting directly to the amp. Instead, it picks up the sound with its microphone.

The power-supply part is on the left of the electret microphone amplifier and the light controller part is on the right. The capacitors C2 and C3 are the capacitive voltage divider and reduces the power supply level. Diodes D1 and D2 rectify the positive swing of the AC voltage. The network composed of L1 and C1 protects the power line from voltage surges. In this circuit design, an electret microphone is being used. Take note that there are two types of electret mics. The first type has three pins for power, ground and output. The second type has only two pins. The second type is used for this circuit.

WARNING: Some parts in the circuit board are subject to lethal potential because the device is connected to 230 V AC. When plugging in the project, place it in a plastic or wooden box to prevent the circuit from shocking you. Avoid connecting this circuit to other appliances (e.g. to the output of an amplifier by means of a cable) because of the absence of a mains transformer. Use only the microphone in the main case to pick up the sound.

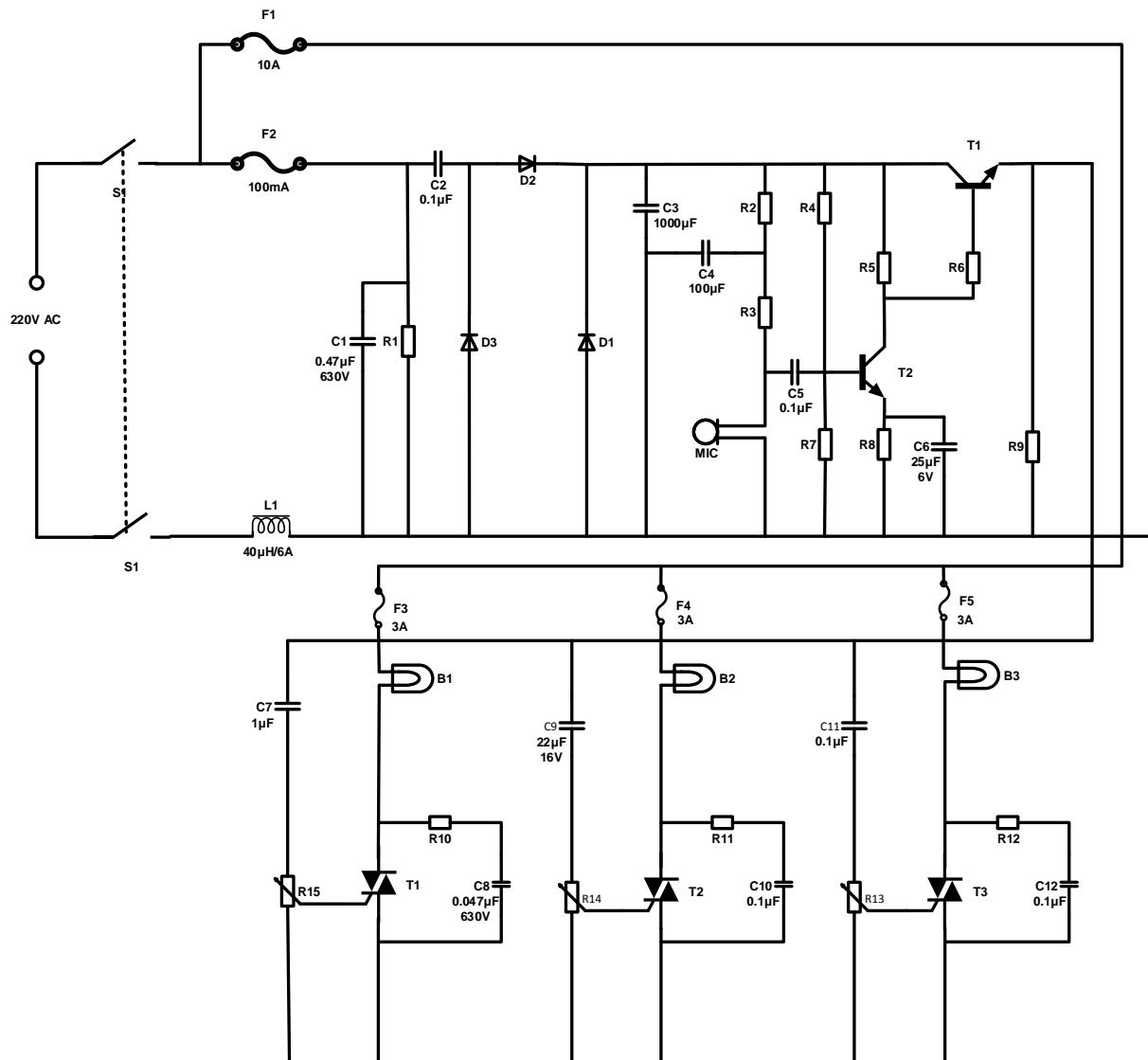

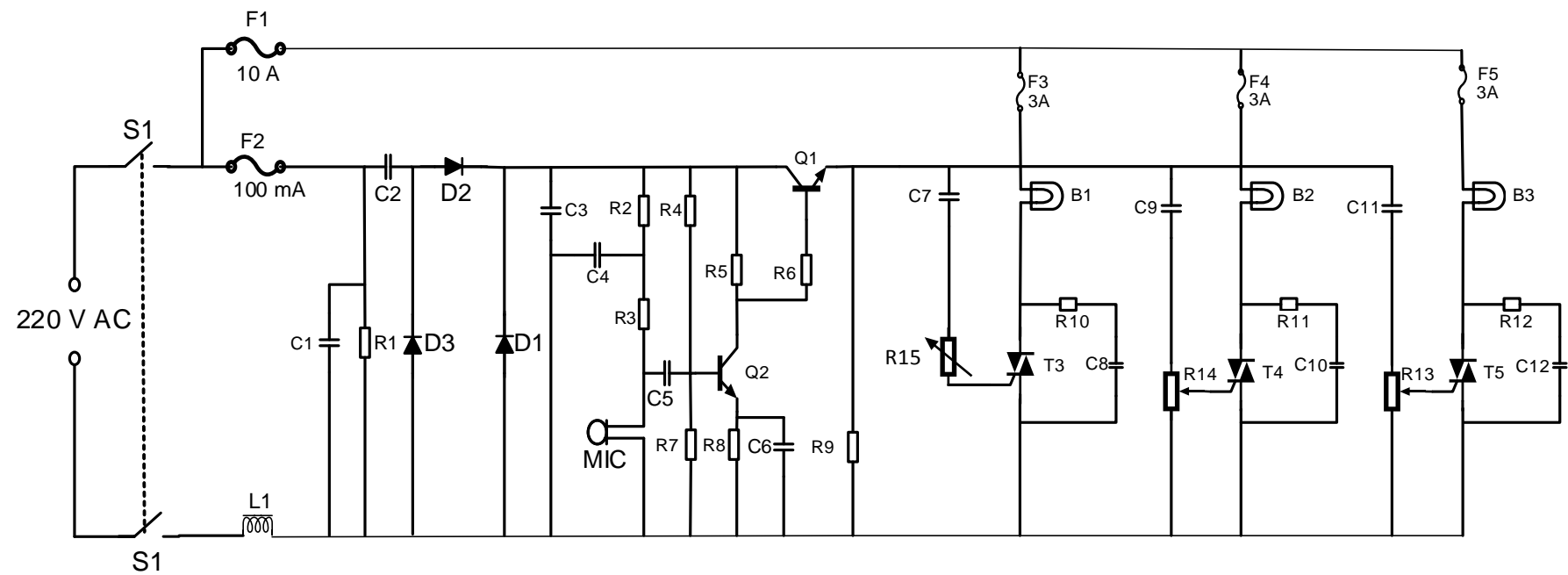

SOUND-TO-LIGHT CONTROLLER CIRCUIT

| COMPONENT LIST | | | |
|----------------|------------------------------------|-------------|---|
| R1 | 560 k Ω /1 W | C8, C10,C12 | 0,047 μ F |
| R2, R3 | 15 k Ω ¼ W | C9 | 22 μ F 16 V |
| R4 | 33 k Ω /¼ W | C11 | 47 μ F 16 V |
| R5, R6, R9 | 1 k Ω ¼ W | D1, D2 | 1N4004 |
| R7 | 18 k Ω ¼ W | D3 | 1N4742 12v/1 W |
| R8 | 560 Ω ¼ W | F1 | 10 A fuse 220 V |
| R10, R11, R12 | 100 k Ω | F2 | 100 mA fuse 220 V |
| R13, R14, R15 | 5 k Ω Pot | F3, F4, F5 | 220 V 3 A fuse |
| C1 | 0,47 μ F 630 V | L1 | 40 μ H 6 A 10-15 turns on a ferrite core |
| C2, C5 | 0,1 μ F/220 V | B1, B2, B3 | 60 W incandescent lamp |
| C3 | 1 000 μ F/16 V electrolytic | Mic | Low-impedance microphone |
| C4 | 100 μ F/16 V | S1A & S1B | Double-pole switch |
| C6 | 25 μ F/6 V | T1,T2 | BC 547 |
| C7 | 1 μ F 16 V | T3,T4,T5 | TIC 106 or BT 136 |

WARNING:

Some parts in the circuit board are subject to lethal potential because the device is connected to 230 V AC. When plugging in the project, place it in a plastic or wooden box to prevent the circuit from shocking you. Avoid connecting this circuit to other appliances (e.g. to the output of an amplifier by means of a cable) because of the absence of a mains transformer. Use only the microphone in the main case to pick up the sound.


6.2 Practical Project 6.2: Automatic Battery Charger with Battery-voltage Bar-graph Display

This automatic battery charger project is based on the National Semiconductor LM350 3 A adjustable regulator. It is designed to charge 12 V lead-acid batteries. When the switch SW1 is pushed, the output of the charger will go up to 14,5 V. The initial charging current is limited to 2 A. As the charge of the battery continues to rise, the charging current decreases to 150 mA and the output voltage is reduced to 12,5 V. At this stage the charging is terminated and the light-emitting diode lights up to indicate that the charging process has been completed.

The schematic diagram below shows how the various components are connected. The first part of the diagram shows how the DC power supply to LM350 is achieved. The combined use of varistor V1 and fuse F1 is to protect the circuit from overcurrent and power surge of the mains supply.

Transformer T1 is used to step down the input voltage from the mains to 16 V AC. Diode bridge DB and electrolytic capacitor E1 are used to rectify the AC voltage to DC voltage. This rectified DC power supply is fed into the input of the second circuit where LM350 and operational amplifier LM301A are used to control the charging current and voltage of the lead-acid battery. Once the charge is full, transistor Q1 will turn ON and LED L1 will be ON to indicate that the charging has been completed. A heat sink is attached to LM350 to transfer the heat generated from the regulator to the ambient.

This bar-graph LED-battery-level-indicator project is based on the LM3914 monolithic IC of the National Semiconductor that senses the voltage levels of the battery and drives the 10 light-emitting diodes based on the voltage level that is detected. It provides a linear analogue display output and has a pin that can be configured to display the output in moving dot or bar graph. The current driving the LEDs is regulated and programmable, hence limiting resistors are not required. The schematic diagram below shows how the various components are connected. Switch S1 is used to change the display type from moving dot to bar graph type. When S1 is ON, the display type is bar graph, but when it is OFF, the display changes to the moving dot type. R3 is used to set the lower limit of the display. Use a variable DC power supply and set the VBAT to 10,5 V. Adjust VR1 until the LED L1 turns ON. Next, set the VBAT to 15 V; adjust VR2 until all the LEDs turn ON (when S1 is ON).

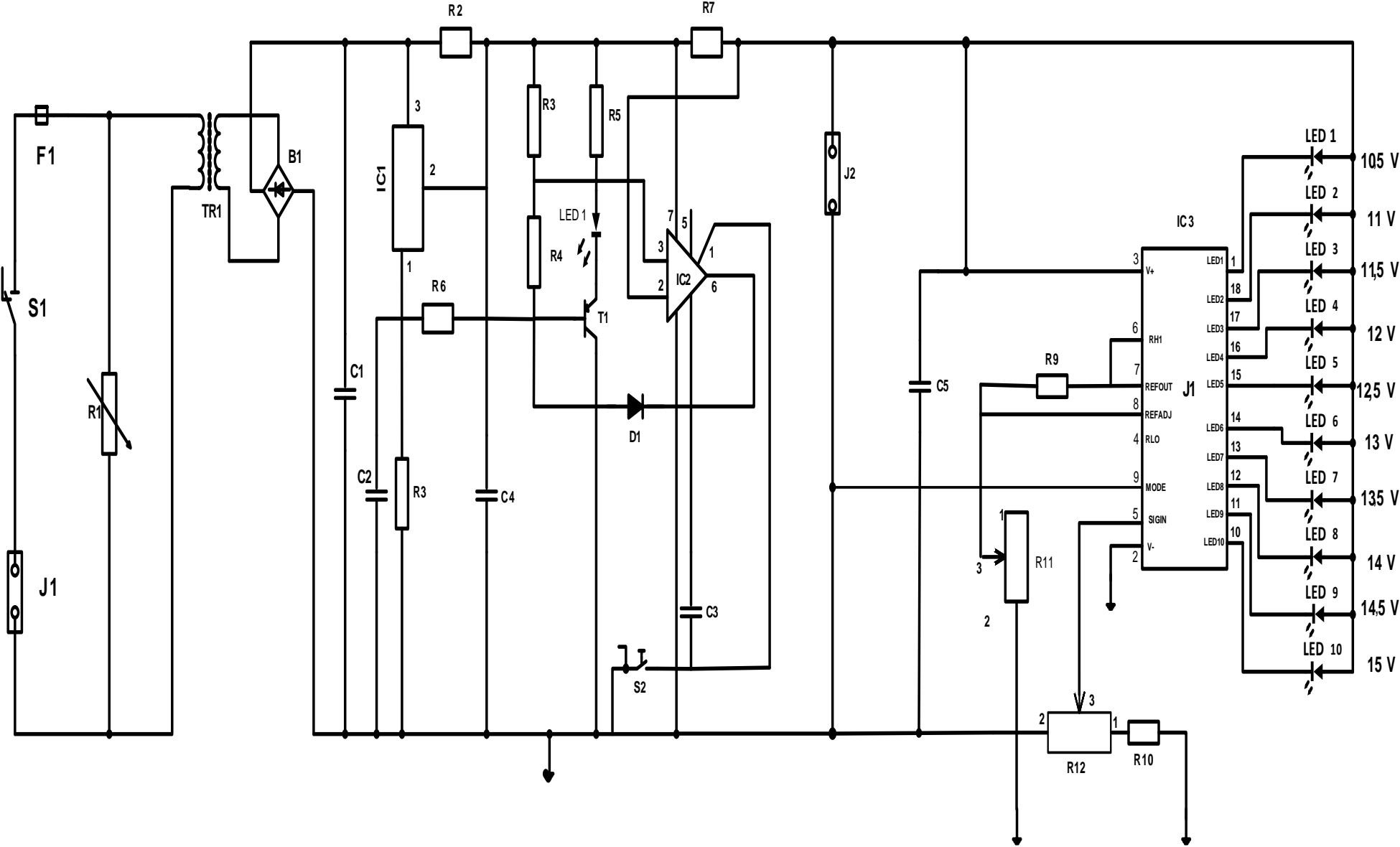

COMPONENT LIST

| | | | |
|-------------|---|-------|--|
| R1 | varistor 14 mm | B1 | 5 A diode bridge |
| R2 | 500 ohm, 5 W | C1 | 6 800 uF 35 V electrolytic capacitor (battery charger) |
| R3, R6 | 15 K ¼ W | C2 | 0,1 uF ceramic 104 |
| R4 | 230 ohm ¼ W | C3 | 1 nF ceramic 102 |
| R5 | 1k | C4 | 1 uF electrolytic 25 volt |
| R7 | 0,2 ohm, 5 W | D1 | 1N 4148 diode |
| R8 | 3k3 ¼ W | IC1 | LM350 16 volt positive voltage regulator |
| J1 | mains supply | IC2 | LM301 H operational amplifier |
| J2 | 12 V connector for battery/battery clamps | S1 | On/Off switch for mains voltage SPST toggle switch |
| F1 | 500 mA fast-blow fuse | S2 | push-to-make switch |
| TR1 | 240 V–16 V transformer 3 A (+/-50 VA) | LED 1 | red LED 5 mm |
| R9 | 1k2 ¼ W 5% | IC 3 | LM3914 N bar-graph display driver |
| R10 | 4k7 ¼ W 5% | C5 | 10 µF 25 volt electrolytic capacitor (bar-graph voltage indicator) |
| R11 | 5k potentiometer | T1 | PN2907 alternative (BC527 or BC 528) |
| LED 1,10 | red, | | |
| LED 4,5,6,7 | green | | |
| LED 2,3,8,9 | amber | | |
| R12 | 5k potentiometer | | |


6.3 Practical Project 6.3: Sine-wave Inverter Circuit Diagram

PLEASE NOTE: The sine-wave inverter has been included to keep up with the current load shedding trends. If this project is too expensive, the **SQUARE WAVE INVERTER** can be built. Schools can purchase one transformer and a set of batteries to demonstrate the workings of this project.

An inverter provides power backup for mains-based appliances in the event of a power failure. Most of the inverters available in the market have complicated circuit designs and are not very economical. Some of them produce a square-wave output, which is undesirable for inductive loads.

Here we designed a simple sine wave inverter circuit that produces 50Hz quasi-sine wave output using a single IC CD4047 and some discrete components, which makes it a very cost-effective solution.

| COMPONENT LIST | |
|---|---|
| SEMICONDUCTORS | |
| IC1 | CD4047 multivibrator |
| SCR1 | 2P4M SCR |
| T1 – T8 | IRF 250 MOSFET |
| T9 – T11 | BS548 NPN transistor |
| ZD1 | 5,1 V, 1W zener diode |
| ZD2 – ZD5 | 5,1 V zener diode |
| D1 – D6 | 1N4007 rectifier diode |
| LED1, LED2 | 5 mm LED |
| RESISTORS (all 0,25 W, \pm% carbon) | |
| R1 | 560 Ω |
| R2, R3 | 1,2 k Ω |
| R4,R5,R6, R8, R9, R11 | 1 k Ω |
| R12 | 2,2 k Ω |
| R7 | 220 Ω |
| R10 | 5,6 k Ω |
| VR1 | 470 k Ω pre-set |
| VR2 – VR4 | 10 k Ω pre-set |
| CAPACITORS | |
| C1 | 0,2 μ F, 100 V ceramic disk |
| C2,C3 | 100 μ F, 35 V electrolytic |
| C4 | 1000 μ F, 35 V electrolytic |
| C5-C7 | 0,47 μ F, 600 V polyester |
| MISCELLANEOUS | |
| PZ1 | Piezo Buzzer |
| S1 | SPST switch |
| X1 | 18-0-18V, 40 A primary to 0-230V-600 V secondary inverter transformer |
| BATT1, BATT2 | 12 V (Ah determined by the size transformer) |

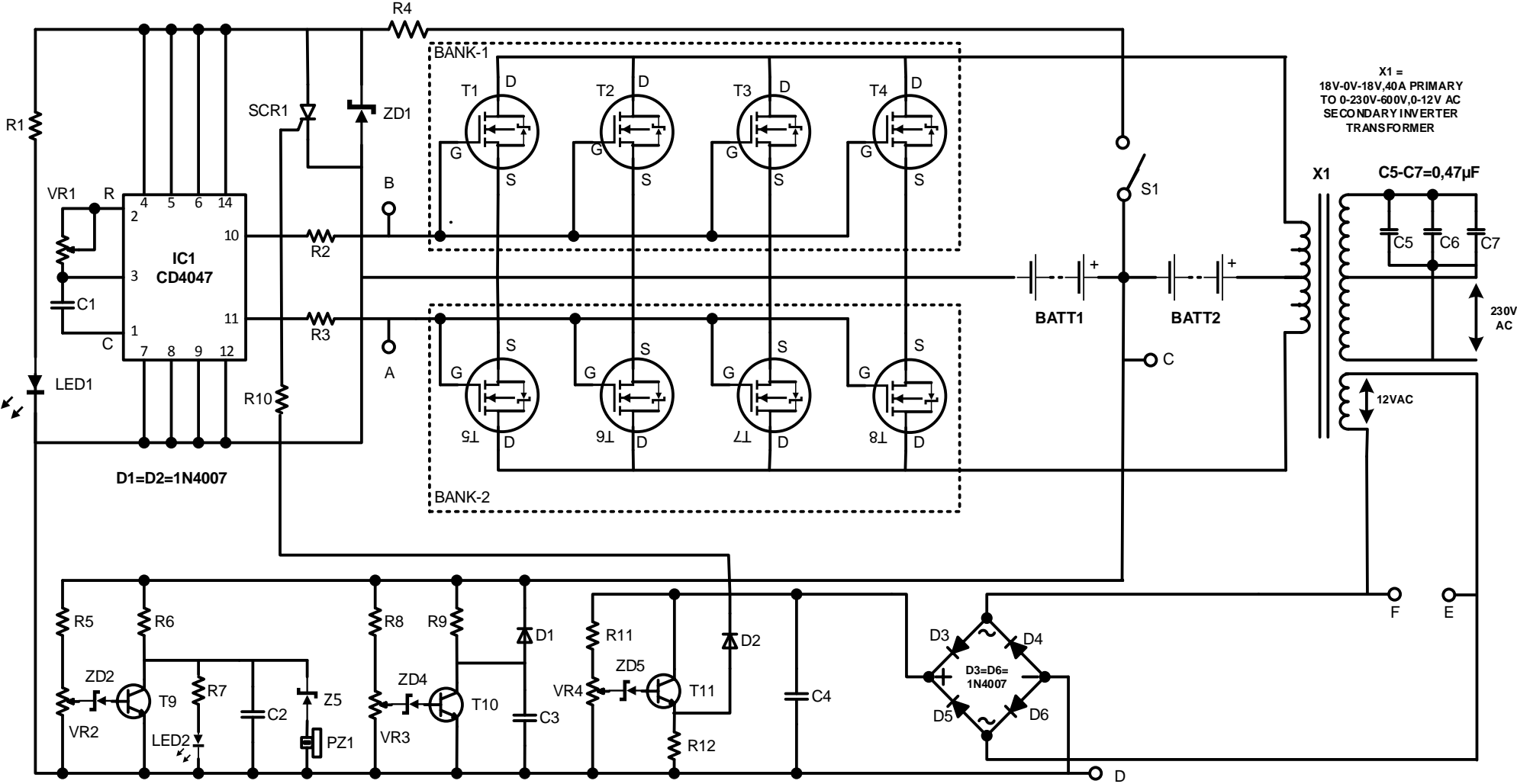

SINE-WAVE INVERTER CIRCUIT DIAGRAM

It comprises a CD4047 multivibrator (IC1), MOSFET, IRF250 MOSFETs (T1 through T8), transistors, and a few discrete components.

IC CD4047 has built-in facilities for a stable and bistable multivibrator. The inverter application requires two outputs that are 180 degrees out of phase. Therefore, IC1 is wired to produce two square-wave output signals at pins 10 and 11 with 50 Hz frequency, 50% duty cycle, and 180-degree phase shift. The oscillating frequency is decided by external pre-set VR1 and capacitor C1.


These two signals drive the two MOSFET banks (bank-1 and bank-2) alternatively. When pin 10 of IC1 is high and pin 11 low, MOSFETs of bank-1 (T1 through T4) conduct, while MOSFETs of bank-2 (T5 through T8) remain in the non-conducting state.

Therefore, a large swing of current flows through the first half of the primary winding of inverter transformer X1 and 230V AC develops across the secondary winding. During the next half cycle, the voltage at pin 10 of IC1 goes low, while the voltage at pin 11 is high. Thus, MOSFETs of bank-2 conduct, while the MOSFETs of bank-1 remain non-conducting. Therefore current flows through the other half of the primary winding and 230 V AC develops across the secondary winding. This way an alternating output voltage is obtained across the secondary winding.

The sine wave output is obtained by forming a tank circuit with the secondary winding of the inverter transformer in parallel with capacitors C5 through C7. Two 2,2 μ F capacitors are connected to the gates of the MOSFETs in both banks with respect to the ground if a proper sine wave is not produced.

The natural frequency of the tank circuit is adjusted to 50 Hz. Current consumption with no load is only 500 mA due to the 50% duty cycle of the square-wave signal. As the load is increased, current consumption increases. The supply voltage to IC1 is limited to 5,1 volts by using Zener ZD1 and resistor R4 with the external battery.

LOW-BATTERY INDICATOR CIRCUIT

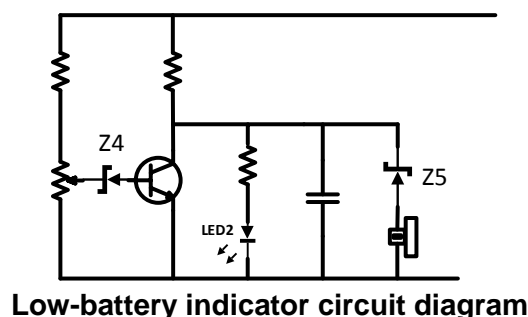


Low-battery indicator circuit diagram

The low-battery indication circuit consists of transistor T9, pre-set VR2, Zener diode ZD2, resistors R5, R6, and R7, LED2, and capacitor C2. The 12 V supply voltage from BATT.1 is applied to the low-battery indicator circuit with a full load (not more than 1 000 watts) connected to the inverter output.

The voltage across the load is 230 V AC. At this instant, adjust pre-set VR2 such that Zener diode ZD2 and transistor T9 conduct to drop the collector voltage to 0.7 volt keeping LED2 'off.' If the supply voltage goes below 10.5 volts, the voltage across the load decreases from 230 V AC to 210 V AC.

At this instant, Zener diode ZD2 and transistor T9 do not conduct, and hence the collector voltage increases to about 10.5 volts and LED2 glows to indicate the low voltage of the battery.

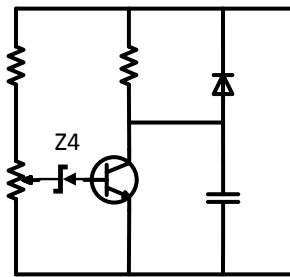LOW-BATTERY CUT-OFF CIRCUIT**Low-battery cut-off circuit diagram**


If the battery is discharged to zero volts repeatedly, the battery life will decrease. The low-battery cut-off circuit consists of transistor T10, pre-set VR3, Zener diode ZD4, resistors R8 and R9, capacitor C3, and diode D1.

Adjust pre-set VR3 such that when the voltage across the load is above 200 volts, Zener diode ZD4 and transistor T10 conduct. The collector voltage of T10 is about 0.7 volts in this case and hence the SCR (SCR1) will not conduct. However, if the voltage across the load goes below 200 volts, Zener diode ZD4 and transistor T10 will not conduct and the collector voltage of T10 will increase, causing the SCR to conduct. Once the SCR conducts, the supply voltage to IC1 (CD4047) will be 0.7 volts, due to which IC1 will be unable to produce the voltage pulses at output pins 10 and 11 and the inverter will turn off automatically. During this state, the SCR remains conducted.

The low cut-off of the inverter can be set at the load voltage of 170 volts for the tube light, fan, etc. So the tube light and fan will not be switched off until the voltage goes below 170 volts.

NO-LOAD CUT-OFF CIRCUIT

If there is no load connected to the output of the inverter, the output voltage is 270 to 290 volts. This voltage is sensed by the 0-12V tap at the secondary winding of inverter transformer X1, which is connected to the no-load cut-off circuit comprising Zener diode ZD5, transistor T11, pre-set VR4, resistors R12 and R11, and capacitor C4.

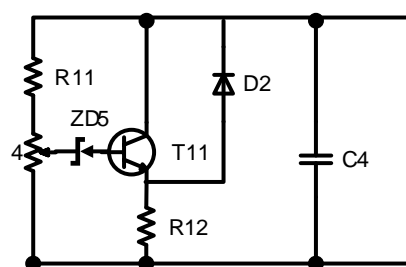**No-load cut-off circuit diagram**

When no load is connected, the voltage at the 12 V tap will also increase. This voltage is rectified by the full-wave bridge rectifier comprising diodes D3 through D6, filtered by capacitor C4 and given to transistor T11.

Adjust pre-set VR4 such that if the inverter voltage goes above 250 volts, Zener diode ZD5 and transistor T11 conduct. This increases the emitter voltage; hence the SCR fires to switch the inverter 'off.' When a proper load is connected, the inverter will automatically turn on.

SINE-WAVE INVERTER PCB DESIGN

An actual size, single-side PCB for the pure sine wave inverter circuit is shown below.

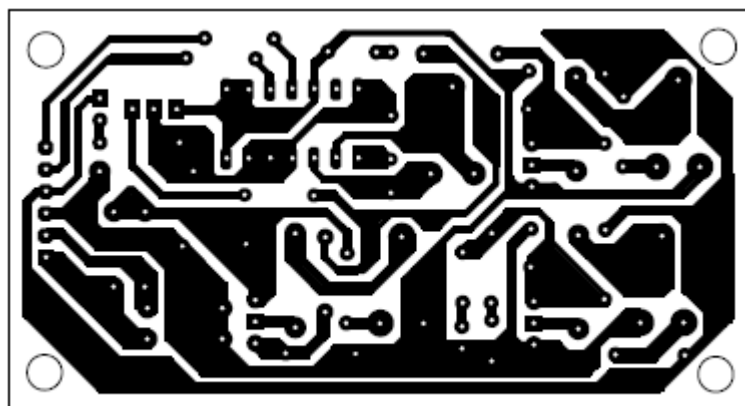


Fig. 2: An actual-size, single-side PCB for the sinewave inverter

A PCB for the sine-wave inverter circuit

A suitable connector CON1 is provided on the PCB to connect the MOSFET banks and the transformer externally. Connector CON1 pins A through F are also marked on the schematic. Assemble the circuit on a PCB as it saves time and minimizes assembly errors. Carefully assemble the components and double-check for any overlooked errors. MOSFETs should be mounted over heat sinks using mica spacers as the insulators between them.

SINE-WAVE INVERTER PCB LAYOUT

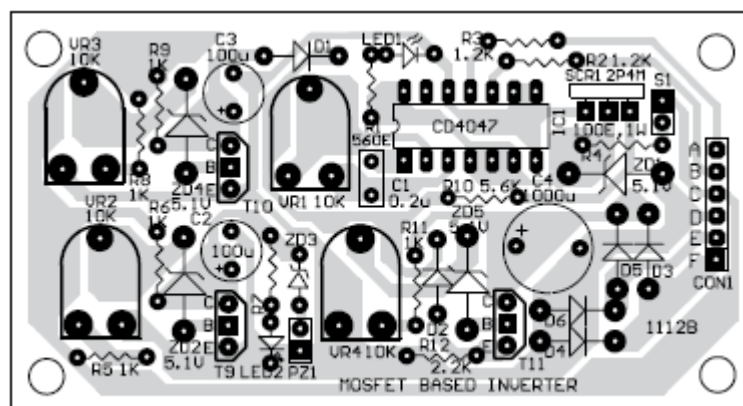


Fig. 3: Component layout for the PCB

Sine-wave inverter PCB layout

Connect the 24V supply terminal directly to the centre tap of the primary winding of the inverter transformer, which carries a maximum current of more than 50 amperes with 1 000 watts.


The current depends on the load applied. There is no need to add a switch in the high-current path to make the inverter turn on and off. The inverter can be switched on and off by low-current switch S1.

OR

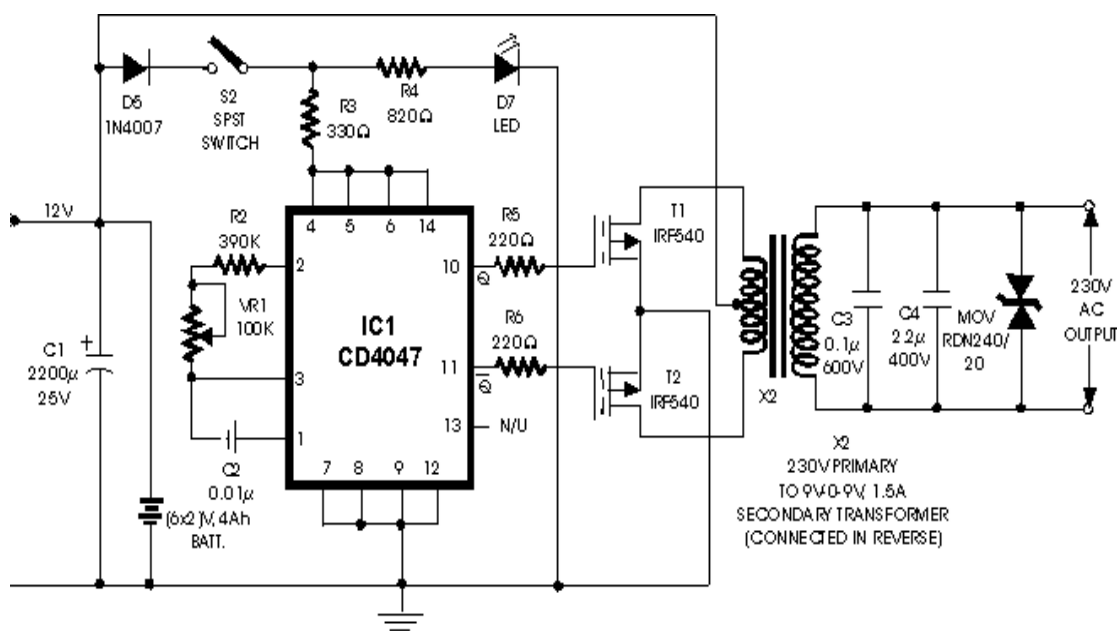6.4 Practical Project 6.4: SQUARE WAVE INVERTER 100 W 12 VDC TO 230 VAC BY IC 4047 – IRF540

A 100 W inverter circuit converts 12 VDC to 230 VAC with IRF540. The circuit applied IC 4047 to generate a continuous wave signal and IRF540 to amplify the signal to be stepped up by the transformer.

NOTE: You will need a 2–3 A centre-tapped transformer to handle/supply a 100 W load.



INVERTER 100 W 12 VDC TO 230 VAC BY IC 4047 – IRF540

| COMPONENT LIST | | | |
|---|-----------|--------------------------|---------------|
| Diode | 1N4007 | VR1 | 100 KΩ |
| C1 | 2 200 μF | R2 | 390 KΩ |
| C2 | 0,01 μF | R3 | 330 Ω |
| C3 | 0,1 μF | R4 | 820 Ω |
| C4 | 2,2 μF | R5 | 220 Ω – 330 Ω |
| D5 | 1N4007 | R6 | 220 Ω – 330 Ω |
| D7 | LED | | |
| MOV | RDN240/20 | | |
| IC 4047 – IRF540 | | 2 x D MOSFET (T1) IRF540 | |
| LED | | S2 SPST switch | |
| Supply 12 V or 12 V DC supply for testing | | | |
| TRANSFORMER on circuit diagram optional; a smaller one can be used for testing. | | | |

NOTE: All circuits MUST include an On/Off switch with an ON indicator and fuse protection.

7. CONCLUSION

On completion of the practical assessment task, learners should be able to demonstrate their understanding of the industry, enhance their knowledge, skills, values and reasoning abilities as well as establish connections to life outside the classroom and address real-world challenges. The PAT furthermore develops learners' life skills and provides opportunities for learners to engage in their own learning.